
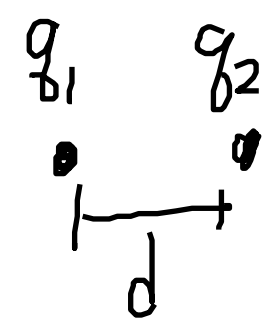


force $F = k \frac{|q_1 q_2|}{d^2}$

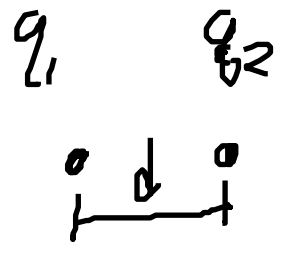


N

energy $PE = k \frac{q_1 q_2}{d}$




J

$V = k \frac{q_s}{d}$

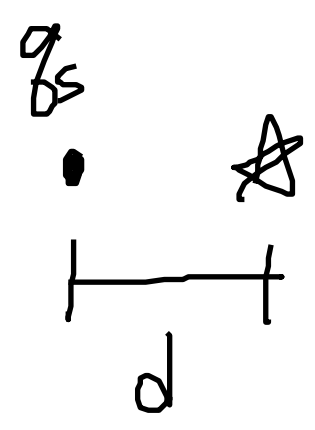

V

HW7 #2

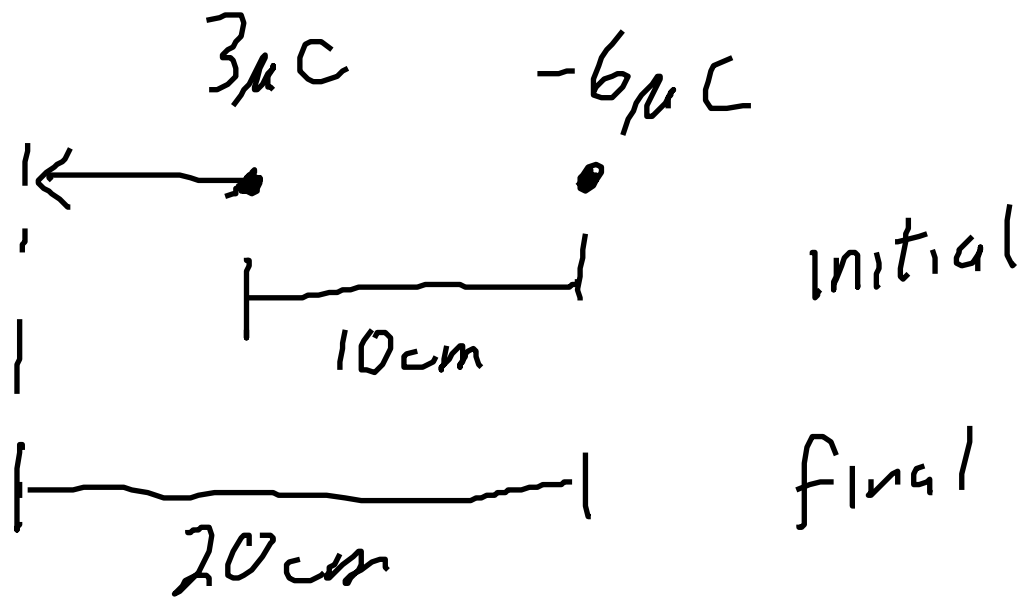


What is change in PE?

$$\Delta PE = PE_f - PE_i$$

$$PE_i = (9 \times 10^9) \frac{(3 \times 10^{-6})(-6 \times 10^{-6})}{(10 \times 10^{-2})} = -1.6\text{J}$$

$$PE_f = (9 \times 10^9) \frac{(3 \times 10^{-6})(-6 \times 10^{-6})}{(20 \times 10^{-2})} = -0.8\text{J}$$
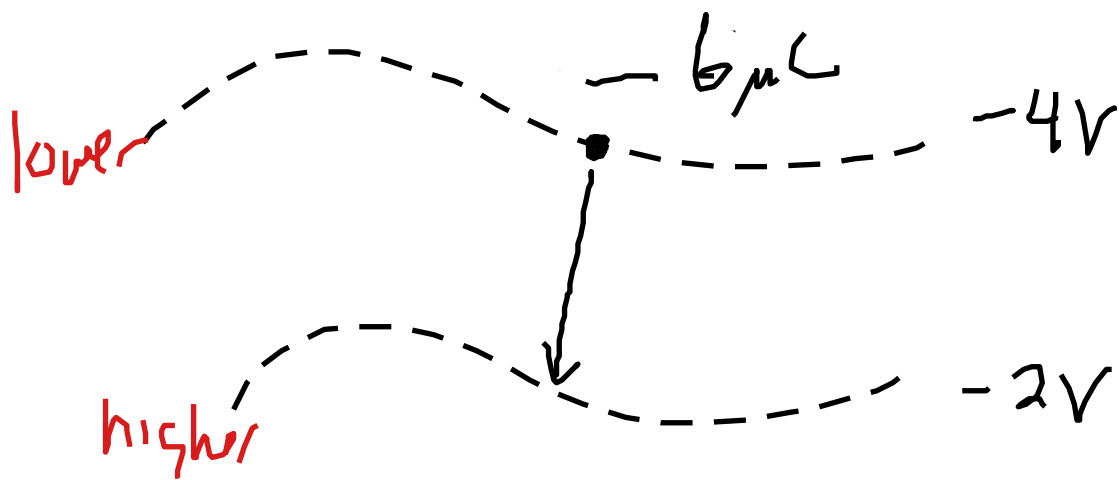
$$\Delta PE = (-0.8) - (-1.6) = -0.8 + 1.6 = \boxed{+0.8\text{J}}$$



$$\Delta PE = q \Delta V$$

$$\Delta PE = (-6 \times 10^{-6}) (V_f - V_i)$$




$$= (-6 \times 10^{-6}) (-2 + 4)$$

$$= -12 \times 10^{-6} \text{ J}$$


$$= -12 \mu\text{J} \quad \text{😊}$$

negative charges like
going uphill


Schematic Diagrams

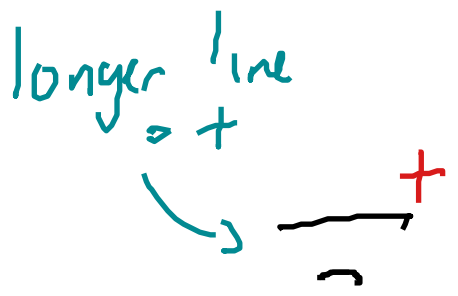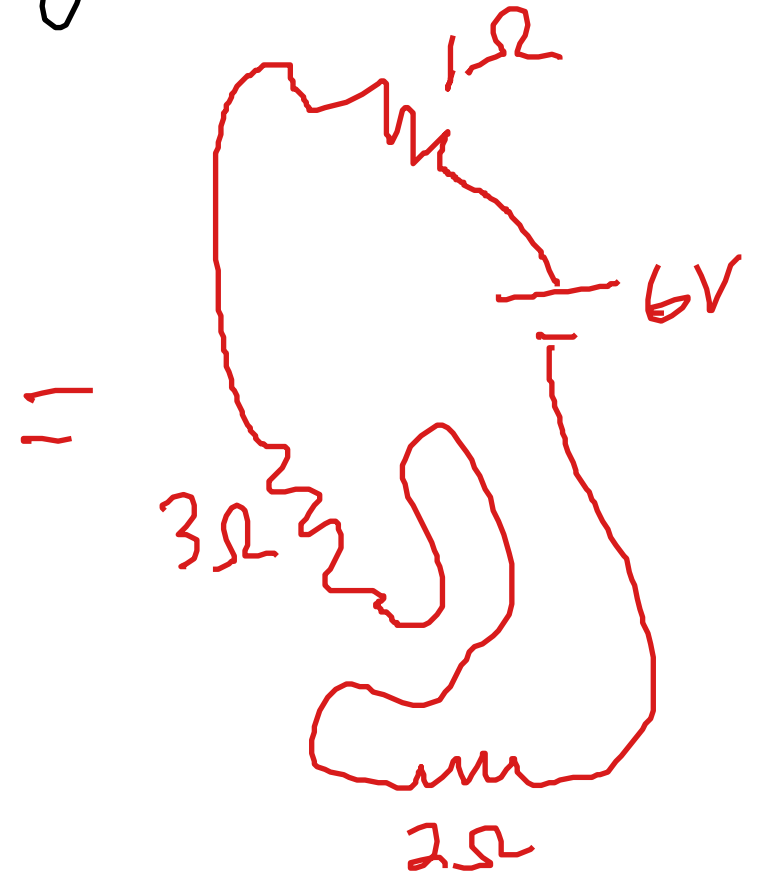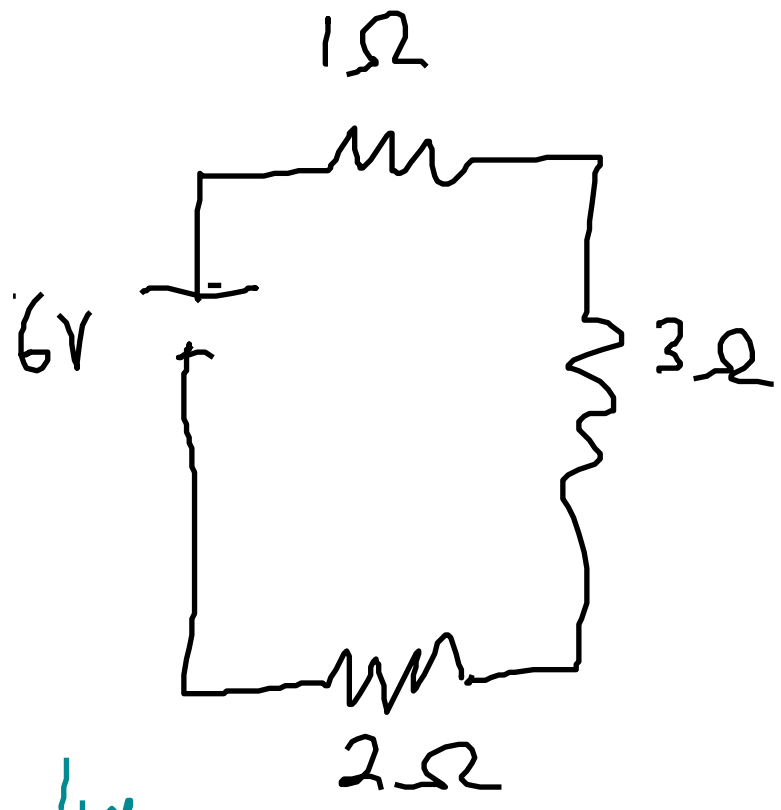

battery / power supply

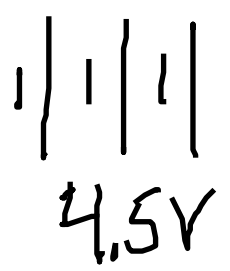


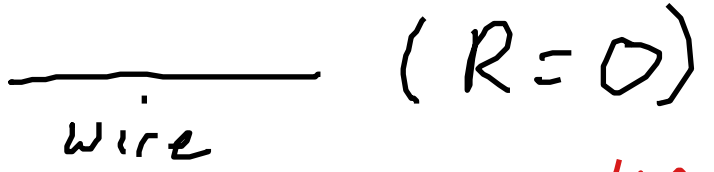"emf" \mathcal{E} of battery
potential difference across
the battery



V is same everywhere along
the wire

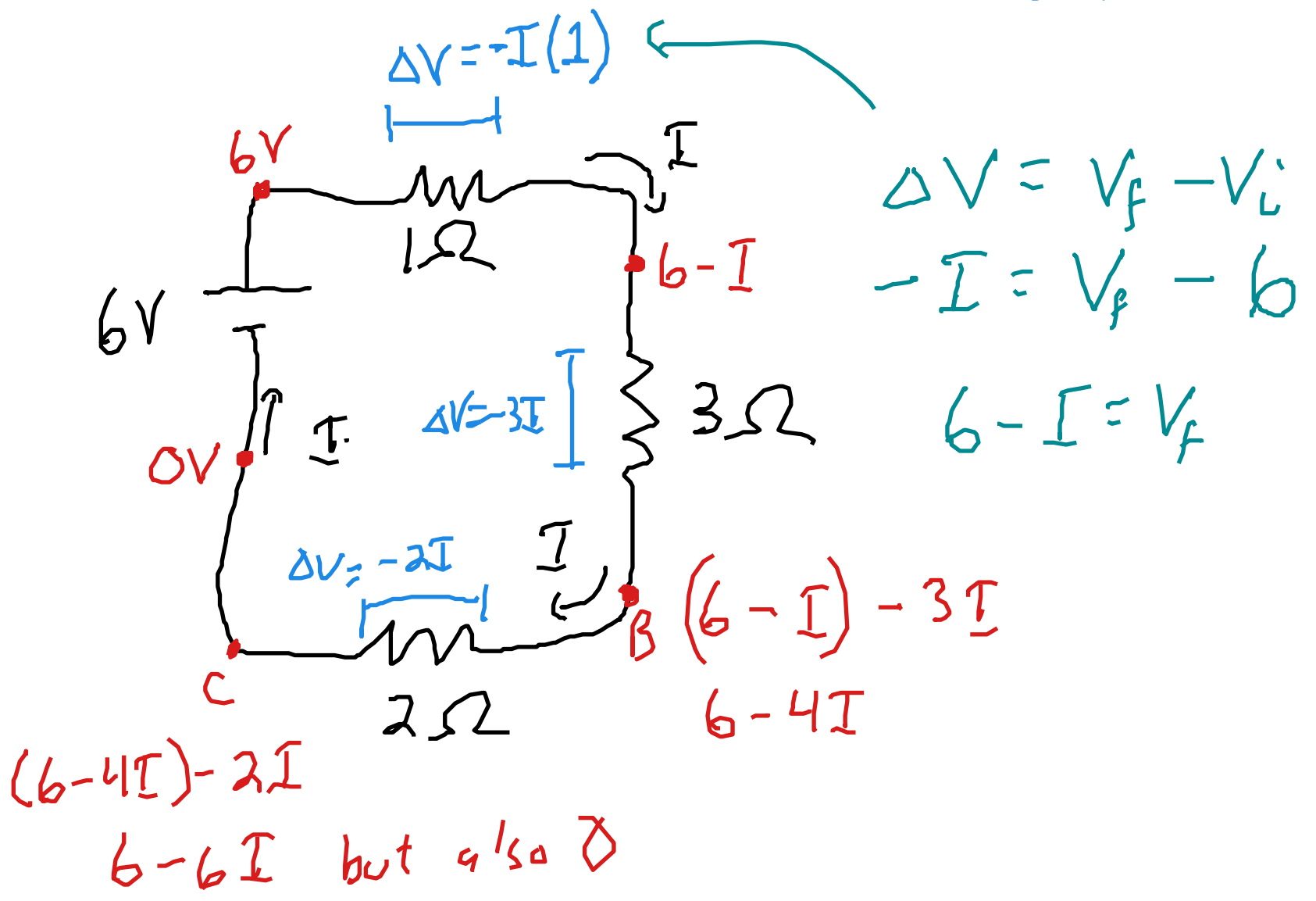Shape doesn't matter,
 the connections do. Ohm's Law
 $\Delta V = IR$



There's only one current where
 we avoid a contradiction

$6 - 6I = 0$
 $\rightarrow 6 = 6I \rightarrow I = 1A$

6

$$P = I \Delta V = I^2 R$$

6V battery supplies $P = (1A)(6V) = 6W$

1Ω resistor takes $P = (1A)^2(1Ω) = 1W$

3Ω takes 3W

2Ω takes 2W

resistors take 6W } consistent
battery supplies 6W }