

# Conductors vs Insulators


- have free-flowing charge carriers inside

(e.g. electrons in a metal)


- charge can flow through material easily

- no/few charge carriers inside

- charge can't flow easily

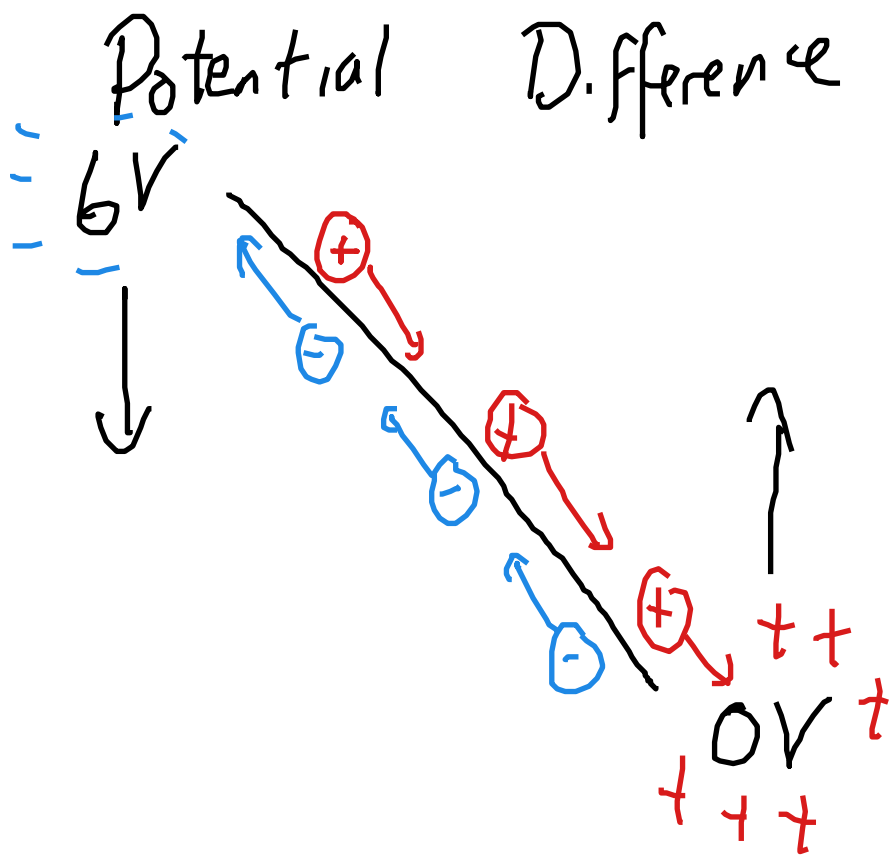

⋮

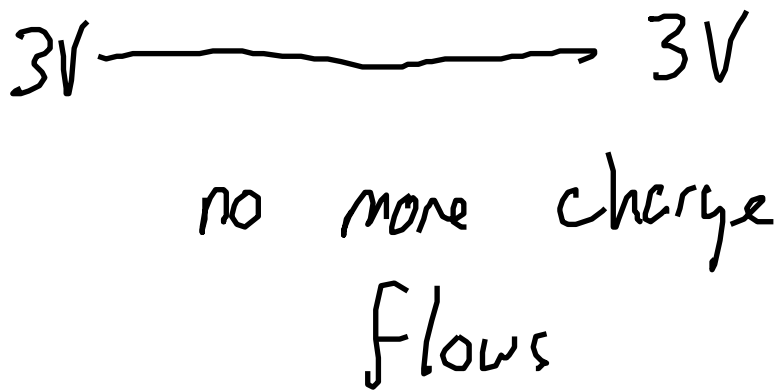

In a


conductor;

charge carriers

flow until

potential is

the same everywhere in conductor

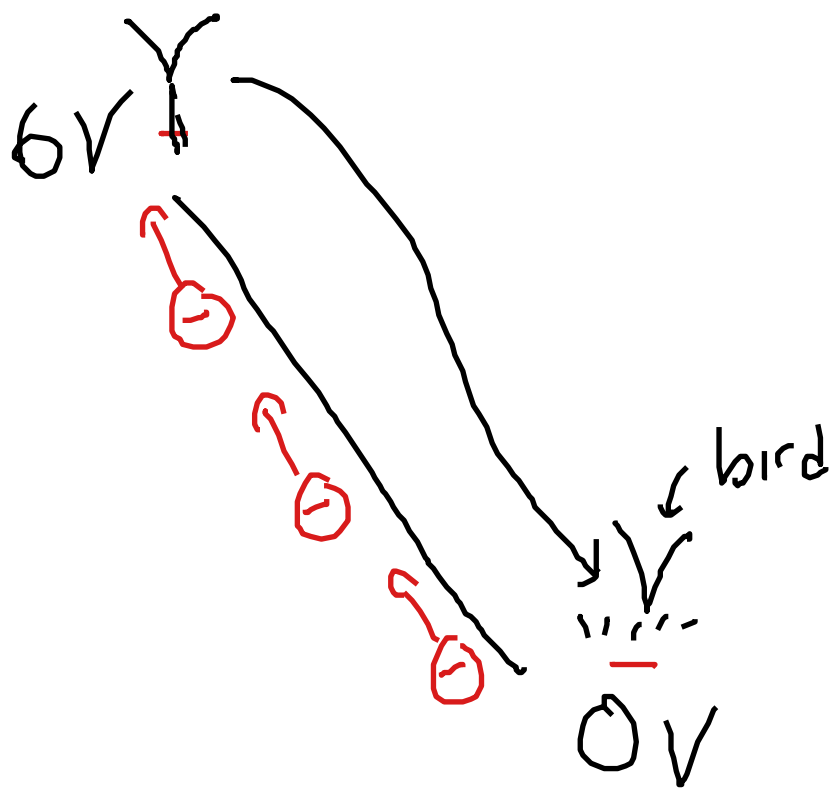

if this process is thwarted  
(charge carriers are continuously  
moved back to their  
starting point)

then charge flow doesn't stop.


flow of charge: current

Current :  $I$  :  $\frac{\text{Charge}}{\text{second}}$

Units of  $I$ :  $1 \frac{C}{s} = 1 \text{ Ampere (A)}$


$1 \text{ A}$  is large but not crazy

$1 \text{ C}$  is crazy large

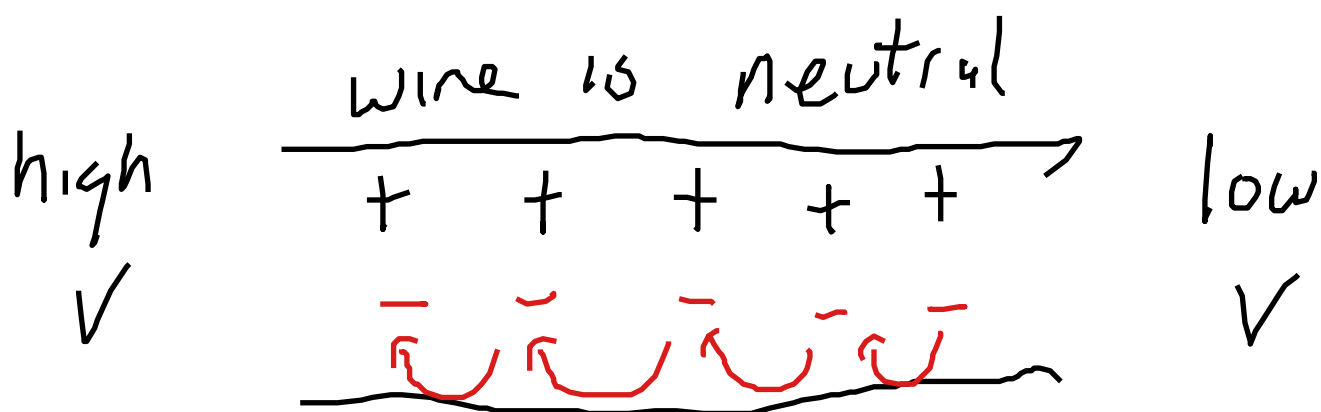


No buildup of charge so long as current makes a closed circuit

# Cut in the wire

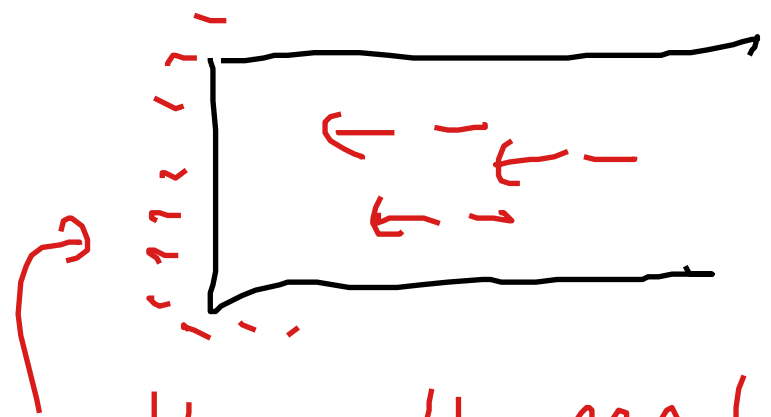

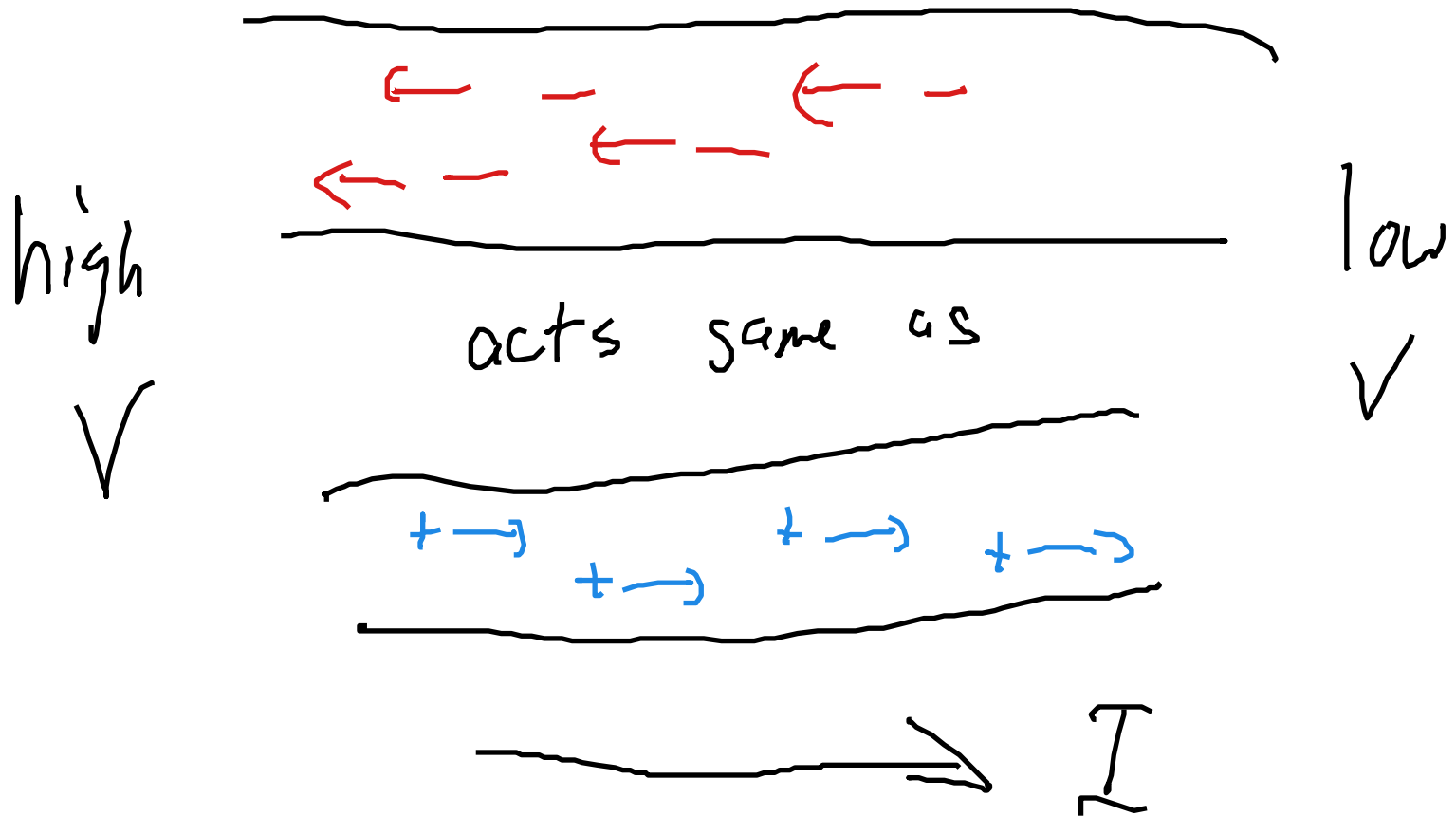this will repel  
newer electrons.  
current will stop (quickly)





"conventional current"!

- direction positive charge carriers would be moving
- flows downhill: high to low  $V$
- electrons move opposite  $I$
- $I$  has direction but is not a vector: only  $\underline{I}$ .

7  
To thwart equilibrium in a conductor  
requires energy

- battery
- power supply

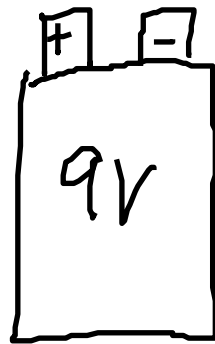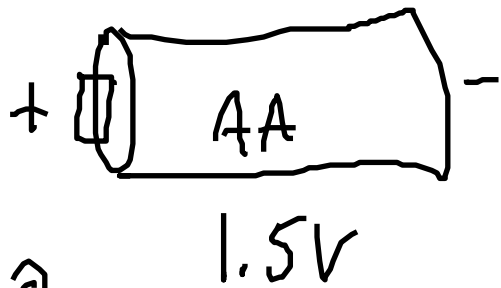

Positive terminal is 1.5V higher  
than the negative terminal  
A battery's primary job is to  
maintain this potential difference


battery  
wants  
to  
maintain  
 $\Delta V$



Wire  
wants  
potential  
to be  
equal

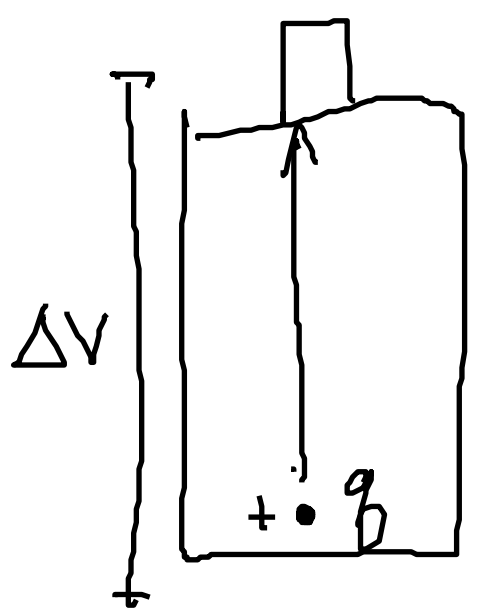- battery acts like a pump,  
moving current back uphill
- battery supplies energy to  
current
- current dissipates energy as it  
flows downhill





# Potential difference

$$\Delta V = V_f - V_i$$

Energy gained by charge :

$$\Delta PE = q \Delta V$$

Power =  
Energy  
per  
second

$$\frac{\Delta PE}{\text{time}}$$

$$= \frac{q \Delta V}{\text{time}}$$

"per second"


$$P = I \Delta V$$

Power: units of  $\frac{\text{Joules}}{\text{second}} = \text{Watt (W)}$

• When current flows up a potential difference, it must be supplied  $P = I \Delta V$  of power

• When current flows downhill, it releases  $P = I \Delta V$  of power.

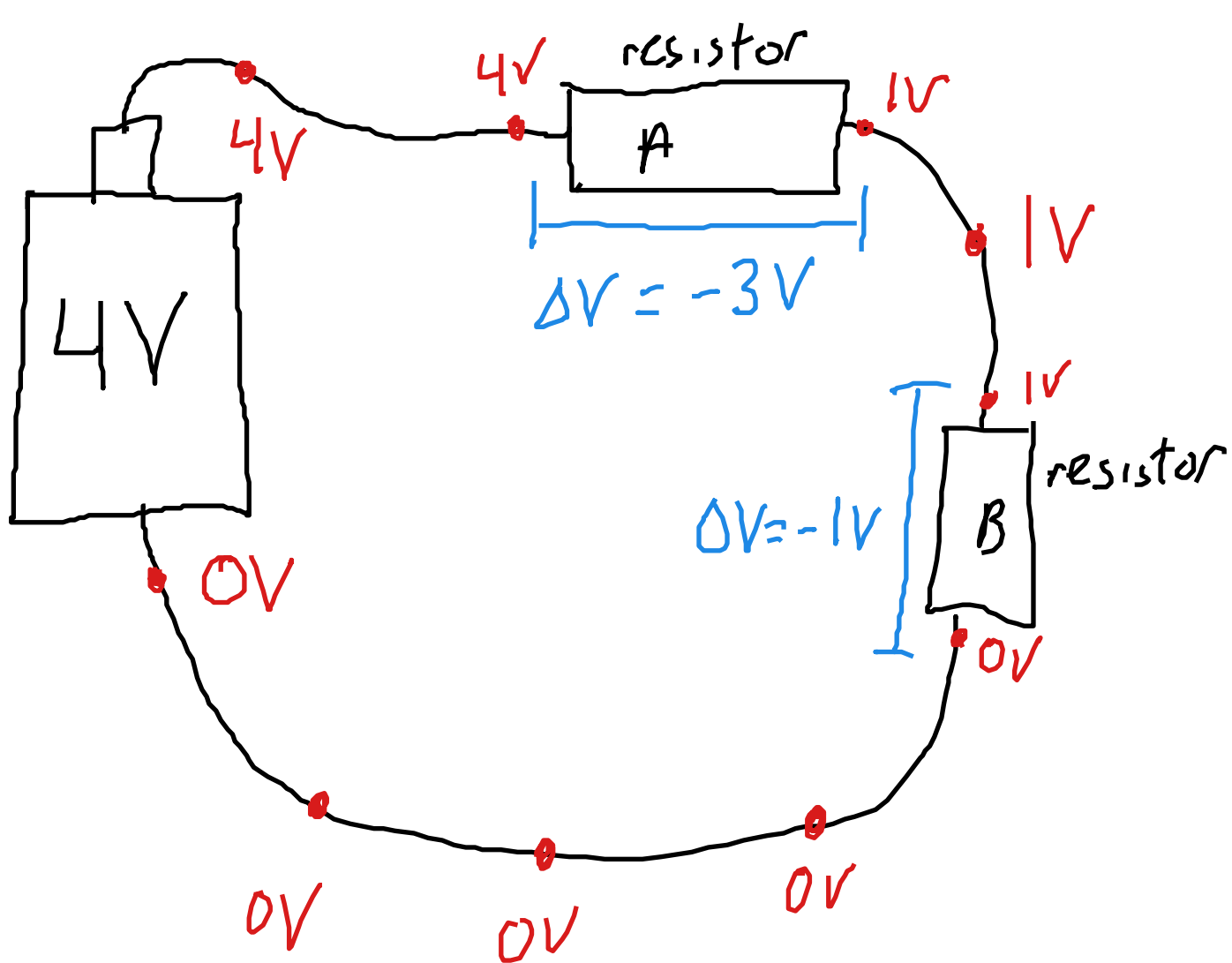Resistors : serve as an obstacle ("friction") to the current, slowing it down



Total change in  $V$   
around a circuit is zero.

4V up, 4V down