

$$I_1 + I_2 = I_3$$

Junction Rule

$$6 - 5I_3 = 0$$

Loop Rules

$$-3 + 6 + 4I_2 = 0$$

$$-4I_2 - 5I_3 + 3 = 0$$

3 unknowns, I_1 , I_2 , I_3

→ need 3 equations

Start with equations having
only one variable


$$6 - 5I_3 = 0 \rightarrow 5I_3 = 6 \rightarrow I_3 = 1.2A$$

$$\underbrace{-3 + 6}_{3} + 4I_2 = 0 \rightarrow 4I_2 = -3$$

$$I_2 = -0.75A$$


$$I_1 + I_2 = I_3 \rightarrow I_1 - 0.75 = 1.2$$

$$I_1 = 1.2 + 0.75 = 1.95A$$

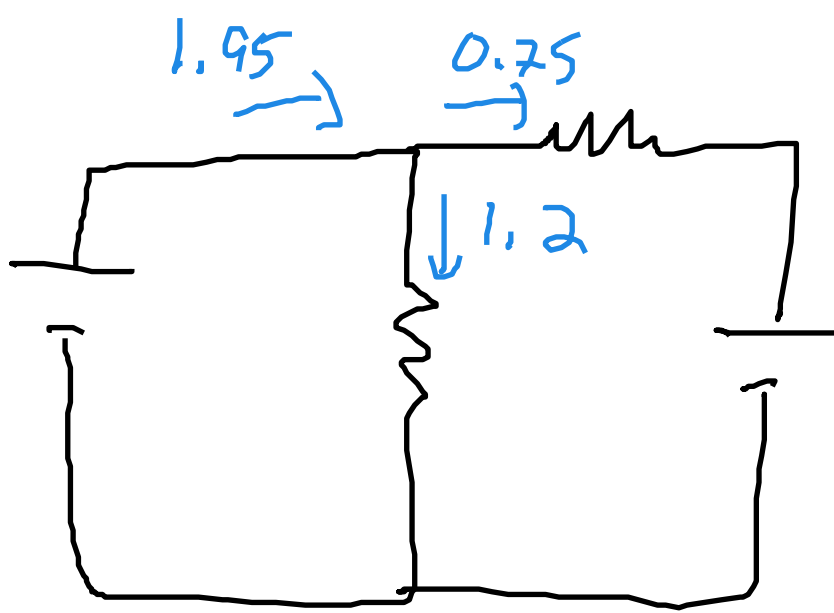

Redraw with correct currents

if you wish —
double-check junction rule

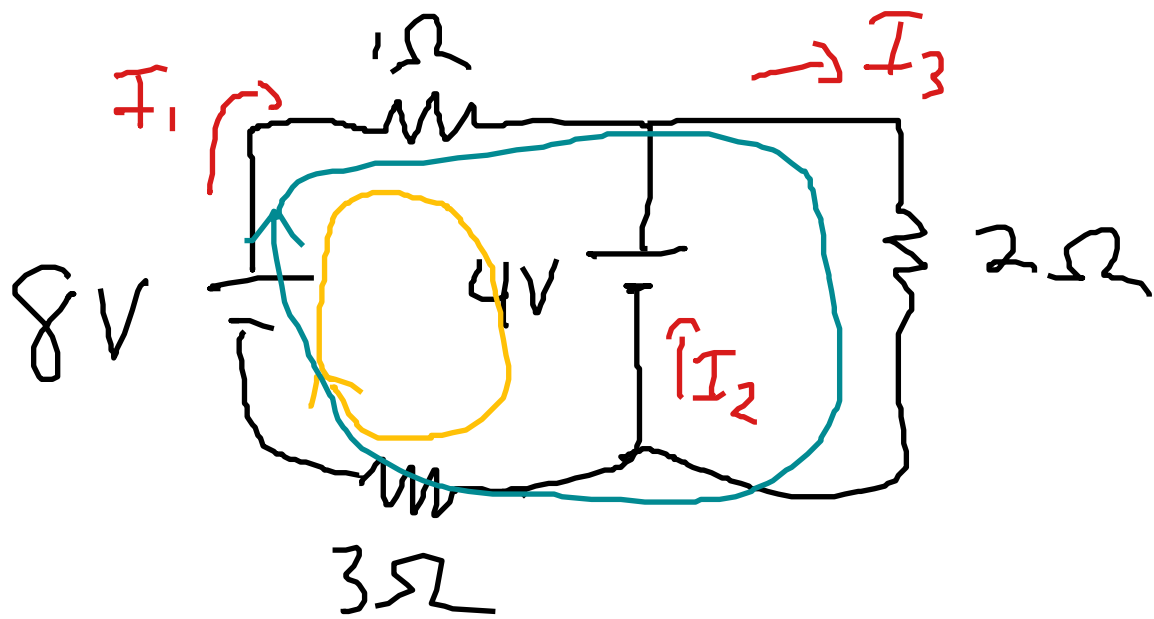

I_1
 I_2
 I_3

$$I_1 = I_2 + I_3$$

$$8 - 1I_1 - 4 - I_2 - 3I_1 = 0$$

$$8 - 1I_1 - 2I_1 - 3I_1 = 0$$

Real equations

$$\textcircled{3} \quad \underline{I}_1 + \underline{I}_2 = \underline{I}_3$$

$$8 - 1\underline{I}_1 - 4 - 3\underline{I}_1 = 0 \quad \leftarrow \begin{array}{l} \text{start} \\ \text{here} \end{array}$$

$$\textcircled{2} \quad 8 - 1\underline{I}_1 - 2\underline{I}_3 - 3\underline{I}_1 = 0$$

$$4 - 4\underline{I}_1 = 0 \rightarrow \underline{I}_1 = 1A$$

$$8 - 4\underline{I}_1 - 2\underline{I}_3 = 0$$


$$8 - 4(1) = 2\underline{I}_3$$

$$4 = 2\underline{I}_3 \rightarrow \underline{I}_3 = 2A$$

$$I_1 + I_2 = I_3$$

$$1 + I_2 = 2$$

$$\rightarrow I_2 = 1A$$

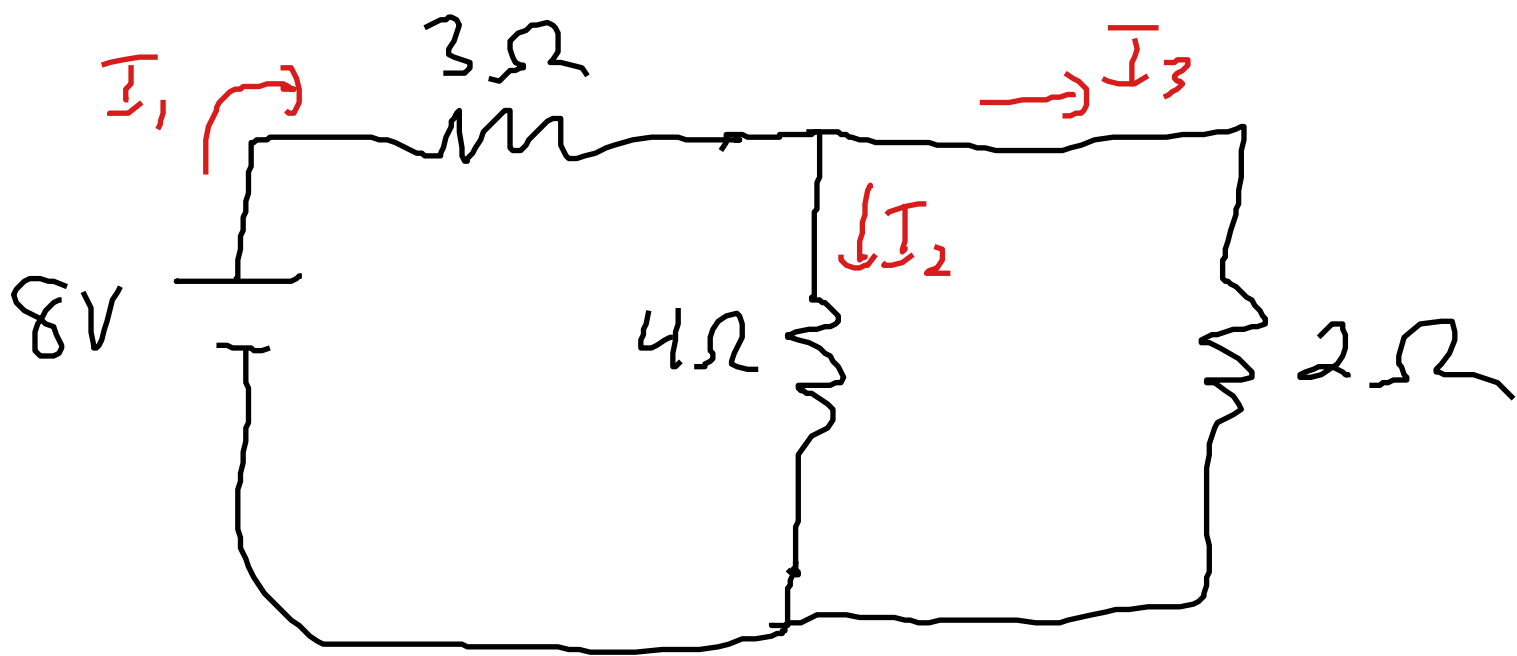

$$I_1 = I_2 + I_3$$

$$8 - 3I_1 - 4I_2 = 0$$

$$-4I_2 + 2I_3 = 0$$

$$8 - 3I_1 - 2I_3 = 0$$

Solve simultaneously (see video)

$$-4I_2 + 2I_3 = 0$$

$$2I_3 = 4I_2$$

$$\frac{I_3}{I_2} = \frac{4\Omega}{2\Omega} \rightarrow I_3 = 2I_2$$

path with half the resistance
gets twice the current

"path of least resistance"