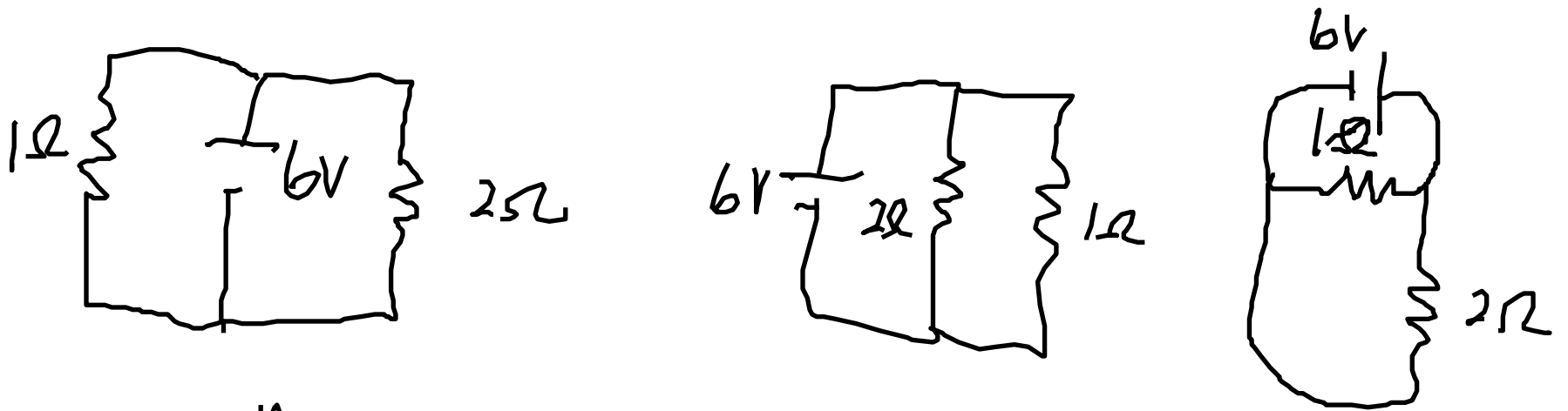



Current in = Current out  
(Steady current)

In this case

$$I_1 = I_2 + I_3$$



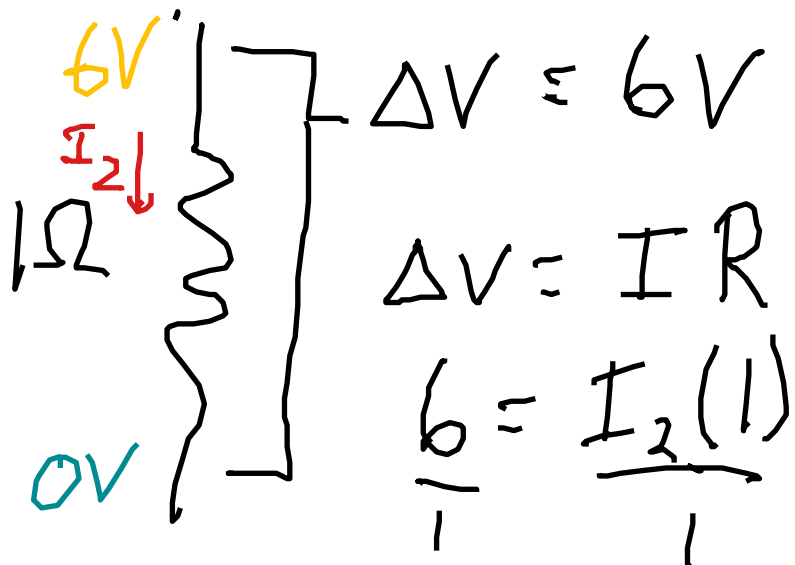All equivalent circuits to  
the one above,




$$\Delta V = 6V$$

$$\Delta V = IR$$

$$6 = \frac{I_2(1)}{1}$$

$$\Rightarrow I_2 = 6A$$

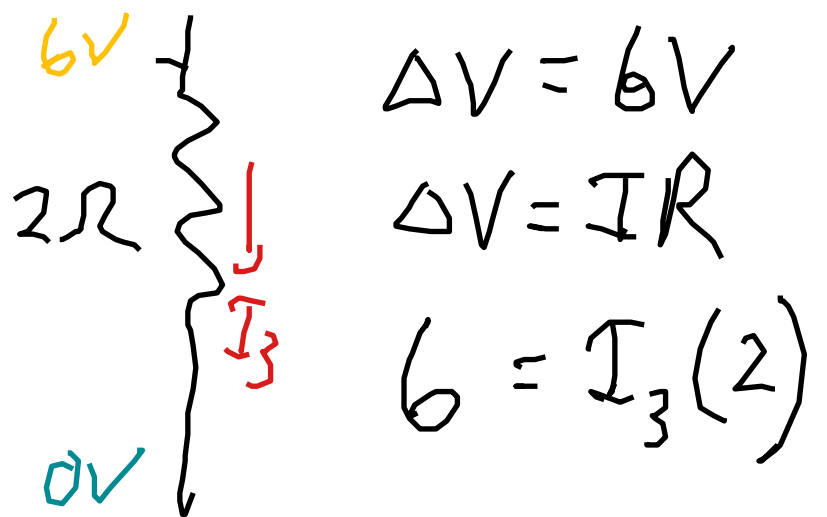


$$\Delta V = 6V$$

$$\Delta V = IR$$

$$6 = I_3(2)$$

$$\rightarrow I_3 = 3A$$


$$I_1 = I_2 + I_3 = 6A + 3A = 9A$$

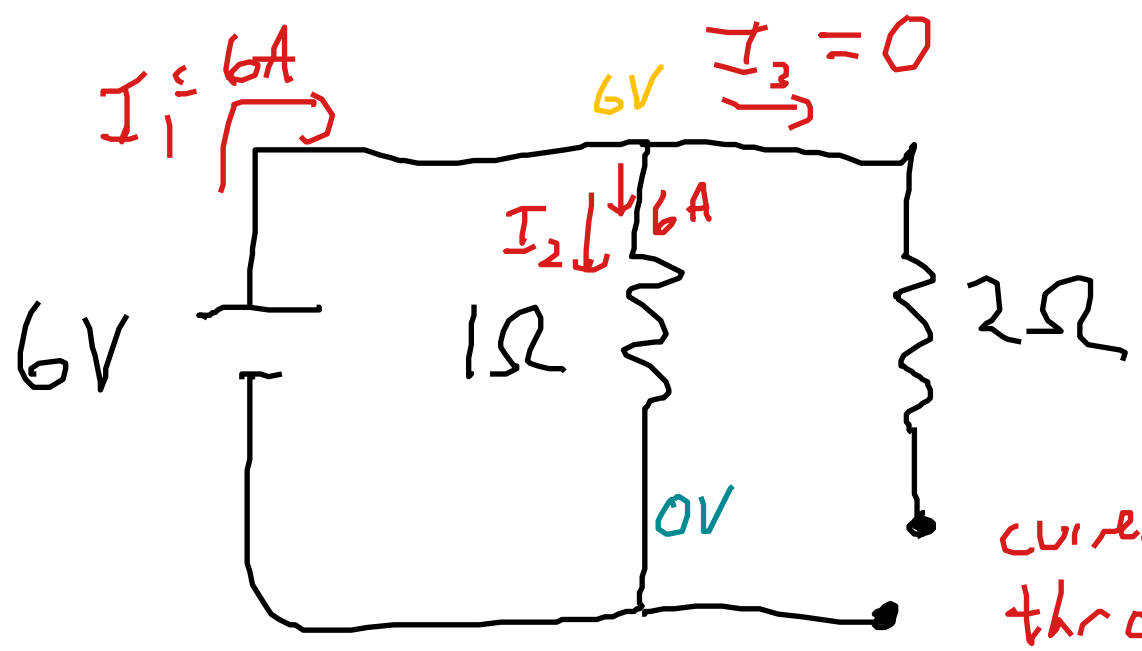

currents can't flow through a gap

What happens to the current through the 1Ω resistor?

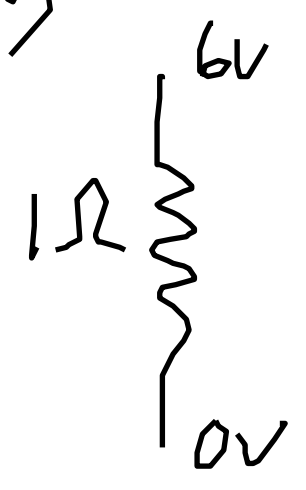
- A) gets bigger (than 6A)
- B) stays same
- C) gets smaller
- D) stops (0A)



$$\Delta V = IR$$

$$6 = I_2 (1)$$

$$I_2 = 6A$$

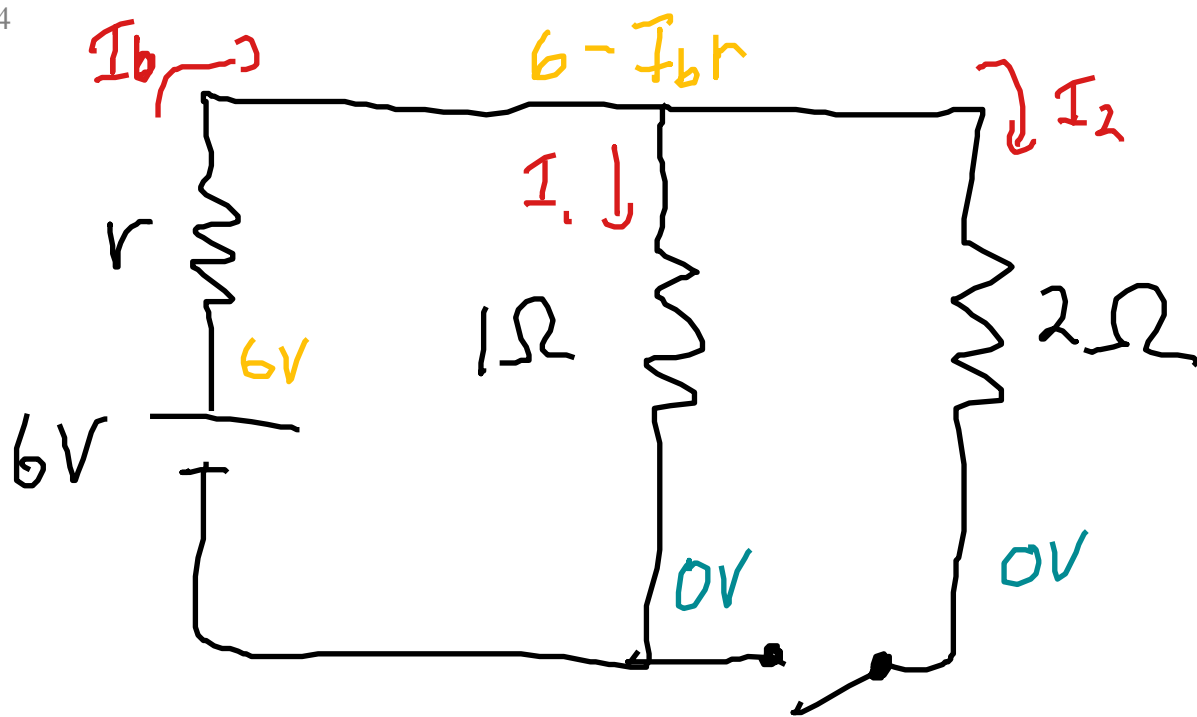

$r$ : internal resistance of power supply

$\Delta V$  across the internal resistance

is  $I_b r$

Remove the 2Ω resistor (open switch)

• then battery supplies less current (intuition)

• then  $6 - I_b r$  gets bigger

•  $\Delta V$  across <sup>smaller</sup> 1Ω is bigger

•  $I_1$  is bigger

$r$  is typically small

• If all other resistances in problem are much bigger than  $r$ , then we can ignore it.

• High-power devices have low resistance maybe less than  $r$ ?

• High-power devices can dim lights