


# Circuit Problems

- Known. battery emfs  
resistances

Solve for currents
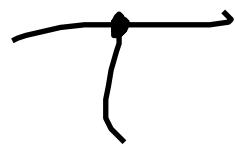
## Kirchhoff's Laws


- junction rule  
for every junction,  
current in = current out



- loop rule

total change of potential  
around any loop is zero.

# Junctions

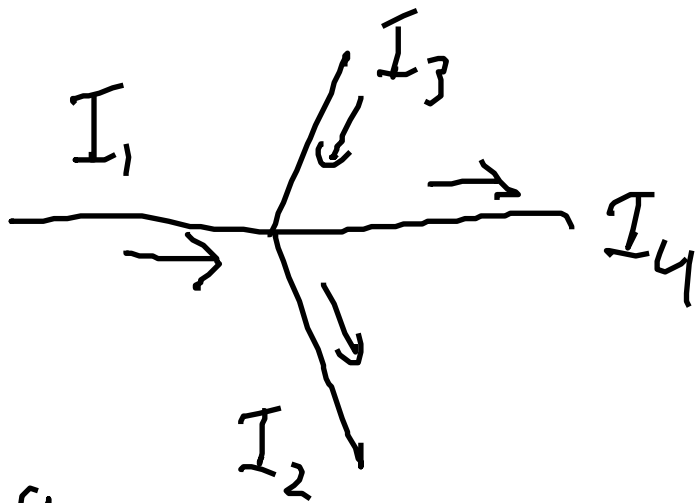

• for each junction,

each wire has a

different label and a direction


"Direction" is like a "positive axis"

( If a current turns out to be a ~~negative~~ number, then it actually goes in the opposite direction )

current in = current out

$$I_1 + I_3 = I_2 + I_4$$

Four unknowns, one equation

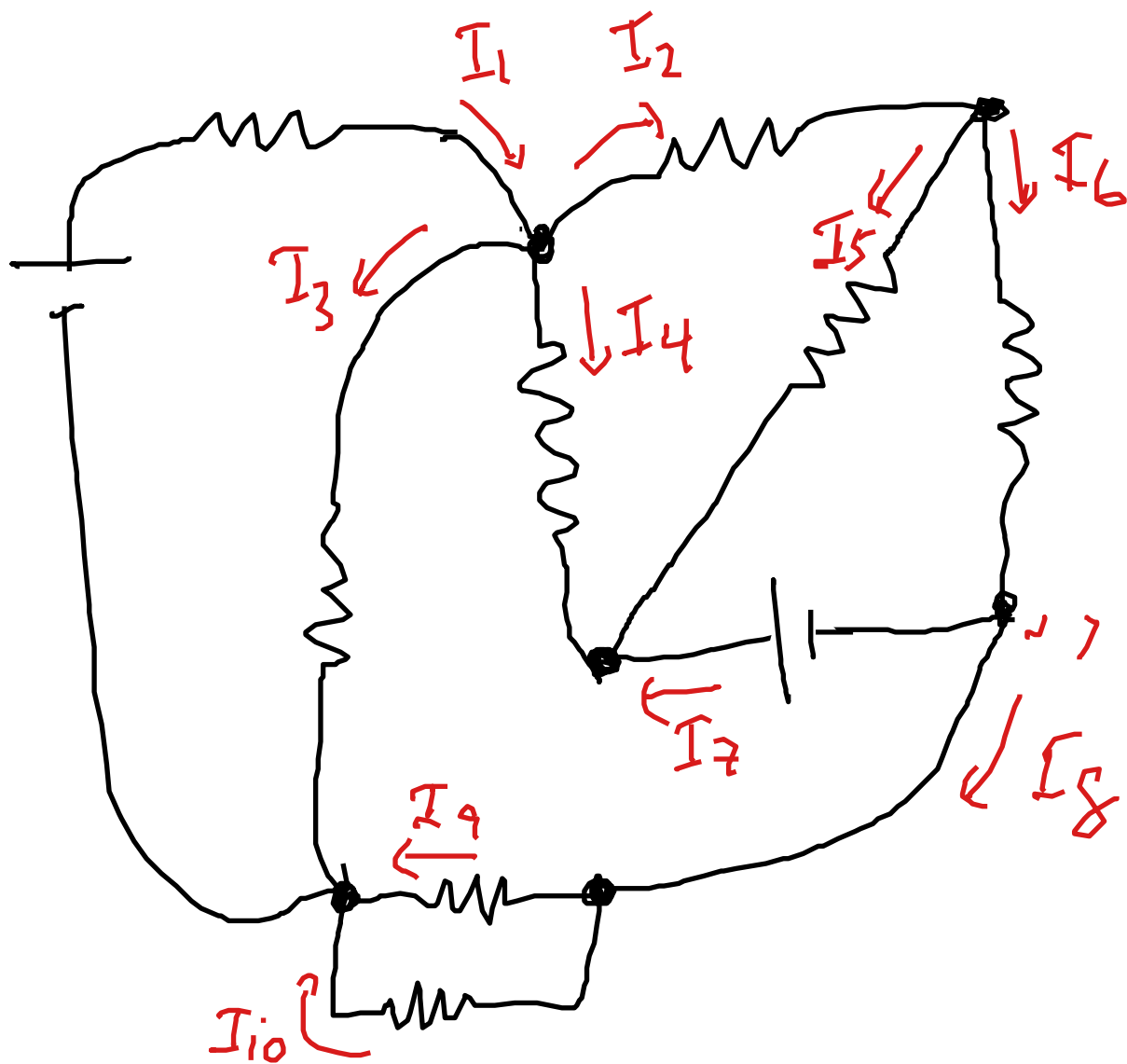

1) Identify currents.

(Use junctions:

every wire at junction has a different label.)

Junction Rule gives us  
1 equation per junction

$$\textcircled{1} \quad I_1 = I_2 + I_3 + I_4$$

$$\textcircled{2} \quad I_2 = I_5 + I_6$$

$$\textcircled{3} \quad I_4 + I_5 + I_7 = 0$$

$$\textcircled{4} \quad I_6 = I_7 + I_8$$

$$\textcircled{5} \quad I_{10} + I_9 + I_3 = I_1$$

$$\textcircled{6} \quad I_8 = I_9 + I_{10}$$

5  
independent  
equations

1

is a  
reworking  
of the  
other 5

ex. ① 
$$I_1 = \underbrace{I_2}_{\textcircled{2}} + I_3 + \underbrace{I_4}_{\textcircled{3}}$$

$$I_1 = I_5 + I_6 + I_3 - I_5 - I_7$$

$$I_1 = \underbrace{I_6}_{\textcircled{4}} + I_3 - I_7$$

$$I_1 = I_8 + I_3$$

$$I_1 = \underbrace{I_9}_{\textcircled{6}} + I_{10} + I_3$$

And I derived  $\textcircled{5}$

At least one junction rule is redundant.

# Loop Rule


total change in potential  
around a closed loop is zero

## Tally Method



1) Pick a point and a direction  
in circuit.


2) Travel through circuit  
keeping track of changes  
in potential ( $\Delta V$ )  
(either  $\mathcal{E}$  or  $IR$ )

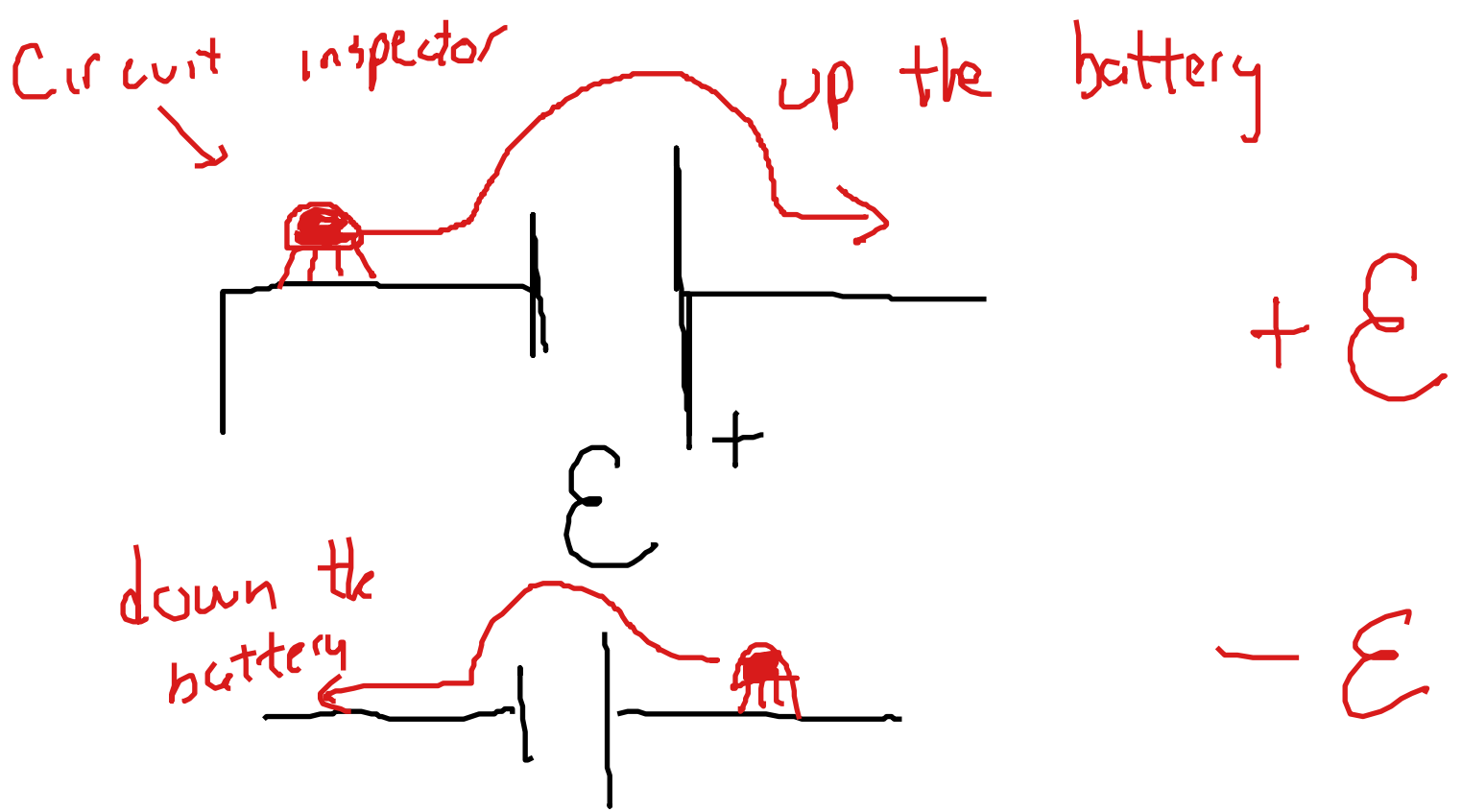3) When you return to starting point,  
sum of changes =  $\square$



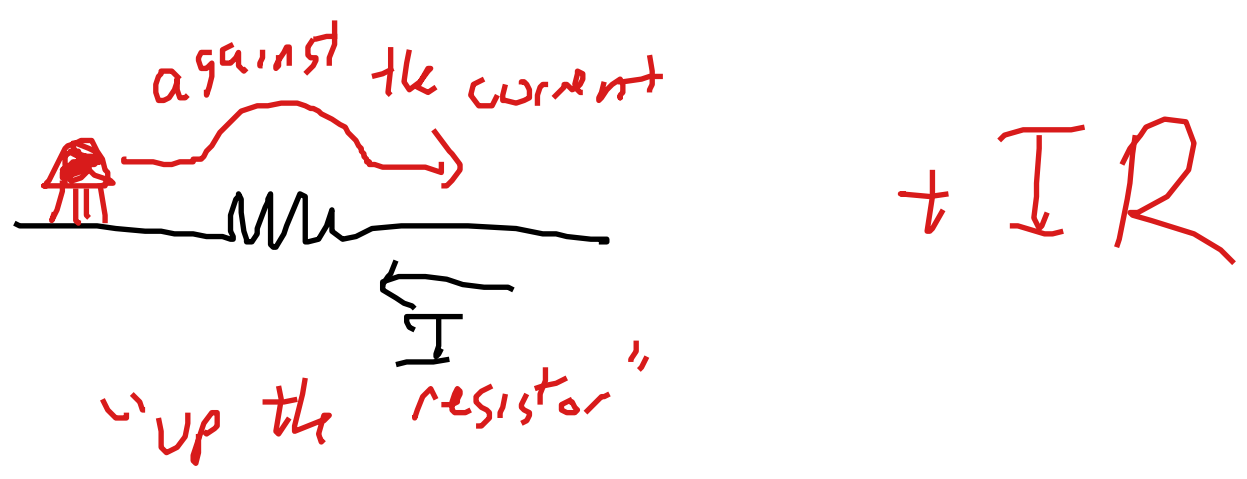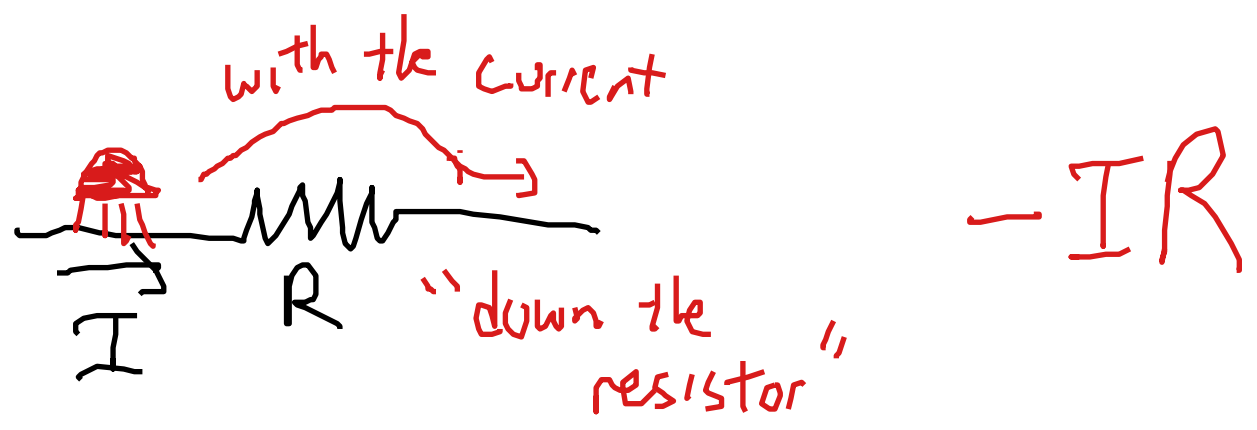(for batteries, current direction doesn't matter)



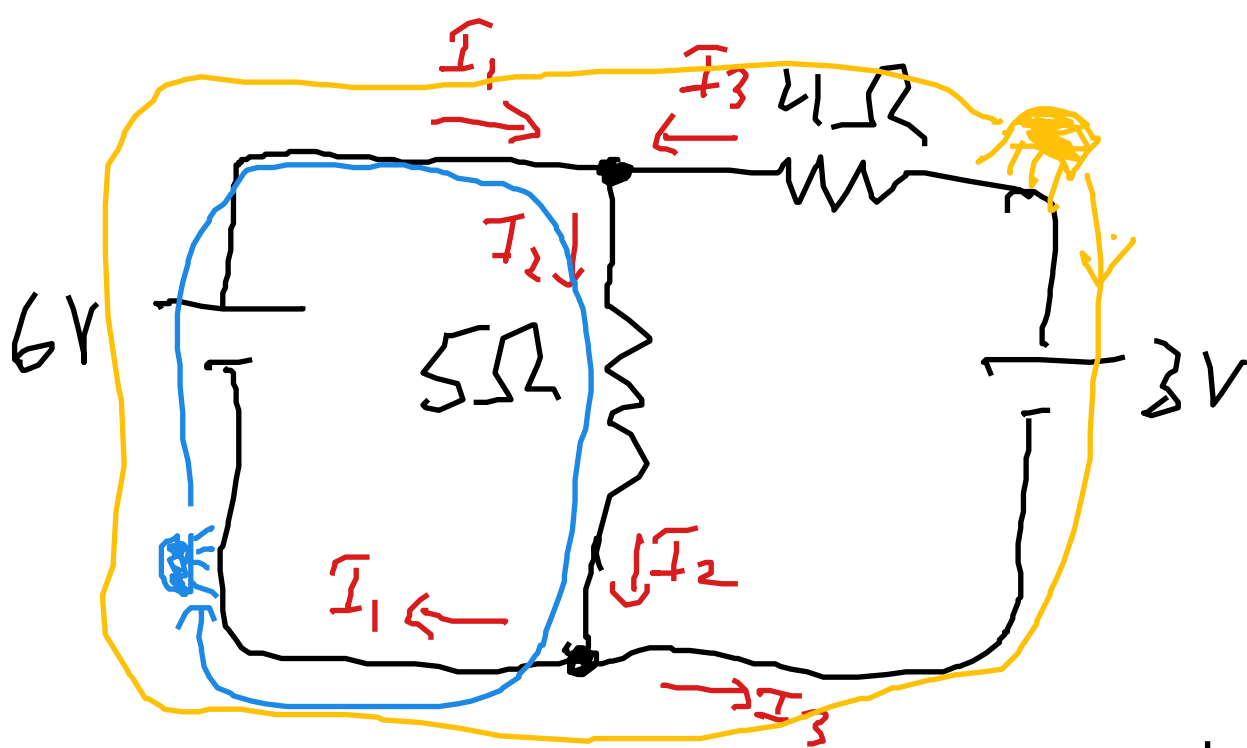

1) I identify the currents, apply junction rule

$$I_1 + I_3 = I_2$$

$$I_2 = I_1 + I_3 \leftarrow \text{redundant}$$

2) Loop rule to get enough equations

$$+6 - 5I_2 = 0 \rightarrow I_2 = \frac{6}{5}$$

$$-3 + 6 + 4I_3 = 0$$