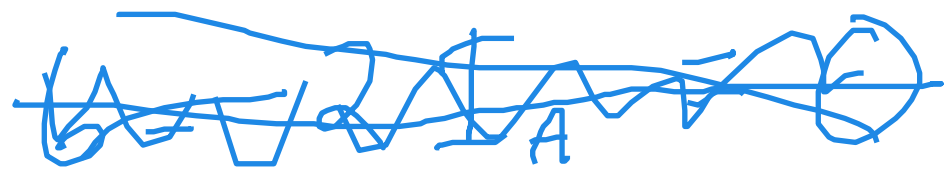


Current in = current out

$$I_A = I_B + I_C$$



$$\begin{aligned} 6 - rI_A - 2I_B &= 0 \\ +rI_A - 6 + 2I_B &= 0 \end{aligned}$$

} different start & direction.
Same loop, same eqns

$$+4I_C - 2I_B = 0$$

$$6 - rI_A - 4I_C = 0$$

Solve for I_A , I_B , I_C

1) Choose one unknown.

2) Write the other unknowns in terms of it.

3) Solve for that choice.

4) Solve for the others

1) Choose I_C .

$$4I_C - 2I_B = 0$$

$$\rightarrow 4I_C = 2I_B$$

$$\rightarrow I_B = 2I_C$$

2) Write I_B in terms of I_C .

2) Write I_A in terms of I_C .

$$I_A = I_B + I_C = (2I_C) + I_C = 3I_C$$

3

3) Solve for I_c

$$6 - rI_A - 2I_B = 0$$

$$6 - r(3I_c) - 2(2I_c) = 0$$

$$6 = 3rI_c + 4I_c$$

$$6 = (3r + 4)I_c$$

$$I_c = \frac{6}{3r + 4}$$

4) Solve for $I_A + I_B$

$$I_A = 3I_c = \frac{18}{3r + 4}$$

$$I_B = 2I_c = \frac{12}{3r + 4}$$

If r is small,
(compared to 2Ω & 4Ω)

$$3r + 4 \approx 4$$

if $r = 0.1$

$$3r + 4 = 4.3 \approx 4$$


$r = 0.01$


$$3r + 4 = 4.03 \approx 4$$

$$I_C \approx \frac{6}{4} = 1.5A$$

$$I_A \approx \frac{18}{4} = 4.5A$$

$$I_B \approx \frac{12}{4} = 3A$$

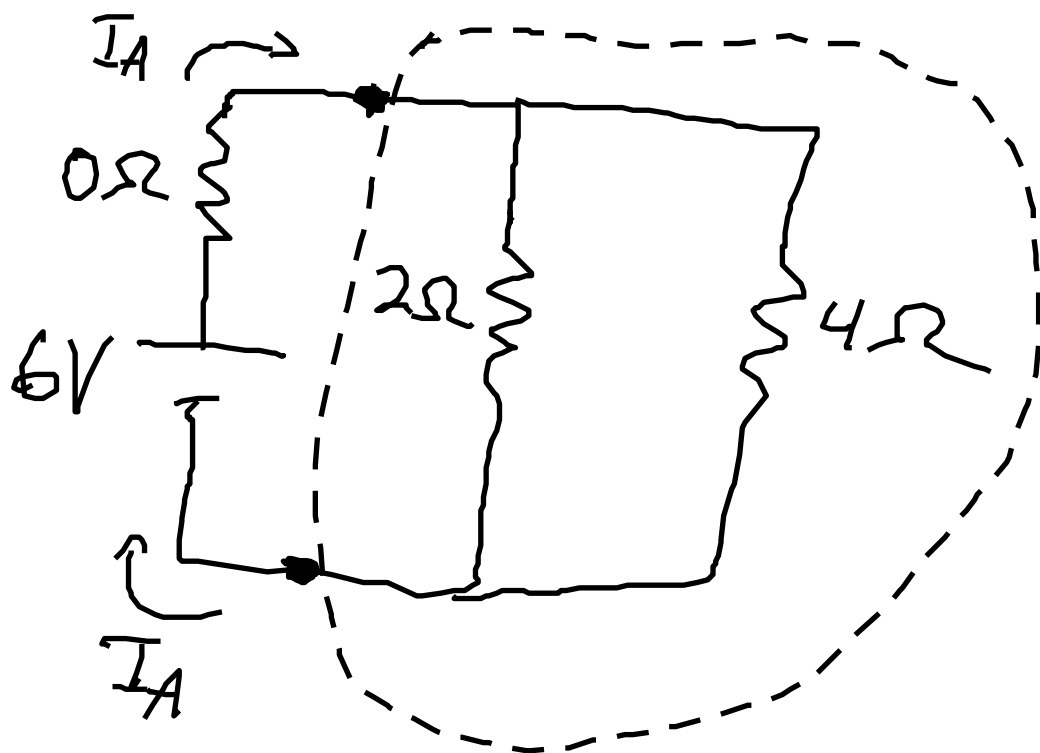

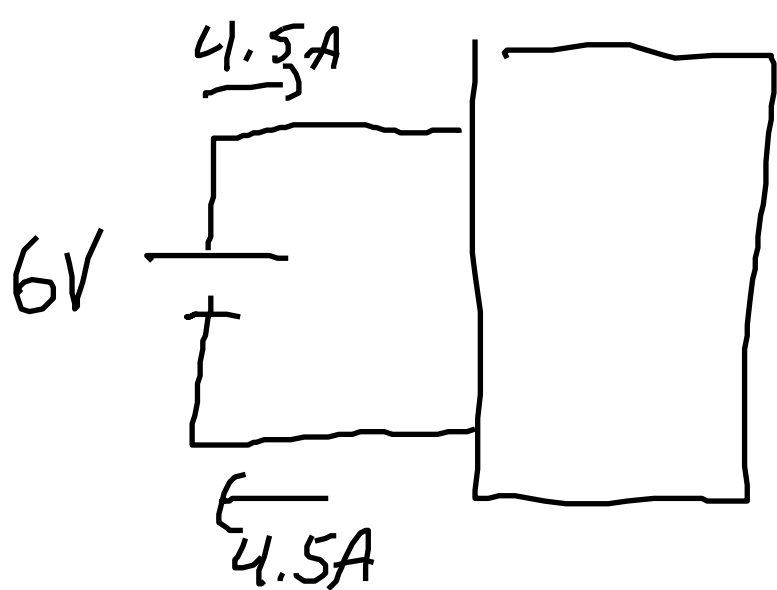

What is resistance of this box?

$$R = \frac{\Delta V}{I} = \frac{6V}{4.5A} = \frac{4}{3} \Omega$$

Combinations of resistors with two terminals have an equivalent resistance R_{eq}

$$R_{eq} = \frac{\Delta V_{\text{terminals}}}{I_{\text{into/out of system}}}$$

As far as the rest of circuit
is concerned, you can
replace comb of resistors
with its R_{eq} & nothing
changes

Resistors In Series




- experience the same current


series



not in series

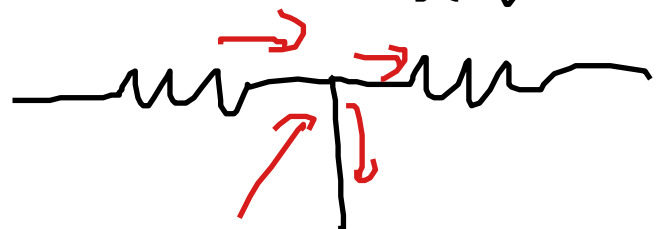


Junctions
break
"series"

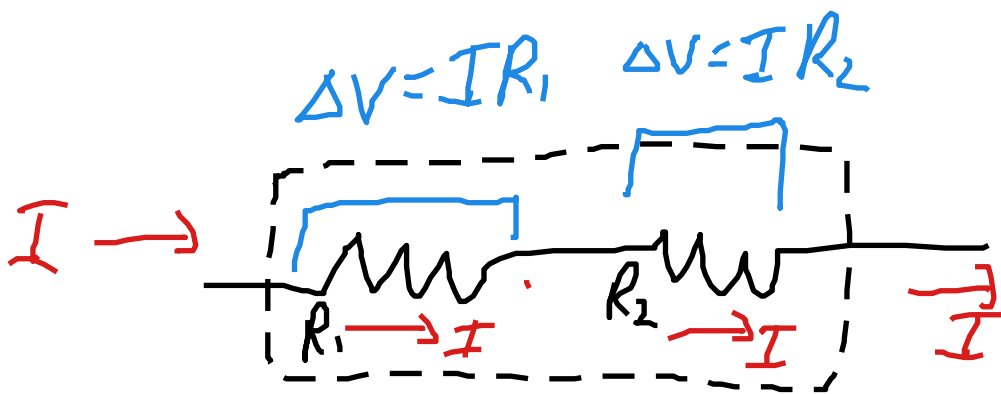


$$R_{eq} = \frac{\Delta V}{I} = \frac{IR_1 + IR_2}{I} = R_1 + R_2$$

Series: $R_{eq} = R_1 + R_2 + \dots$


Resistors in Parallel

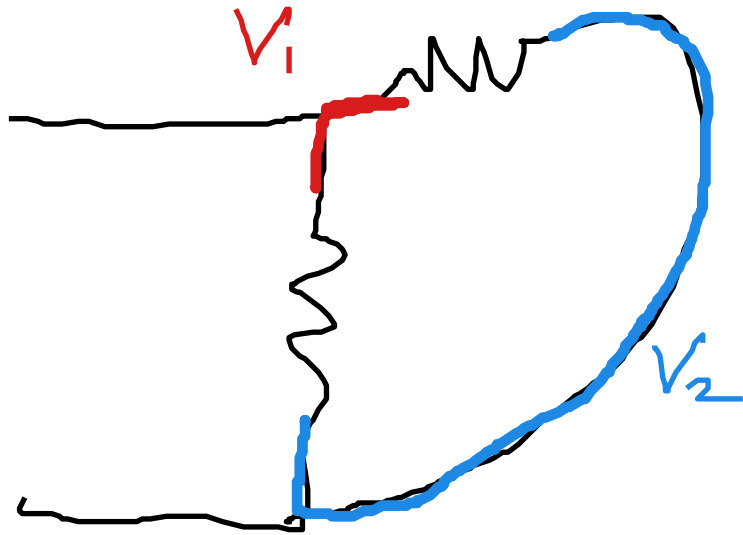

Both resistors have same ΔV .

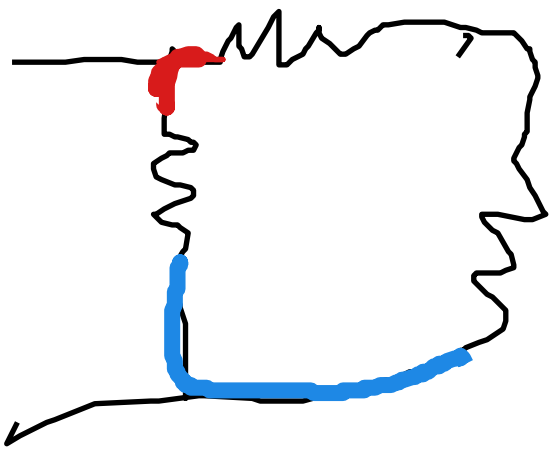

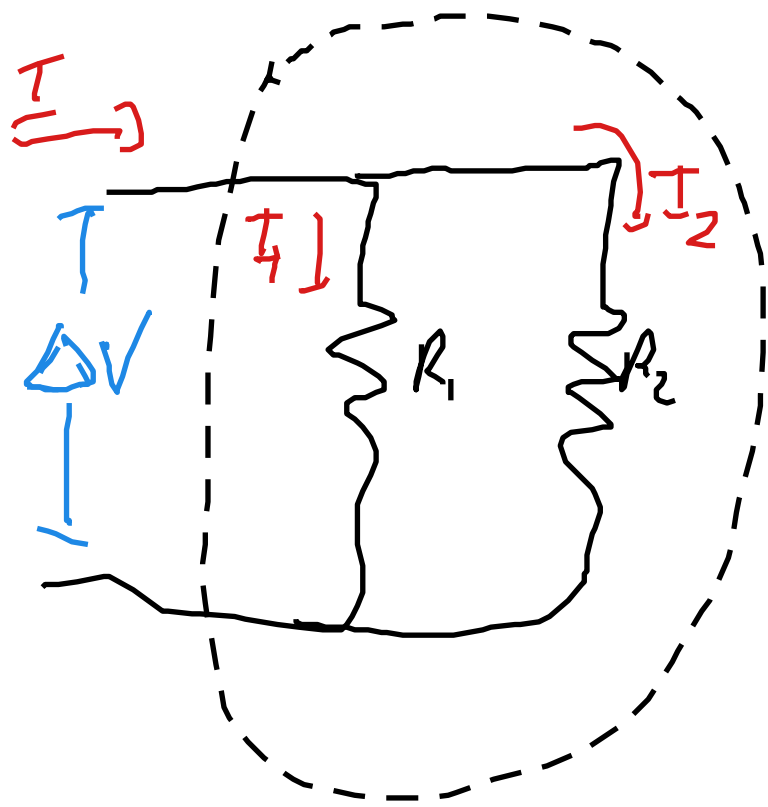Other
resistors &
batteries
block parallel



$$\Delta V = I_1 R_1 \rightarrow I_1 = \frac{\Delta V}{R_1}$$

$$\Delta V = I_2 R_2 \rightarrow I_2 = \frac{\Delta V}{R_2}$$

$$I = I_1 + I_2$$

$$I = \frac{\Delta V}{R_1} + \frac{\Delta V}{R_2} = \frac{\Delta V}{R_{eq}}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$$