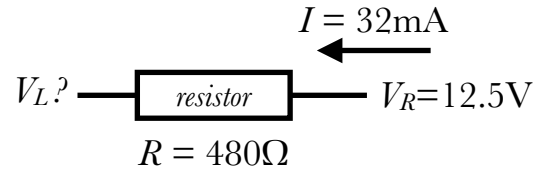


# Physics 102 Homework #8

*first draft due Wednesday, March 29th  
final draft due Sunday, April 2nd*

- 1a.** This resistor has a resistance of  $480\Omega$ , and  $32\text{mA}$  of current flows to the left into it. The right end of the resistor is at a potential of  $V_R = 12.5\text{V}$ . What is the potential difference  $\Delta V$  across the resistor?



The potential difference across a resistor is given by Ohm's Law:  
 $\Delta V = IR = (32\text{mA})(480) = \mathbf{15.4\text{V}}$ .

- 1b.** What is the potential  $V_L$  of the left end of the resistor?

The potential on the left side must be smaller than  $12.5\text{V}$  by that amount, or  $12.5\text{V} - 15.4\text{V} = \mathbf{-2.9\text{V}}$ .

- 1c.** What is the power output by the resistor?

The power output by a resistor can be calculated several ways, all giving the same answer:  
 $P = I^2R = (32 \times 10^{-3}\text{A})^2(480\Omega) = \mathbf{0.49\text{W}}$ .

$$P = I\Delta V = (32 \times 10^{-3}\text{A})(15.4\text{V}) = \mathbf{0.49\text{W}}$$

$$P = \frac{(\Delta V)^2}{R} = \frac{(15.4\text{V})^2}{480\Omega} = \mathbf{0.49\text{W}}$$


- 1d.** What is the current that flows out of the resistor?

The current that flows into the resistor is the same as the current that flows out of it:  $\mathbf{32\text{mA}}$ .

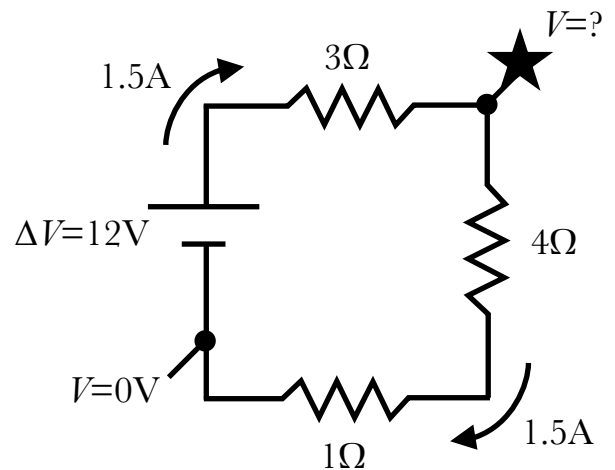- 2.** A 12V battery makes 1.5A of current through a 4Ω, 3Ω, and a 1Ω resistor.  
**a.** How much power does the battery supply?

The power supplied by a battery is  $P = I\Delta V$  where  $I=1.5\text{A}$  and  $\Delta V = 12\text{V}$ , the potential difference across the battery. Thus

$$P = (1.5\text{A})(12\text{V}) = \mathbf{18\text{W}}$$



- 2b.** How much power is dissipated by the 4Ω resistor?

The power output by a resistor is given by the formulas  $P = I\Delta V$ ,  $P = I^2R$ , or  $P = \frac{(\Delta V)^2}{R}$ . But we don't know the potential difference across the 4Ω resistor, but we do know the current. Thus we'll use the second equation:


$$P = I^2R = (1.5)^2(4) = \mathbf{9\text{W}}$$

- 2c.** If the potential at the negative end of the battery is 0V, what is the potential  $V$  at the star?

The potential at the top-left corner of the circuit is 12V higher than 0V, so 12V.

The potential drop across the 3Ω resistor is  $\Delta V = IR = (1.5)(3) = 4.5\text{V}$ . Thus the potential at the star is  $12\text{V} - 4.5\text{V} = \mathbf{7.5\text{V}}$ .

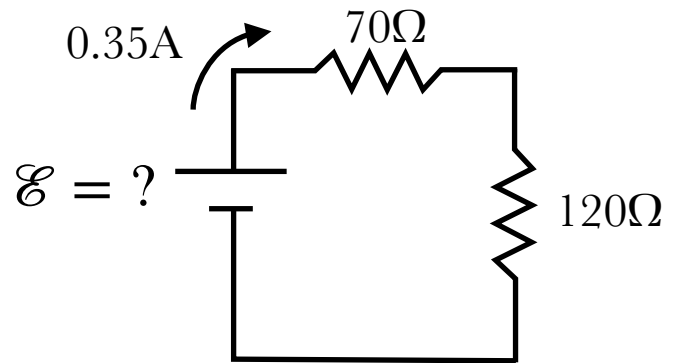3. A battery causes 0.35A of current to flow through two resistors,  $70\Omega$  and  $120\Omega$ . What is the emf of the battery?



The potential drop across the  $70\Omega$  resistor is  $\Delta V = (0.35\text{A})(70\Omega) = 24.5\text{V}$ , and the potential drop across the  $120\Omega$  resistor is  $\Delta V = (0.35\text{A})(120\Omega) = 42\text{V}$ . The total drop across both resistors is  $24.5 + 42 = \mathbf{66.5\text{V}}$ , and so this must be equal to the rise of the potential through the battery: in other words, its **emf**.