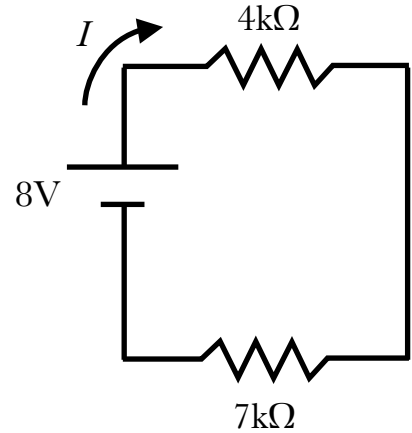


# Physics 102 Homework #9


first draft due Wednesday, April 12th  
final draft due Sunday, April 16th

1. Find the current in this circuit.



2. Consider this circuit.

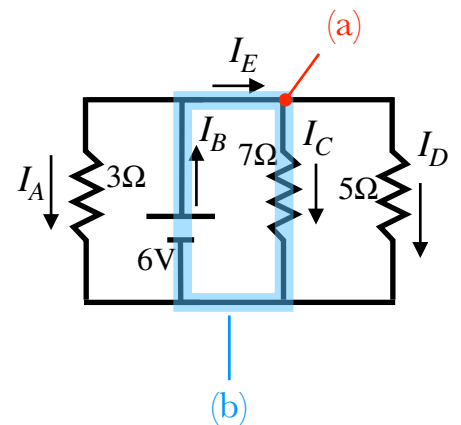
a) Write a junction rule equation for the junction marked (a).



b) Write a loop rule equation for the loop marked (b).

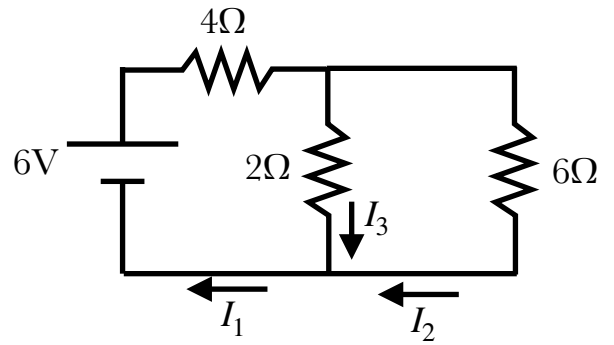c) Find the current  $I_A$ .

**3a.** Write a junction rule equation for this circuit.




**3b.** Write two loop rule equations for this circuit.

**3c.** Use your equations to solve for  $I_1$ ,  $I_2$ , and  $I_3$  in this circuit, and fill in the table.

$I_1$	
$I_2$	
$I_3$	

4. Real batteries have an internal resistance  $r$  in addition to its emf  $\mathcal{E}$ . Suppose we have a real battery with  $\mathcal{E} = 9\text{V}$  and an internal resistance  $r = 5\Omega$ .

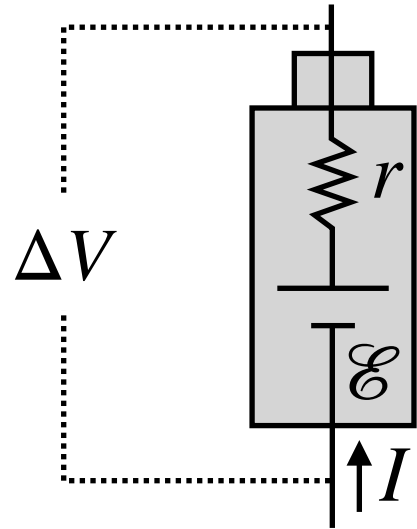
a. What is the potential difference  $\Delta V$  across the ends of this battery, as a function of the current  $I$  through it?



b. What is the maximum amount of current  $I_{\max}$  that can be produced by this battery?

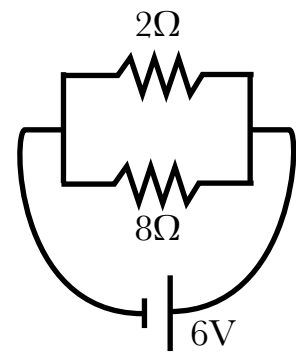c. The power output of the battery is  $P = I\Delta V$ . The maximum power output by the battery when  $I = \frac{1}{2}I_{\max}$ . Find the maximum power output of the battery.

**5a.** What is the equivalent resistance of these two resistors?



**5b.** Use the equivalent resistance to find the current through the 6V battery.

**6.** What is the equivalent resistance of this set of resistors?  
Use resistance reduction.

