

Physics 102 Homework #9

first draft due Wednesday, April 12th
final draft due Sunday, April 16th

1. Find the current in this circuit.

Starting from the negative end of the battery, we can build a loop equation:


$$+8 - 4kI - 7kI = 0$$

We solve that for I by first moving both I terms to the right side:

$$8 = 4kI + 7kI = 11kI$$

$$\Rightarrow I = \frac{8}{11k} = 7.2 \times 10^{-4} \Omega = \mathbf{0.72mA}.$$

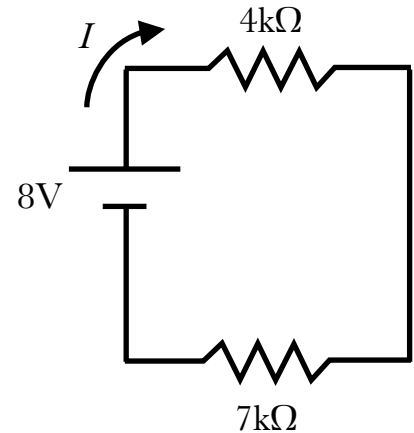
(Handy tip: when it comes to metric prefixes, $1/k = m$.)



2. Consider this circuit.

- a) Write a junction rule equation for the junction marked (a).

$$I_E = I_C + I_D$$

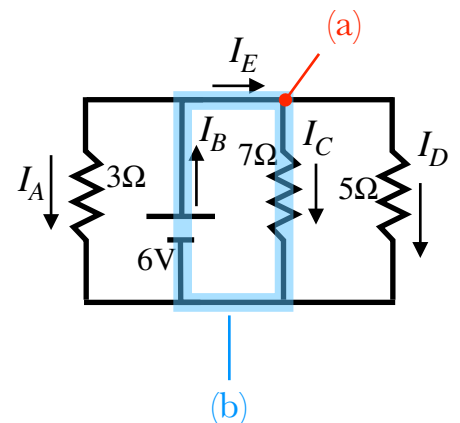

- b) Write a loop rule equation for the loop marked (b).

$$6 - 7I_C = 0$$


- c) Find the current I_A .

$$6 - 3I_A = 0 \Rightarrow I_A = 2A$$

3a. Write a junction rule equation for this circuit.

The junction on the bottom has currents I_2 and I_3 in and I_1 out. Thus

$$I_2 + I_3 = I_1.$$

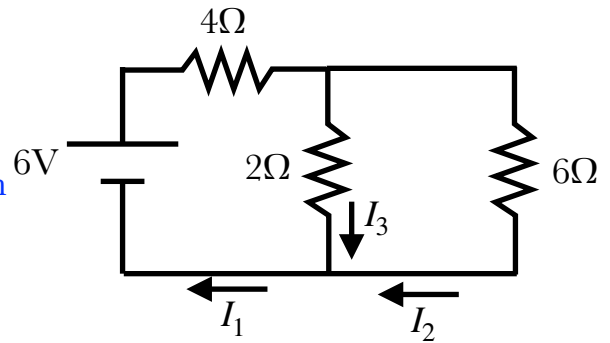

3b. Write two loop rule equations for this circuit.

There are three loop equations, but I only need two:

Left loop: $6 - 4I_1 - 2I_3 = 0$

Big loop: $6 - 4I_1 - 6I_2 = 0$

Right loop: $-2I_3 + 6I_2 = 0$

3c. Use your equations to solve for I_1 , I_2 , and I_3 in this circuit, and fill in the table.

I'm going to rewrite the other variables in terms of I_2 . To do that,

I use the right loop equation, solving it for I_3 to get $I_3 = 3I_2$.

Then I substitute that into the junction equation to get

$$I_1 = I_2 + 3I_2 \implies I_1 = 4I_2.$$

Now I can substitute these two results into the big loop equation to get a single equation in terms of I_2 , and then solve that:

$$6 - 4(4I_2) - 6I_2 = 0 \implies 6 = 22I_2 \implies I_2 = \mathbf{0.27A}.$$

Now I can substitute this into the other two equations I solved, giving me


$$I_3 = 3I_2 = \mathbf{0.81A} \quad \text{and} \quad I_1 = 4I_2 = \mathbf{1.08A}.$$

I_1	1.08A
I_2	0.27A
I_3	0.81A

4. Real batteries have an internal resistance r in addition to its emf \mathcal{E} . Suppose we have a real battery with $\mathcal{E} = 9\text{V}$ and an internal resistance $r = 5\Omega$.

a. What is the potential difference ΔV across the ends of this battery, as a function of the current I through it?

$$\Delta V = \mathcal{E} - Ir = 9 - 5I$$

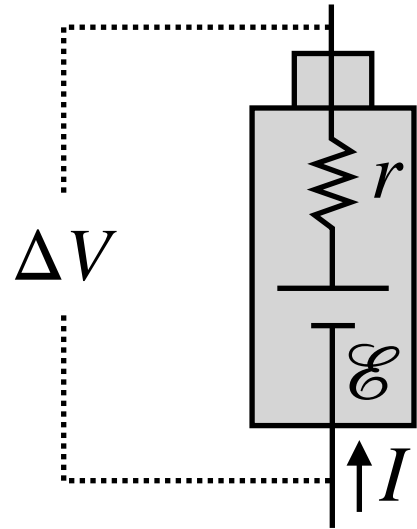

b. What is the maximum amount of current I_{\max} that can be produced by this battery?

The voltage ΔV across the battery has to be positive for any current to flow. Thus $\Delta V = \mathcal{E} - Ir \geq 0 \implies I \leq \frac{\mathcal{E}}{r} = \frac{9\text{V}}{5\Omega} = 1.8\text{A}$, which is I_{\max} .

c. The power output of the battery is $P = I\Delta V$. The maximum power output by the battery when $I = \frac{1}{2}I_{\max}$. Find the maximum power output of the battery.

The power output is $P = I\Delta V = I(\mathcal{E} - Ir) = \mathcal{E}I - I^2r$. If $I = \frac{1}{2}I_{\max} = \frac{\mathcal{E}}{2r}$,

then $P = \mathcal{E} \frac{\mathcal{E}}{2r} - \left(\frac{\mathcal{E}}{2r}\right)^2 r = \frac{\mathcal{E}^2}{2r} - \frac{\mathcal{E}^2}{4r} = \frac{\mathcal{E}^2}{4r}$. Or in our case,

$$P = \frac{9^2}{4(5)} = 4.05\text{W}.$$


5a. What is the equivalent resistance of these two resistors?

The equivalent conductance (reciprocal resistance) of this pair of parallel resistors is

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{2} + \frac{1}{8} = \frac{5}{8}$$

The equivalent resistance is found by flipping both sides upside-down:
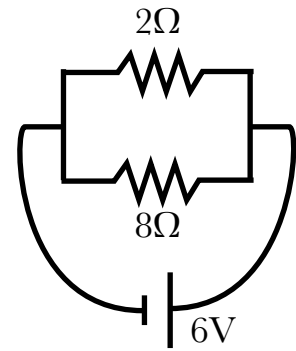
$$R_{eq} = \frac{8}{5} \Omega = \mathbf{1.6\Omega}.$$



5b. Use the equivalent resistance to find the current through the 6V battery.

The potential drop across the pair of resistors is $\Delta V = 6V$, and so the current that runs through both of them combined is $I = \frac{\Delta V}{R_{eq}} = \frac{6V}{1.6\Omega} = \mathbf{3.75A}$.

6. What is the equivalent resistance of this set of resistors?

Use resistance reduction.

There are no resistors in parallel (yet); however, the 2Ω and 6Ω resistor are in series. Thus we can replace them with a single resistor having the same equivalent resistance $R_{eq} = 2\Omega + 6\Omega = 8\Omega$. *I find it is handy to redraw the circuit with the replacement added.*

Now we have two resistors in parallel. Their effective conductance is

$$\frac{1}{R_{eq}} = \frac{1}{8\Omega} + \frac{1}{4\Omega} = \frac{3}{8}$$

and so

$$R_{eq} = \frac{8}{3} \Omega = \mathbf{2.67\Omega}.$$

