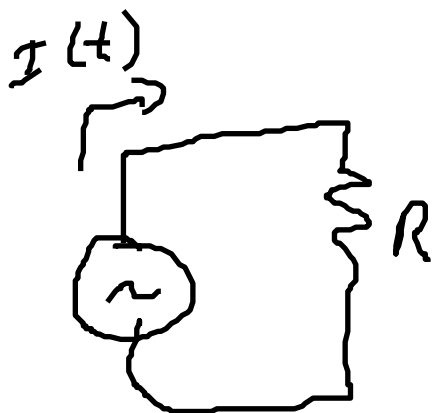


① $\mathcal{E}(t) = \mathcal{E}_0 \cos(\omega t)$





$$I(t) = I_0 \cos(\omega t + \phi)$$

(general)

$$I(t) = \frac{\mathcal{E}(t)}{R} = \frac{\mathcal{E}_0}{R} \cos(\omega t)$$

In Sync

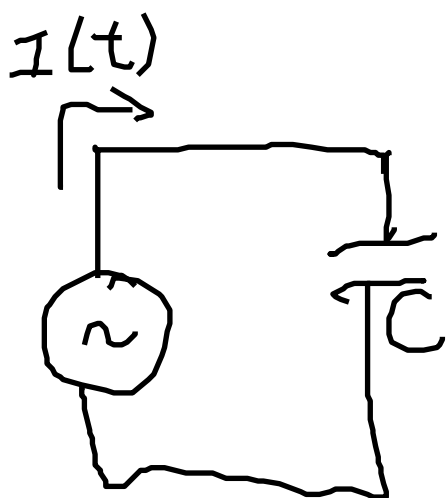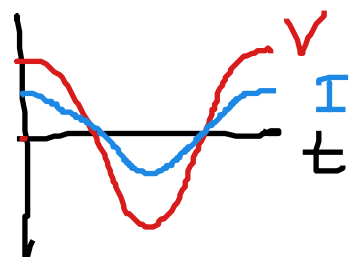

$$\Delta V = \frac{Q}{C}$$

$$Q = \int I dt$$


$$I(t) = -\omega C \mathcal{E}_0 \sin \omega t$$

$$I(t) = -\frac{\mathcal{E}_0}{X_C} \sin \omega t$$


X_C : reactance of capacitor

big X_C , small current

$$X_C = \frac{1}{\omega C}$$

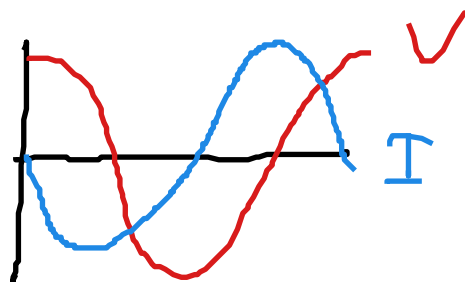


Current
leads
voltage

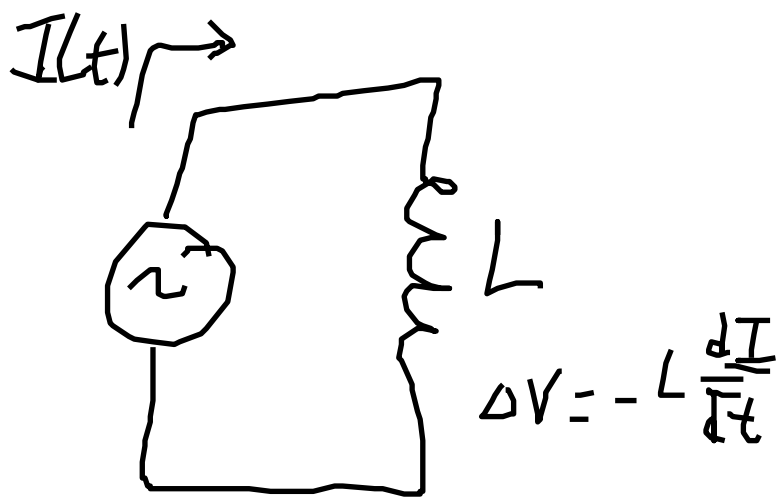


$$I(t) = \frac{\mathcal{E}_0}{\omega L} \sin \omega t$$

$$= \frac{\mathcal{E}_0}{X_L} \sin \omega t$$

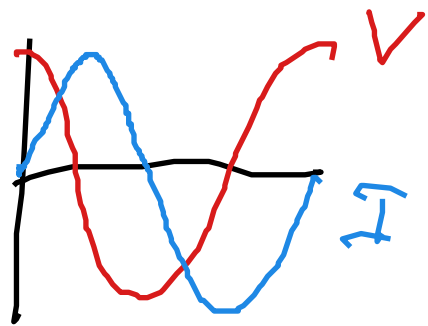$X_L = \omega L$: reactance of inductor
big X_L , small current



current lags voltage

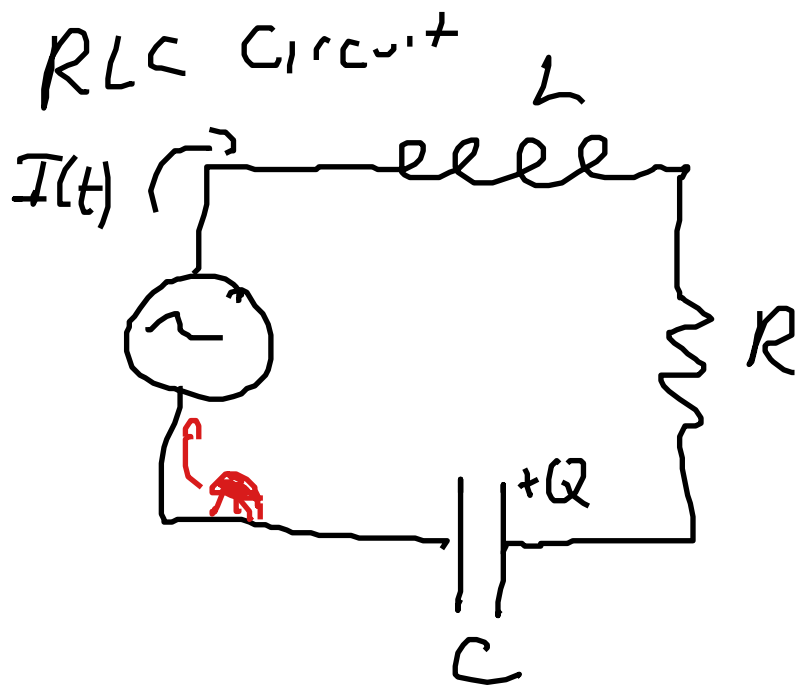

$$\mathcal{E}(t) = \mathcal{E}_0 \cos(\omega t - \phi)$$

$$I(t) = I_0 \cos(\omega t)$$

$$\frac{dI}{dt} = -I_0 \omega \sin \omega t$$

$$Q = \int I dt = \frac{I_0}{\omega} \sin(\omega t)$$

$$\mathcal{E}(t) - L \frac{dI}{dt} - IR - \frac{Q}{C} = 0$$

$$\mathcal{E}(t) = L \frac{dI}{dt} + IR + \frac{Q}{C}$$

$$\begin{aligned} \mathcal{E}_0 \cos(\omega t - \phi) = & -I_0 L \omega \sin \omega t \\ & + I_0 R \cos \omega t \\ & + \frac{I_0}{\omega C} \sin \omega t \end{aligned}$$

$$\begin{aligned} \frac{\mathcal{E}_0}{I_0} \cos(\omega t - \phi) = & R \cos \omega t + \left(\frac{1}{\omega C} - L\omega \right) \sin \omega t \\ = & R \cos \omega t + (X_C - X_L) \sin \omega t \end{aligned}$$

$$Z = \frac{E_0}{I_0}$$

impedance of circuit

$$I_0 = \frac{E_0}{Z}$$

big Z , small current

$$\cos(\omega t - \phi) = \cos \omega t \cos \phi + \sin \omega t \sin \phi$$

$$\begin{aligned} Z \cos \omega t \cos \phi &+ Z \sin \omega t \sin \phi \\ = R \cos \omega t &+ (X_C - X_L) \sin \omega t \end{aligned}$$

$$Z \cos \phi = R$$

$$Z \sin \phi = X_C - X_L$$

$$Z^2 \cos^2 \phi + Z^2 \sin^2 \phi = R^2 + (X_C - X_L)^2$$


$$Z^2 = R^2 + (X_C - X_L)^2$$

$$Z = \sqrt{R^2 + (X_C - X_L)^2}$$

$$\frac{Z \sin \phi}{Z \cos \phi} = \frac{X_C - X_L}{R}$$

$$\tan \phi = \frac{X_C - X_L}{R}$$

ϕ : how much
out of sync
is I from V

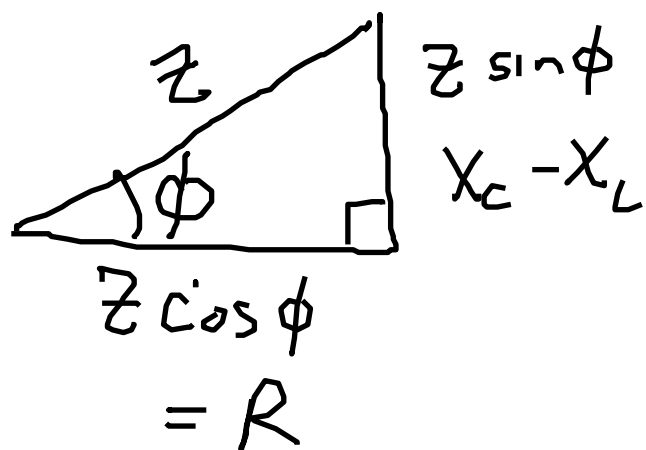

To maximize current, $I_0 = \frac{\mathcal{E}_0}{Z}$
 minimize impedance

$$Z = \sqrt{R^2 + (X_C - X_L)^2}$$


$$Z(\omega) = \sqrt{R^2 + \left(\frac{1}{\omega C} - \omega L\right)^2}$$

to minimize $Z(\omega)$

choose ω so $X_C = X_L$

$$\frac{1}{\omega C} = \omega L \rightarrow \omega^2 = \frac{1}{LC}$$
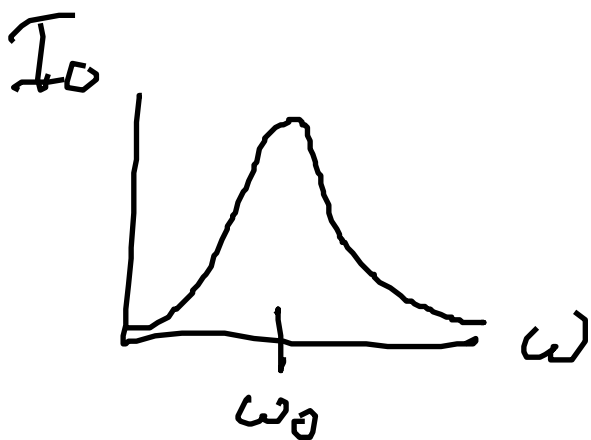
$$\rightarrow \boxed{\omega_0 = \frac{1}{\sqrt{LC}}}$$



resonant frequency

$$\phi = 0$$

current is in sync
with the voltage

7
Power output by resistor
in an RLC circuit

$$P(t) = I(t)^2 R$$

$$\langle P \rangle = \langle I^2 \rangle R$$

$$= \frac{1}{2} I_0^2 R$$

I_0 : max
current
or peak
current

$$P_{avg} = I_{rms}^2 R$$

$$I_{rms} = \sqrt{\langle I^2 \rangle}$$

$$= \sqrt{\frac{1}{2} I_0^2}$$

$$I_{rms} = \frac{1}{\sqrt{2}} I_0$$

$$\approx 0.7 I_0$$

$$Z = \frac{V_0}{I_0}$$

$$V_{rms} = \frac{1}{\sqrt{2}} V_0$$

$$Z = \frac{V_{rms}}{I_{rms}} \rightarrow I_{rms} = \frac{V_{rms}}{Z}$$

$$\langle P \rangle = I_{rms}^2 R$$

$$= I_{rms} I_{rms} R$$

$$= \frac{V_{rms}}{Z} I_{rms} R$$

$$= I_{rms} V_{rms} \frac{R}{Z}$$

$$= I_{rms} V_{rms} \cos \phi$$

average
power
out put
by
resistor

power
factor