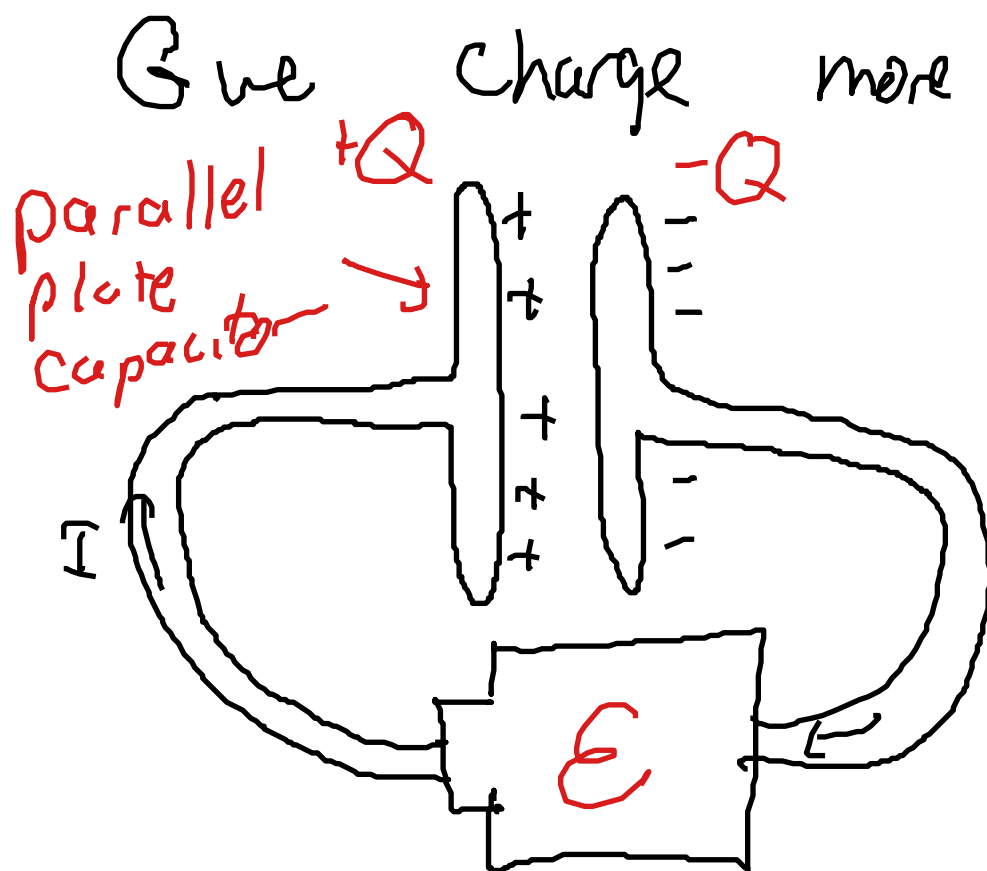


No steady current possible because of buildup of Charge.



Give Charge more space


takes longer for current to stop

Capacitor charges from the battery

unt. 1 $Q = CE$
then it stops

RC Circuits

- Discharge a capacitor

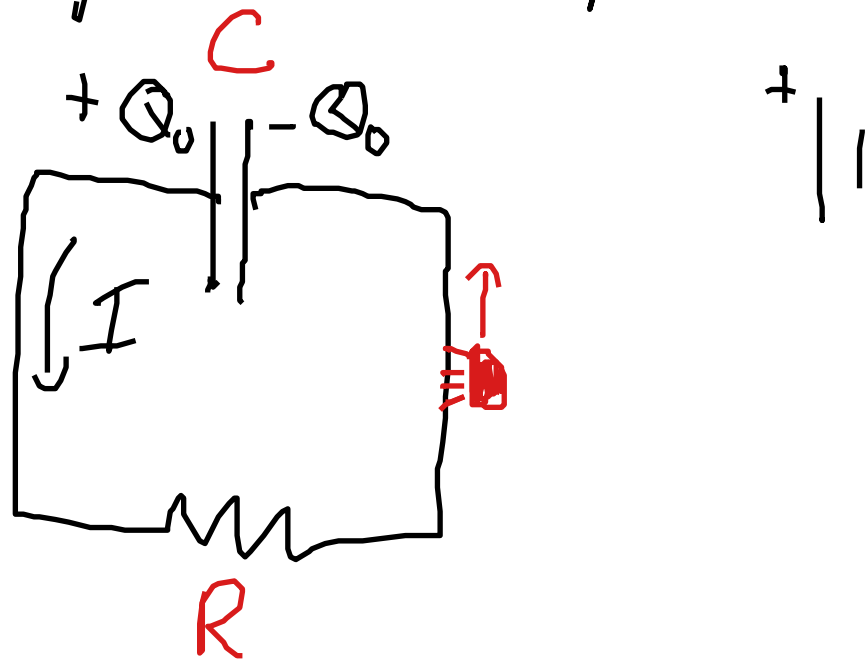

Let $Q(t)$ be the charge on positive plate.

$$+ \frac{\overbrace{Q(t)}^{\Delta V_C}}{C} - I(t)R = 0$$

$$\frac{dQ}{dt} = -I$$

$$\frac{Q(t)}{C} + \frac{dQ}{dt} R = 0$$

First-Order Differential Equation

$$\frac{dQ(t)}{dt} = -\frac{Q(t)}{RC}$$

$$Q(t) = A e^{-t/\tau}$$

τ :
time constant

A is arbitrary
constant

$$e^{x\tau}$$

x must
be dimensionless

$$\frac{dQ(t)}{dt} = A \left(-\frac{1}{\tau} e^{-t/\tau} \right)$$

$$\frac{dQ}{dt} = -\frac{Q}{RC}$$

$$-\frac{A}{\tau} \underbrace{e^{-t/\tau}} = -\frac{1}{RC} A \underbrace{e^{-t/\tau}}$$

$$\cancel{+\frac{A}{\tau}} = -\cancel{\frac{A}{RC}}$$

$$\boxed{\tau = RC}$$

$$R = \frac{\Delta V}{I}$$

$$C = \frac{Q}{\Delta V}$$

$$\text{Units: } \Omega F = \frac{\cancel{V}}{A} \frac{C}{\cancel{V}} = \frac{C}{C/s} = s$$

$$Q(t) = A e^{-t/RC}$$

Discharging a capacitor

Initial condition: $Q(t=0) = A e^0$

$$Q_0 = A$$

initial amount
of charge


Discharging a capacitor

$$Q(t) = Q_0 e^{-t/RC}$$

$$I(t) = -\frac{dQ}{dt} = -Q_0 \left[-\frac{1}{RC} e^{-t/RC} \right]$$


$$I(t) = \underbrace{\frac{Q_0}{RC}}_{I_0} e^{-t/RC}$$

I_0

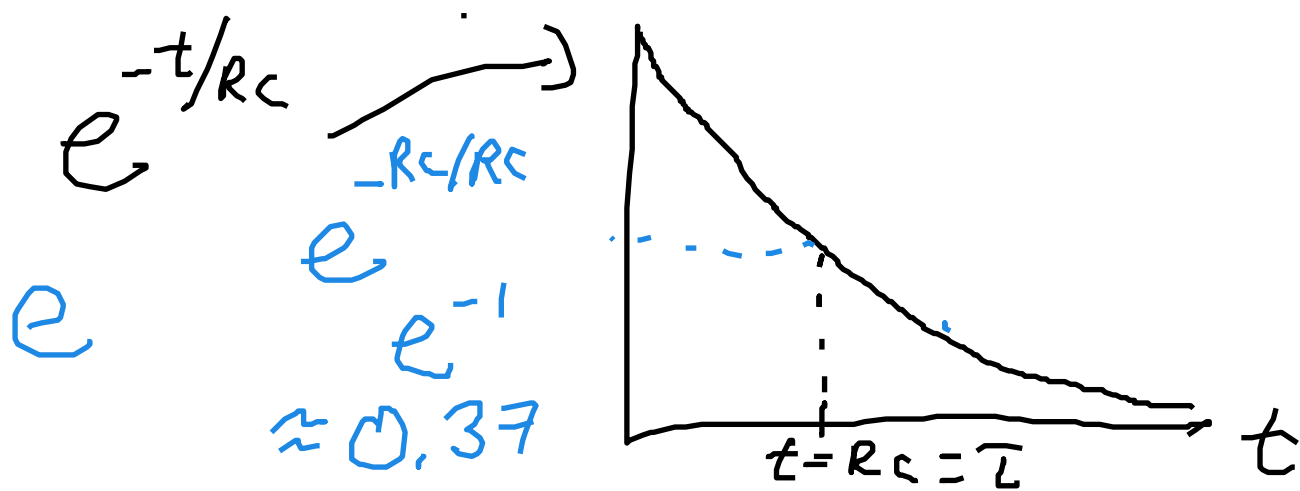

$$t = 0 \quad e^{-t/R_C} = 1$$
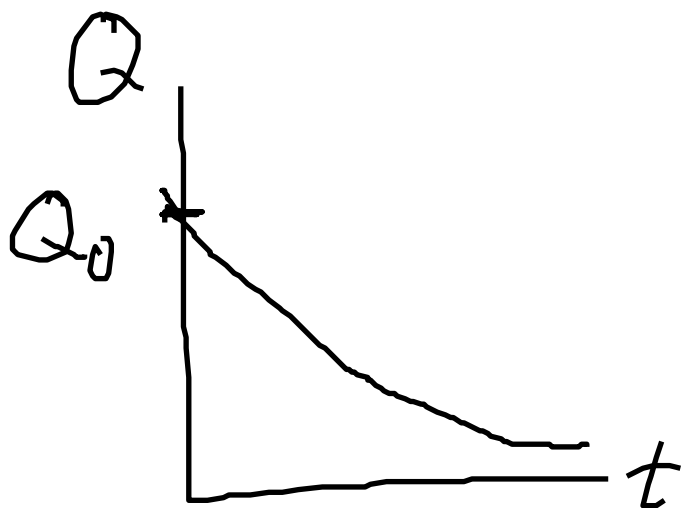
$$t \rightarrow \infty: e^{-t/R_C} \rightarrow 0$$



$$t = 0: Q = Q_0$$


$$I = \frac{Q_0}{R_C}$$

$$t \rightarrow \infty: Q = 0$$

$$I = 0$$

7
 τ is Time for $e^{-t/\tau}$ to
reach $37\% = \frac{1}{e}$

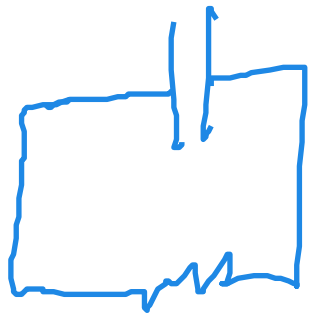
Gives a sense of "how long"
it takes to decay



$$\tau = RC$$

Big C : big τ , holds lots of
Charge, less pressure
to discharge,
takes longer

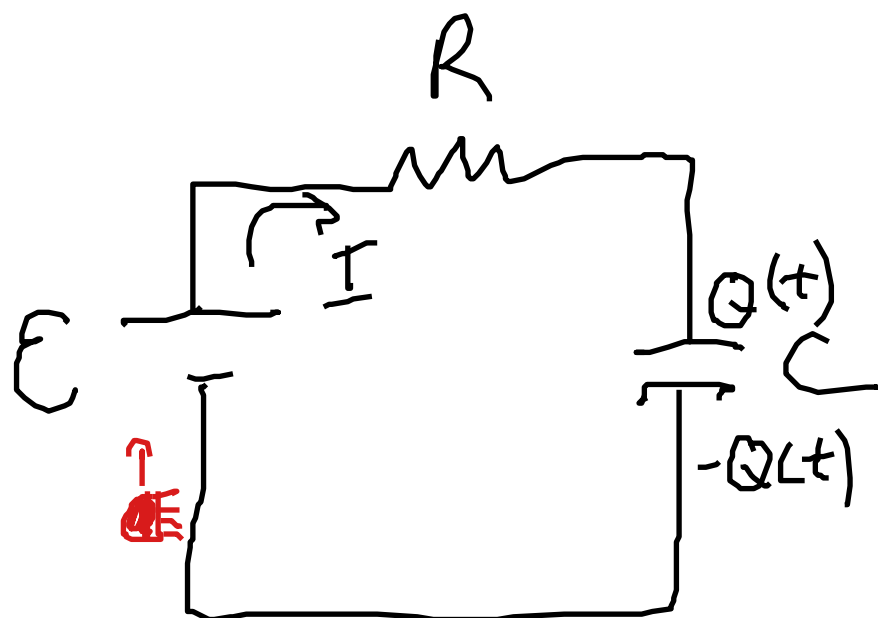Big R : big τ . Current is restricted
so takes longer
to discharge



↓ down the capacitor
from + to -

$$+E - IR - \frac{Q}{C} = 0$$

$$I = \frac{E}{R} - \frac{Q}{RC}$$

$$\frac{dQ}{dt} = +I$$

$$\frac{dQ}{dt} = \frac{E}{R} - \frac{Q}{RC}$$

$$Q(t) = A(1 - e^{-t/\tau})$$

$$= A - Ae^{-t/\tau}$$

$$\frac{dQ}{dt} = -A \left(-\frac{1}{\tau} e^{-t/\tau} \right)$$

$$= \frac{A}{\tau} e^{-t/\tau} = I$$

$$\frac{dQ}{dt} = \frac{\mathcal{E}}{R} - \frac{Q}{RC}$$

$$\frac{A}{\tau} e^{-t/\tau} = \frac{\mathcal{E}}{R} - \frac{1}{RC} A [1 - e^{-t/\tau}]$$

Get all "t" stuff to one side

$$\underbrace{\left[\frac{A}{\tau} - \frac{A}{RC} \right]}_{\circ} e^{-t/\tau} = \underbrace{\left[\frac{\mathcal{E}}{R} - \frac{A}{RC} \right]}_{\circ}$$

can only be true for all time

if $\circ = \circ$

$$\frac{A}{\tau} - \frac{A}{RC} = 0 \rightarrow \tau = RC$$

$$\frac{\cancel{E}}{\cancel{R}} - \frac{A}{\cancel{RC}} = 0 \rightarrow A = CE$$

Charging a capacitor

$$Q(t) = CE(1 - e^{-t/RC})$$


$$I(t) = \frac{\cancel{CE}}{\cancel{RC}} e^{-t/RC}$$

$$= \frac{E}{R} e^{-t/RC}$$

$$t=0: Q(0) = CE(1-1) = 0$$

$$I(0) = \frac{E}{R}(1) = E/R$$

empty capacitor
acts like a wire

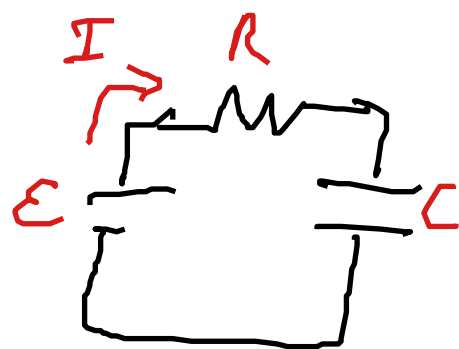

$$t = \infty: Q(\infty) = C\mathcal{E}(1-0) = C\mathcal{E}$$

$$I(\infty) = \frac{\mathcal{E}}{R}(0) = 0$$

full capacitor acts like a break
in wire

$$Q = C\mathcal{E} = C\Delta V$$

what we
would've said before