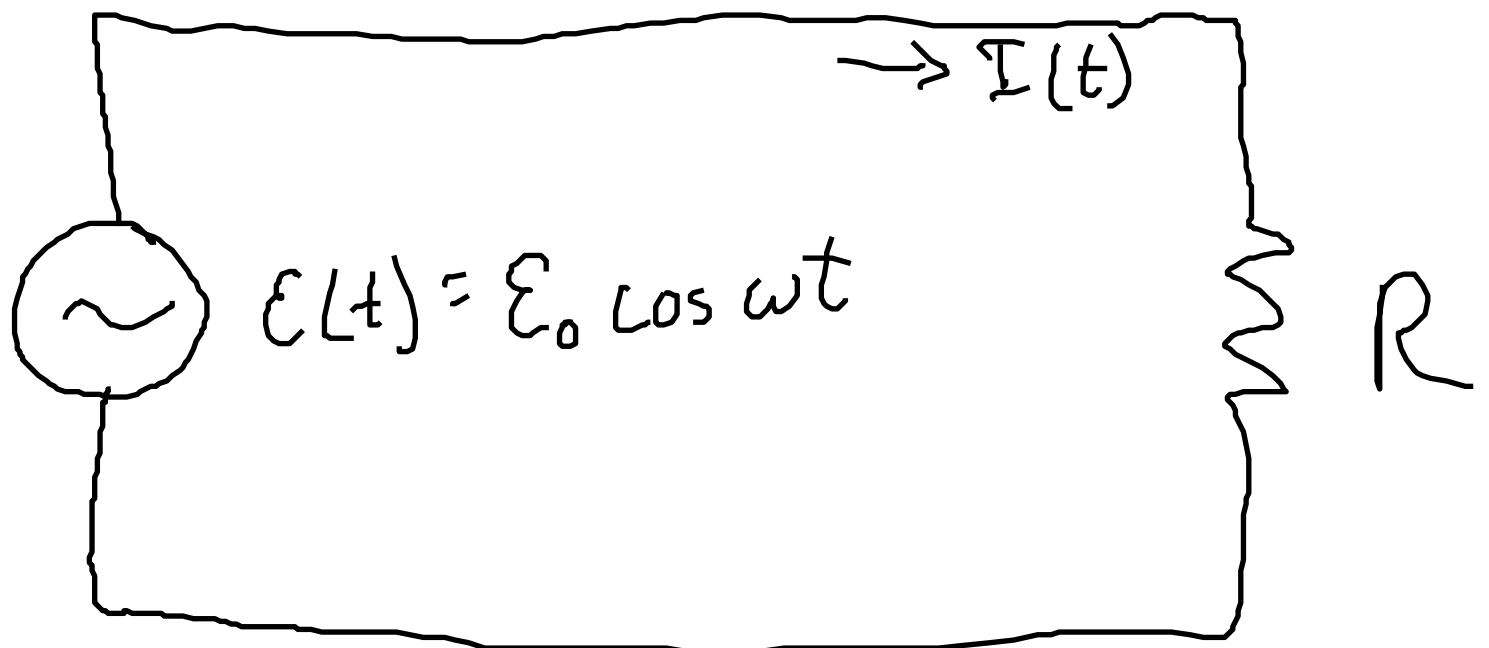



Driven AC Circuits




$$\Delta V = IR$$

$$I = \frac{\Delta V}{R}$$
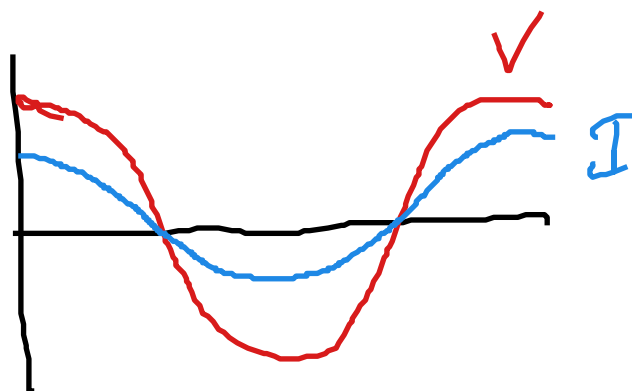
$$I(t) = \frac{\mathcal{E}_0}{R} \cos \omega t$$



in phase

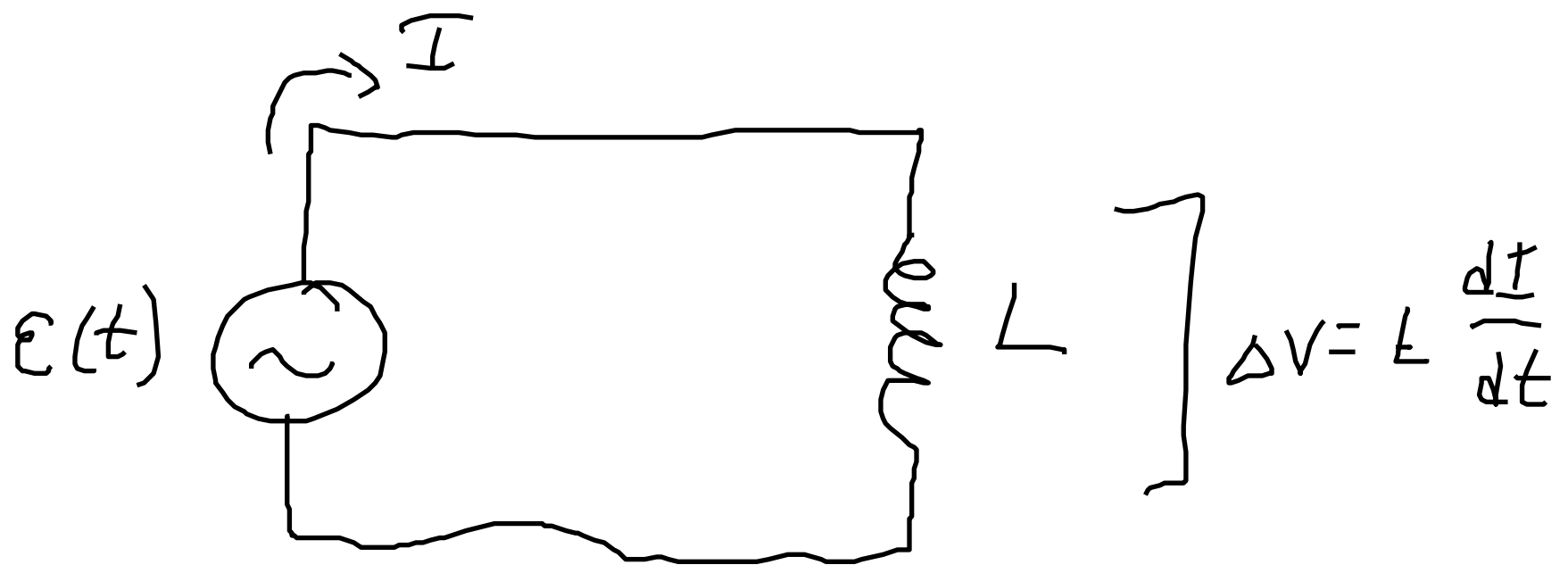

$$\int E_0 \cos \omega t = L \frac{dI}{dt} \times dt$$

$$\int E_0 \cos \omega t \, dt = \int L \, dI$$

$$E_0 \frac{1}{\omega} \sin \omega t = L I$$

$$\frac{E_0}{L\omega} \sin \omega t = I(t)$$


reactance of inductor

$$X_L = L\omega \quad \text{in ohms}$$


Big X_L , small current

high frequency ω , big X_L ,
small current

(L fights harder
against quick changes)

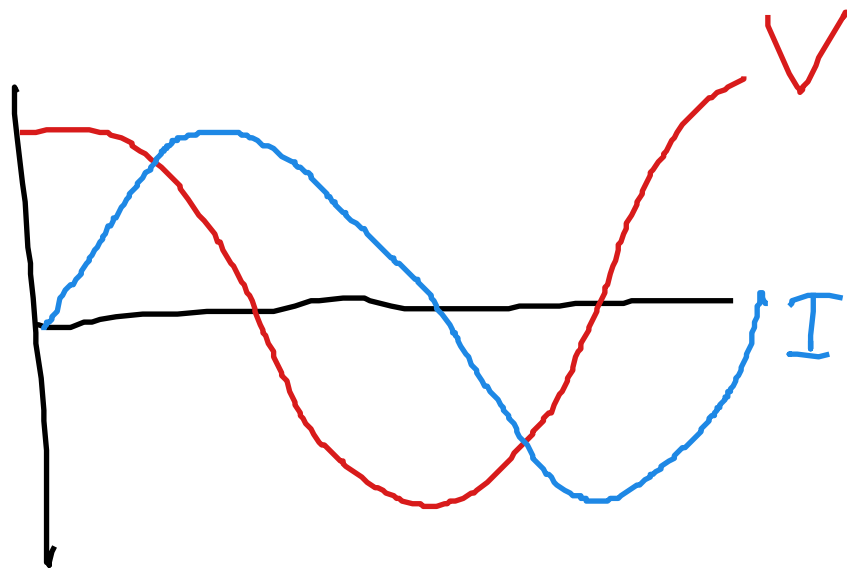

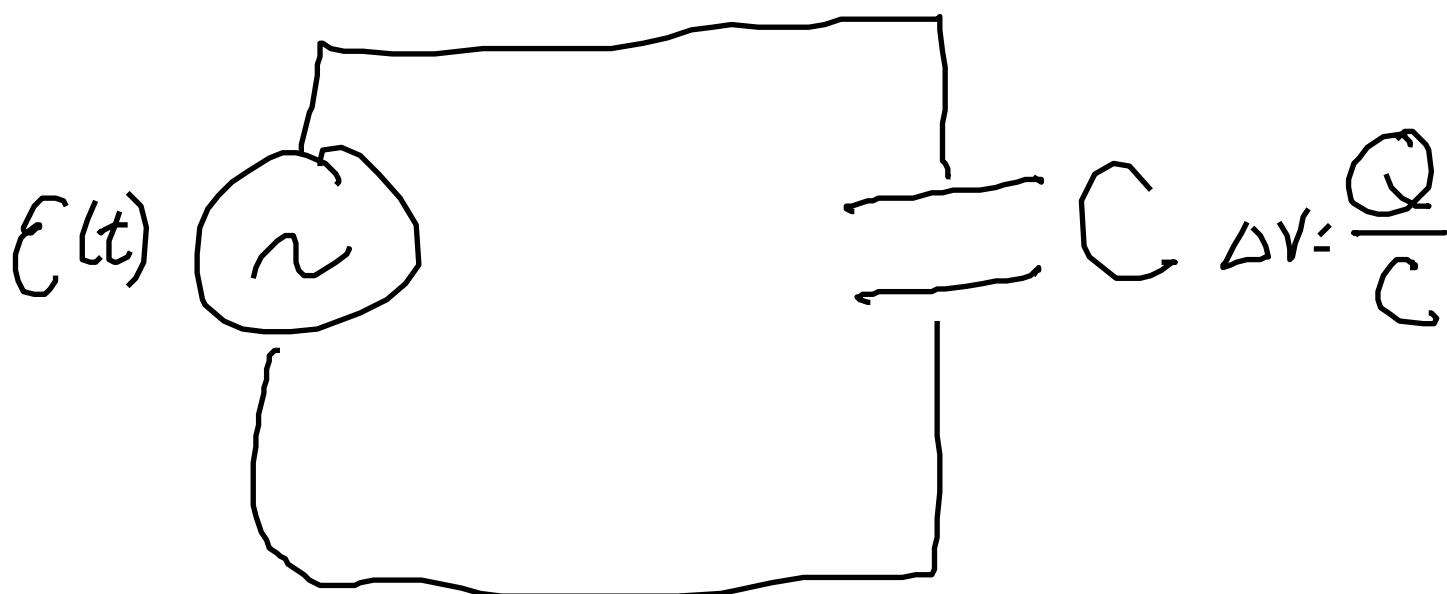current lags the voltage
out of phase by $\frac{\pi}{2}$



$$E_0 \cos \omega t = \frac{Q}{C}$$

$$Q = C E_0 \cos \omega t$$

ignore right now

$$I(t) = \frac{dQ}{dt} = -C\omega E_0 \sin \omega t$$

reactance of capacitor

$$X_C = \frac{1}{C\omega}$$

$$I(t) = \frac{E_0}{X_C} \sin \omega t$$

↑
high ω , low reactance

capacitor
doesn't fill up