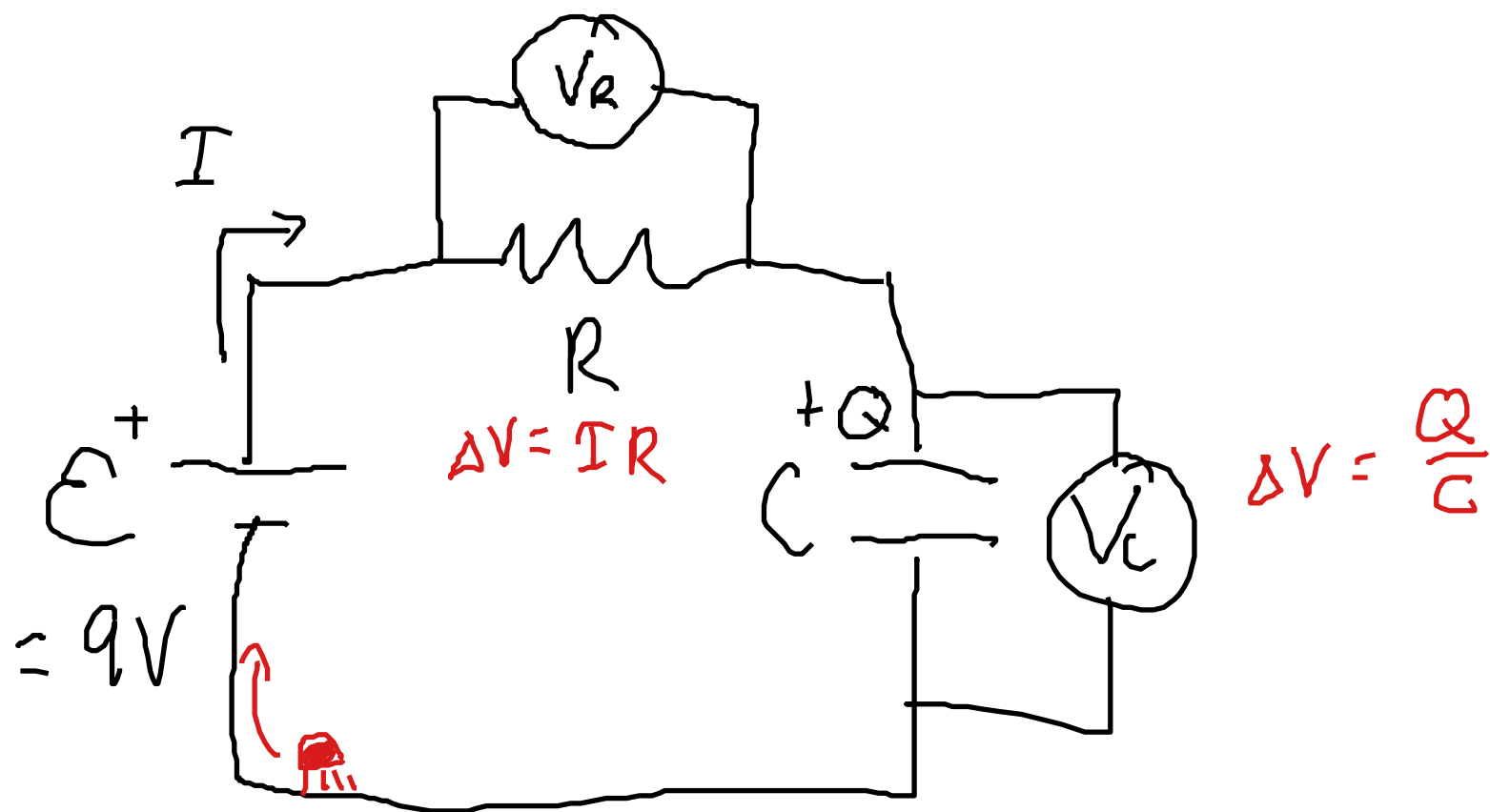


RC Circuits



At time $t=0$,
Capacitor is empty. $Q=0$

there's a current
 $\Delta V_R \neq 0$

cap is empty
 $\Delta V_C = 0$

$$\Delta V_R = 9V = E$$

$$+9 - \Delta V_R + 0 = 0$$

/

At time $t = \infty$,


trickles to a
↓ stop

$$\Delta V_R = IR = 0 \quad \Delta V_C = \frac{Q}{C} \neq 0$$

$$\Delta V_C = 9V$$

Inductor


(Solenoid)

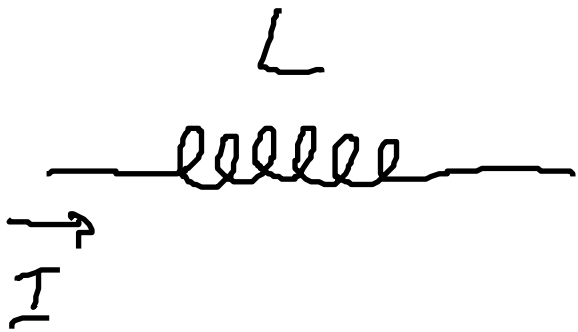

If I is steady, inductor is just a wire

If I is increasing

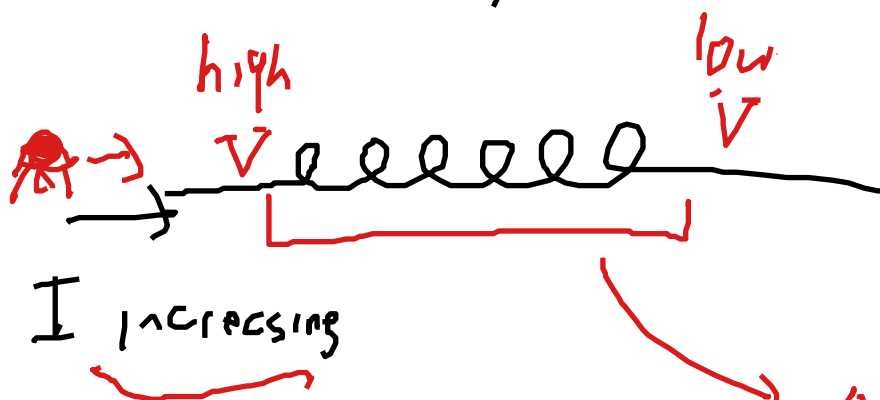
inductor tries to create an induced current in the opposite direction to fight it : acts like a resistor



$$\Delta V < 0$$


like a resistor

$$\Delta V = -L \frac{dI}{dt}$$

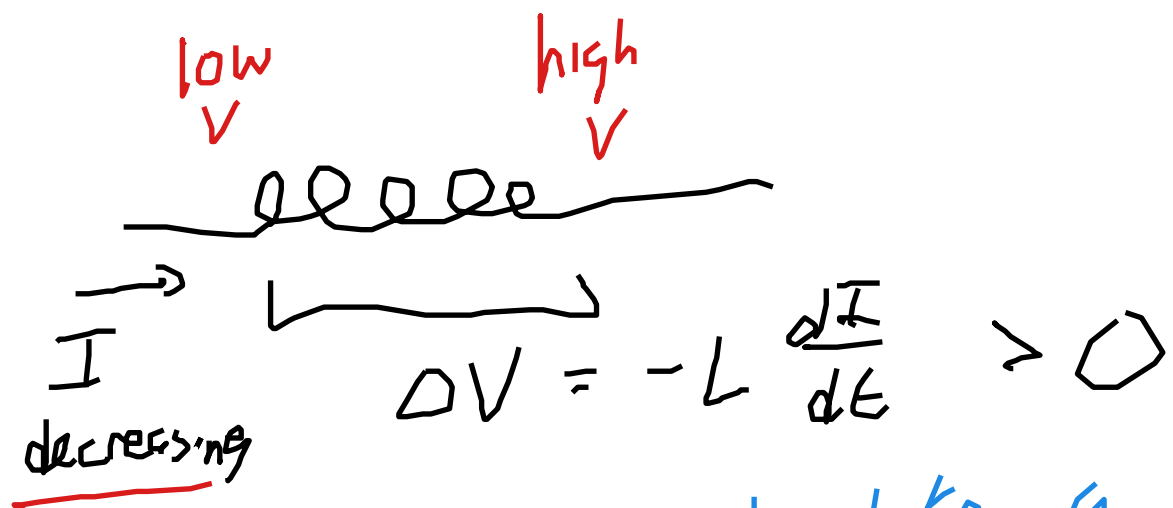

$$\frac{dI}{dt} < 0$$

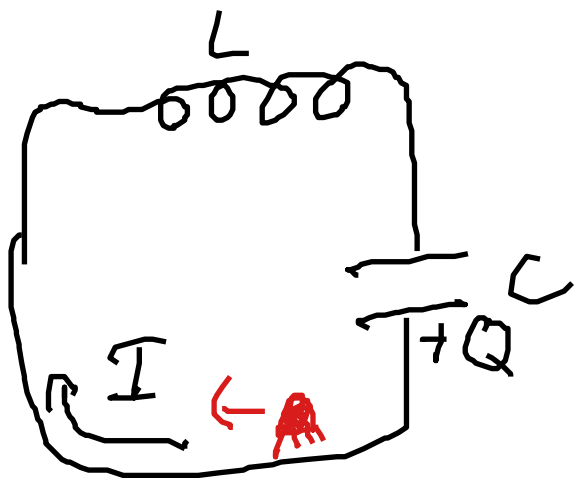act like a battery
giving the current
a boost



LC Circuit

C starts filled

$$-L \frac{dI}{dt} + \frac{Q}{C} = 0$$

$$\frac{Q(t)}{C} = L \frac{dI(t)}{dt}$$

$$I = -\frac{dQ}{dt}$$

$$= L \frac{d}{dt} \left(-\frac{dQ}{dt} \right)$$

$$\frac{Q(t)}{C} = -L \frac{d^2 Q(t)}{dt^2}$$

second-order differential equation

- two arbitrary constants

- If you can guess a solution
you're right

$$\frac{d^2 Q}{dt^2} = -\frac{1}{LC} Q(t)$$

← arbitrary →

$$Q(t) = A \cos(\omega t) + B \sin(\omega t)$$

OR (better)

must be solved for

$$Q(t) = \underbrace{A}_{\text{arbitrary}} \cos(\omega t + \underbrace{\phi_0}_{\text{arbitrary}})$$

$$\frac{dQ}{dt} = -A\omega \sin(\omega t + \phi_0)$$

$$\frac{d^2Q}{dt^2} = -A\omega^2 \cos(\omega t + \phi_0)$$

$$\underbrace{-A\omega^2 \cos(\omega t + \phi_0)} = -\underbrace{\frac{1}{LC}} A \cos(\omega t + \phi_0)$$

$$+ \cancel{A}\omega^2 = + \frac{1}{LC} \cancel{A}$$

$$\omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$Q(t) = A \cos\left(\frac{t}{\sqrt{LC}} + \phi_0\right)$$


$\phi_0 = 0$ for moment

angular frequency $\omega = 2\pi f$
 frequency f

$$Q_0 = A$$

$$I_{\max} =$$

$$\frac{Q_0}{\sqrt{LC}}$$

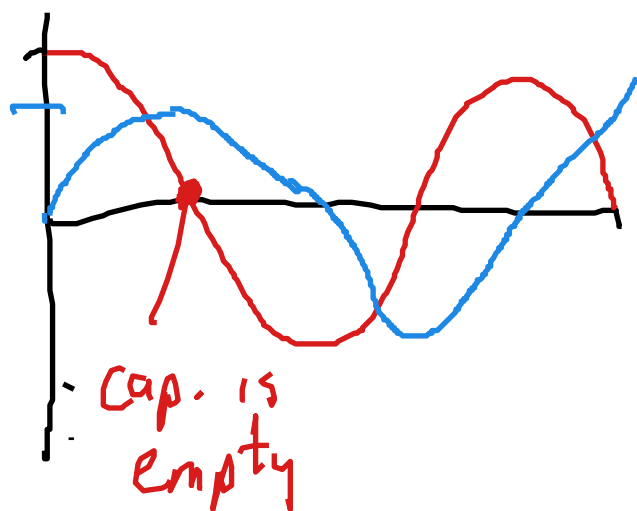

of oscillations per second

$$I(t) = - \frac{dQ}{dt}$$

$$= Q_0 \omega \sin(\omega t + \phi_0)$$

When Q is maximum, $I = 0$

When $Q = 0$, current "should" stop
 but inductor won't let it

current keeps flowing & capacitor
 charges in opposite direction

$$\omega = \frac{1}{\sqrt{LC}} = 2\pi f$$

frequency
of
oscillation

$$f = \frac{1}{2\pi\sqrt{LC}}$$

Big C: small frequency
(takes time to discharge)

Big L: small frequency
inductor restricts current
& keeps it going


$$L \frac{d^2 Q}{dt^2} + \frac{1}{C} Q = 0$$

analogy with $Q \leftrightarrow x$
position

$$L \frac{d^2 x}{dt^2} + \frac{1}{C} x = 0$$

force that depends on x

$$ma = -kx$$

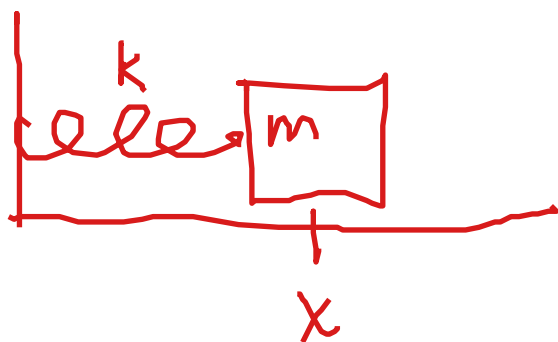

$$Q \leftrightarrow x$$

$$I = \frac{dQ}{dt} \leftrightarrow v$$

velocity

L acts like m : inertia
 $\frac{1}{C}$ acts like k

$$\frac{d^2 Q}{dt^2} \leftrightarrow a$$