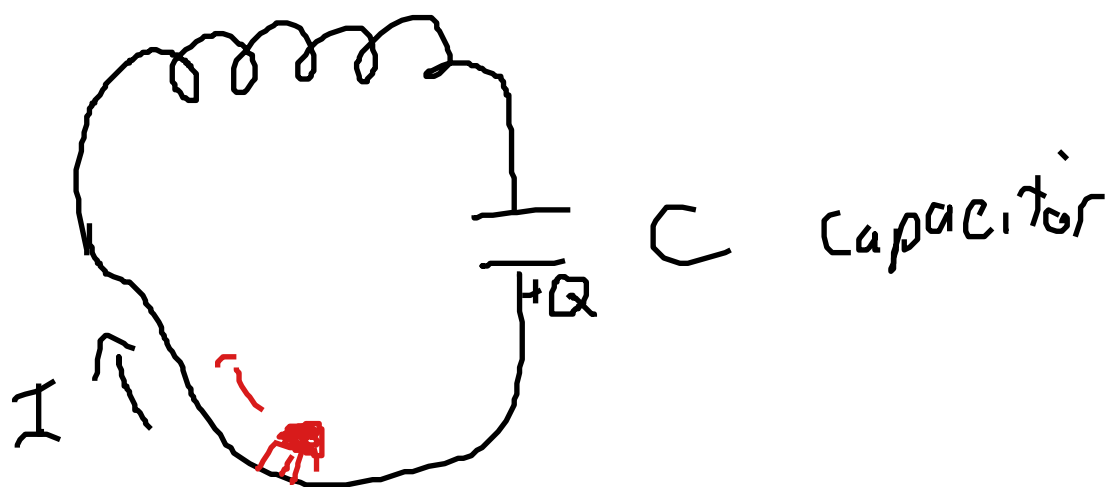


inductor
 L




$$I = - \frac{dQ}{dt}$$

As $^+$ current
flows,
 Q decreases

$$-L \frac{dI}{dt} + \frac{Q}{C} = 0$$

$$Q(t) = Q_0 \cos\left(\frac{1}{\sqrt{LC}} t + \phi_0\right)$$

$$I(t) = - \frac{dQ}{dt} = \frac{Q_0}{\sqrt{LC}} \sin\left(\frac{1}{\sqrt{LC}} t + \phi_0\right)$$

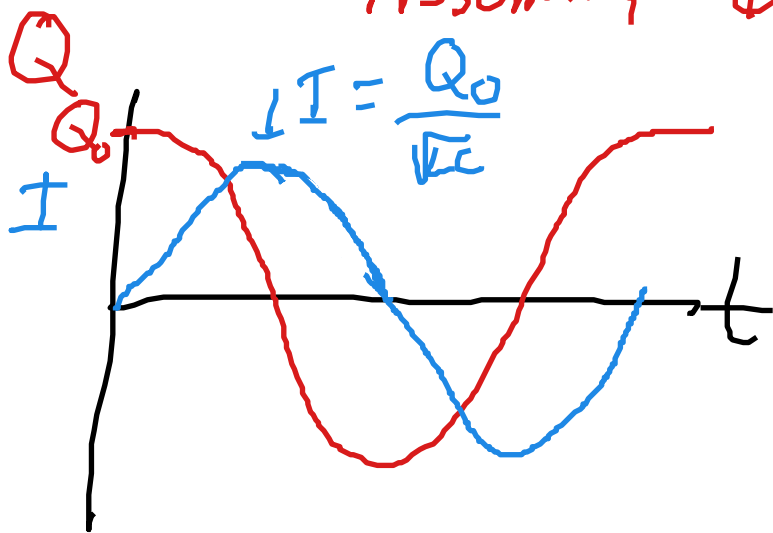Assuming $\phi_0 = 0$ 


$$\omega = \frac{1}{\sqrt{LC}}$$

$$f = \frac{\omega}{2\pi} = \frac{1}{2\pi\sqrt{LC}}$$

Q & I are out-of-phase with each other by $\pi/2$.

$$L \frac{d^2 Q}{dt^2} + \frac{Q}{C} = 0$$

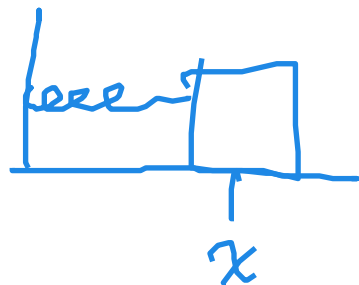
$$m \frac{d^2 x}{dt^2} + kx = 0 \rightarrow ma = -kx$$



$$E_c = \frac{1}{2} \frac{Q^2}{C}$$

energy in a capacitor

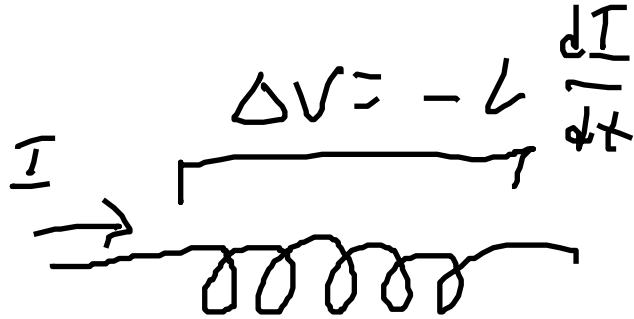Where does the energy go
when capacitor is empty?
into the inductor.



$$P = I \Delta V$$

$$dt \times P = -L I \frac{dI}{dt} \times dt$$

$$\int P dt = -L \int I dI$$

$$\int \frac{dE}{dt} dt = -L \left(\frac{1}{2} I^2 \right) \leftarrow \begin{array}{l} - : \\ \text{energy} \\ \text{stolen from} \\ \text{current} \end{array}$$

$$E_L = \frac{1}{2} L I^2$$

$\leftarrow$ + :
energy stored
in inductor

$$E_{\text{tot}} = \frac{1}{2} \frac{Q^2}{C} + \frac{1}{2} L I^2$$

$Q_0 < 0$

$\omega = \frac{1}{\sqrt{LC}}$

$$= \frac{1}{2C} \left[Q_0 \cos(\omega t) \right]^2 + \frac{1}{2} L \left[Q_0 \omega \sin(\omega t) \right]^2$$


$$\frac{1}{2C} Q_0^2 \cos^2 \omega t + \frac{1}{2} L Q_0^2 \omega^2 \sin^2(\omega t)$$

$\uparrow$
 $\frac{1}{LC}$

$$= \frac{1}{2C} Q_0^2 \cos^2 \omega t + \frac{1}{2C} Q_0^2 \sin^2(\omega t)$$

$$= \frac{Q_0^2}{2C} \left[\cos^2 \omega t + \sin^2 \omega t \right]$$
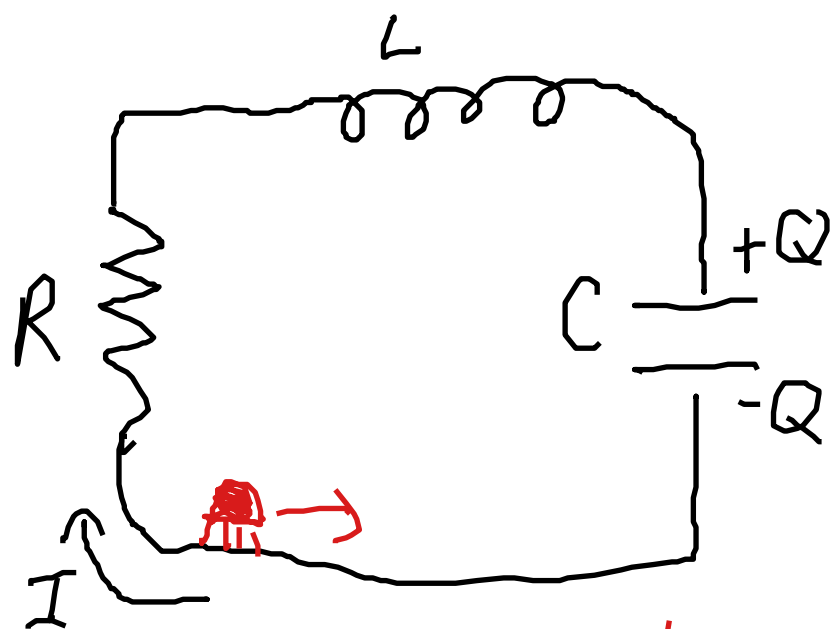
$$E_{\text{tot}} = \frac{Q_0^2}{2C} [1] \quad \text{constant}$$



different!

$$I = + \frac{dQ}{dt}$$

upstream
in inductor

$$+ \frac{Q}{C} + L \frac{dI}{dt} + IR = 0$$

$$\frac{1}{C} Q(t) + L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} = 0$$

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q(t) = 0$$

$$ma + \underbrace{L \frac{dI}{dt}}_{\text{air resistance (or frictionish)}} + \underbrace{kx}_{\text{spring force}}$$

$$\hat{Q} = Q_0 e^{-t/\tau} \cos(\omega t)$$

$$\underbrace{\left[\frac{1}{LC} - \frac{R}{L\tau} + \frac{1}{\tau^2} - \omega^2 \right]}_{=0} \cos \omega t + \underbrace{\left[2\frac{\omega}{\tau} - \frac{R\omega}{L} \right]}_{=0} \sin \omega t = 0$$

$$\downarrow \quad \frac{2\omega}{\tau} - \frac{R}{L}\omega = 0$$

$$\frac{2}{\tau} = \frac{R}{L} \rightarrow \tau = \frac{2L}{R}$$

big τ
slow decay

$$\frac{1}{LC} - \frac{R}{L\tau} + \frac{1}{\tau^2} - \omega^2 = 0$$


$$\frac{1}{LC} - \frac{R}{L} \frac{R}{2L} + \frac{R^2}{4L^2} - \omega^2 = 0$$

$$\frac{1}{LC} - \frac{R^2}{2L^2} + \frac{R^2}{4L^2} - \omega^2 = 0$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$


$$\omega^2 = \omega_0^2 - \left(\frac{R}{2L}\right)^2$$
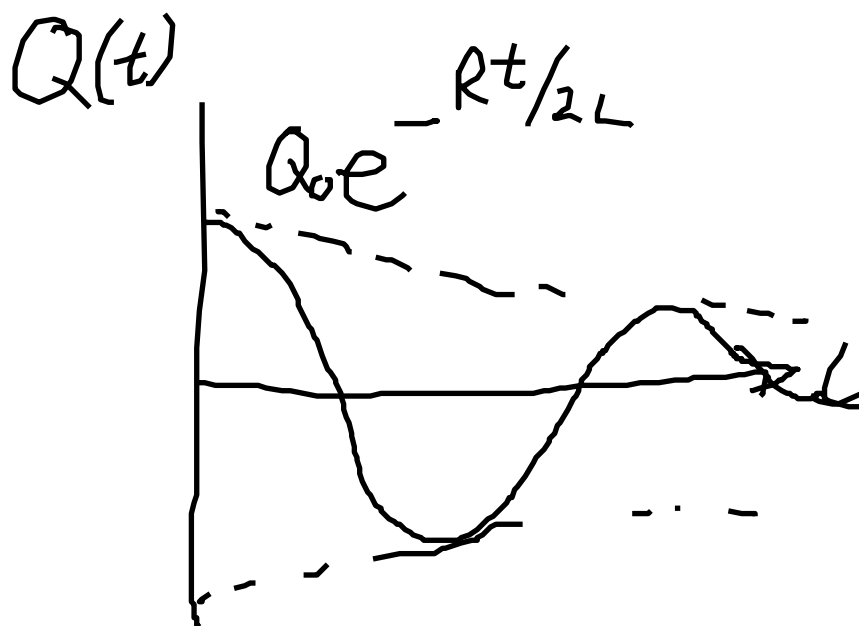
$$\omega = \sqrt{\omega_0^2 - \left(\frac{R}{2L}\right)^2}$$



Alternating Current

$$V(t)$$

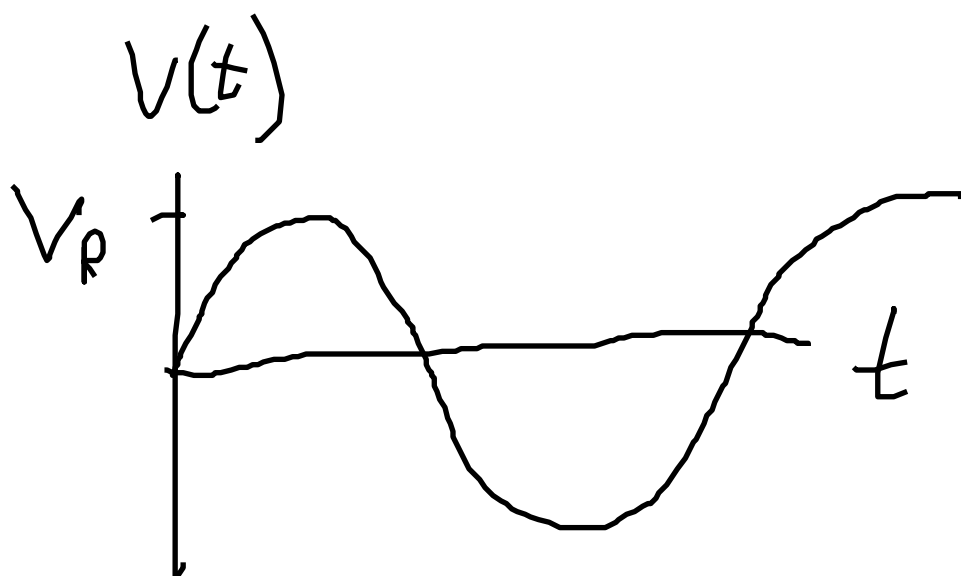


$$V(t) = V_p \cos(\omega t + \phi_0)$$

V_p : peak voltage

ω : ^{angular} frequency of oscillation

$$V(t) = V_p \cos(2\pi f t + \phi_0)$$

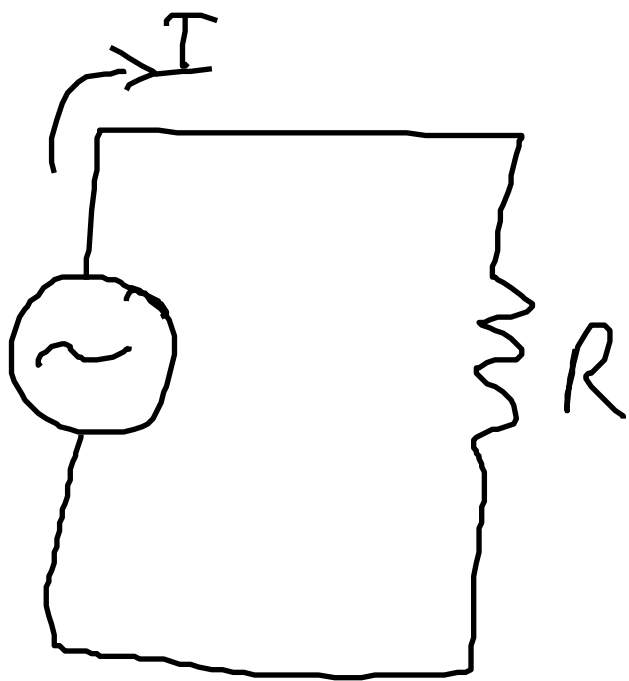

$$V(t) = V_p \cos(2\pi f t)$$


$$I(t) = \frac{V(t)}{R} = \frac{V_p}{R} \cos(2\pi f t)$$

$$P_{\text{output by resistor}} = I^2 R = \frac{V_p^2}{R} \cos^2(2\pi f t)$$

$$= \frac{V_p^2}{R} \cos^2(2\pi f t)$$

average
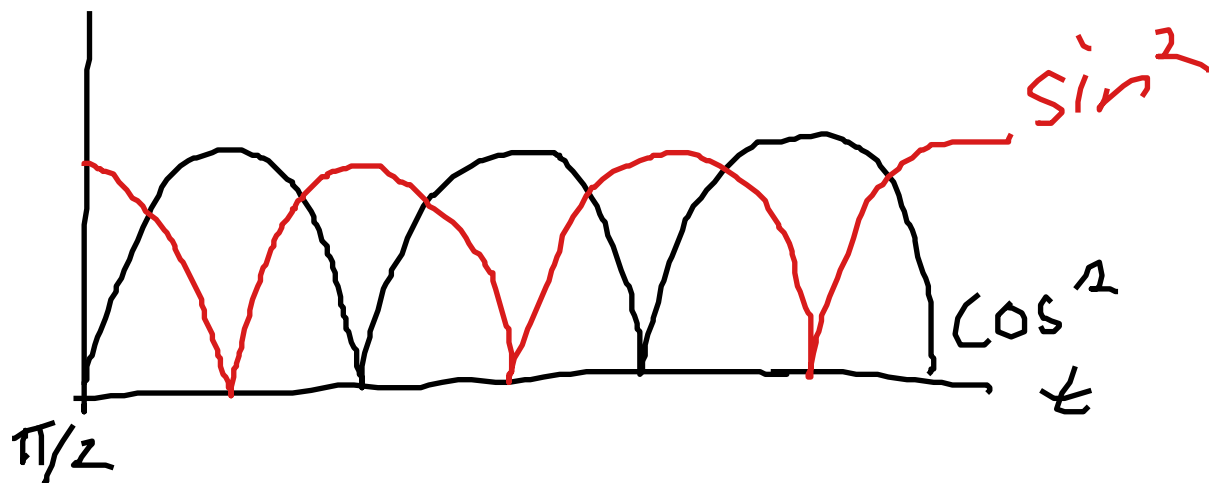
$$\langle P \rangle = \frac{V_p^2}{R} \langle \cos^2 2\pi f t \rangle$$



$$\langle \cos^2 + \sin^2 \rangle = 1$$

$$\langle \cos^2 \rangle + \langle \sin^2 \rangle = 1$$

$$2 \langle \cos^2 \rangle = 1$$

$$\langle \cos^2 \rangle = \frac{1}{2}$$

$$\langle P \rangle = \frac{1}{2} \frac{V_p^2}{R}$$

I'd really like to
write $\langle P \rangle = \frac{V_r^2}{R}$

$$\frac{1}{2} \frac{V_p^2}{R} = \frac{V_r^2}{R}$$

$$V_r^2 = \frac{V_p^2}{2}$$

$$\rightarrow V_{rms} = \frac{V_p}{\sqrt{2}}$$

what electricians talk about
in AC circuits

$$US: V_{rms} = 120V \quad f = 60Hz$$

$$V_p = 120 \times \sqrt{2} = 170V$$