
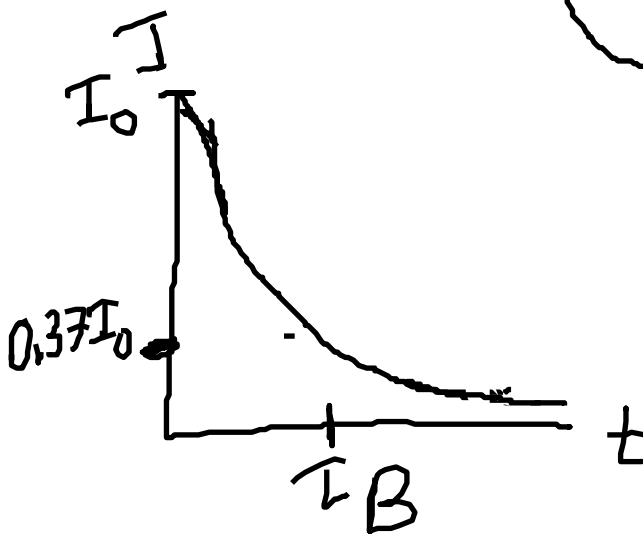
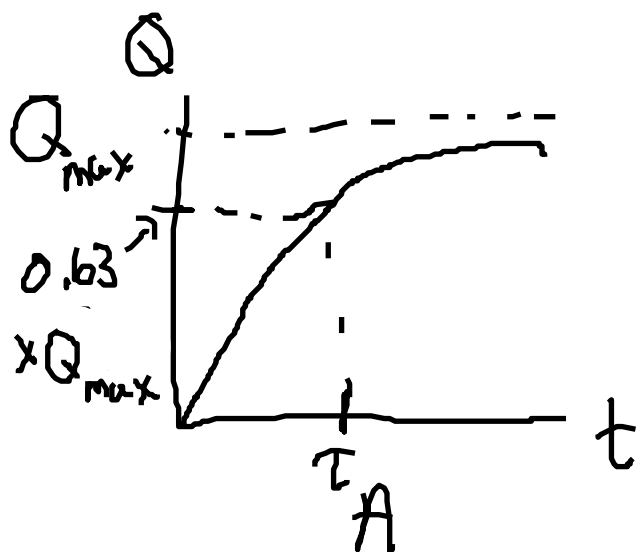


RC Circuits

- charging

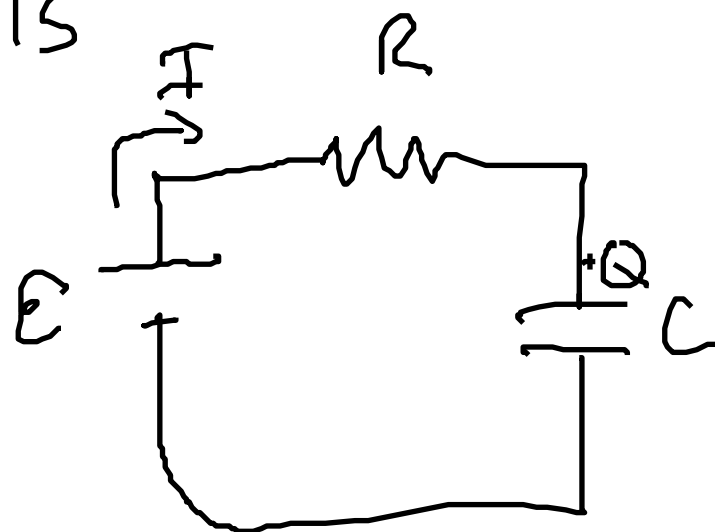

$$Q(t) = Q_{\max} (1 - e^{-t/RC})$$

$$I(t) = I_0 e^{-t/RC}$$

$$Q_{\max} = CE$$

$$I_0 = \frac{E_0}{R}$$

$\tau = RC$: time constant

time needed for $e^{-t/\tau}$ to reach 37%


• discharging

if I
is positive

Q is
decreasing

$$I = - \frac{dQ}{dt}$$

(sometimes $+$, sometimes $-$)

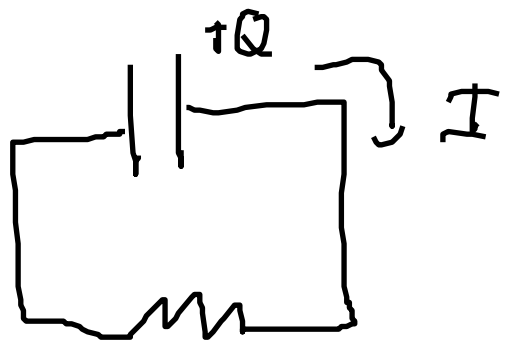


$$Q = Q_0 e^{-t/RC}$$

Q_0 = given
initial charge

$$I = I_0 e^{-t/RC}$$

$$I_0 = \frac{\Delta V}{R}$$


$$= \frac{Q_0}{RC}$$

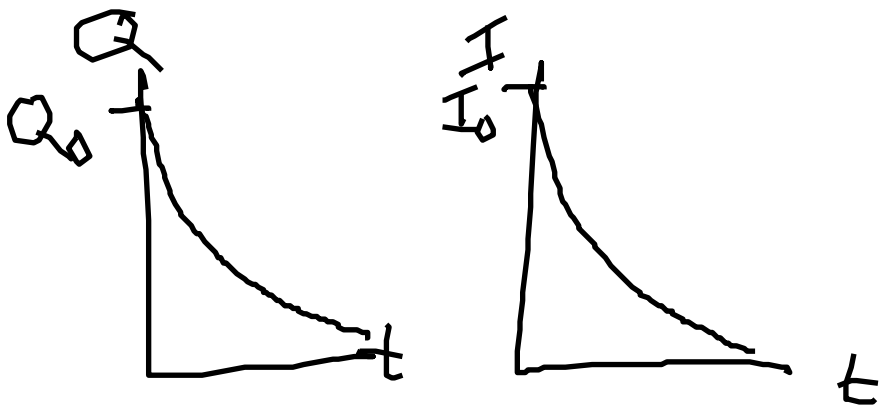

Suppose $C = 300 \mu\text{F}$ and $R = 200 \Omega$

How long for Q to reach
~37% of its initial value?
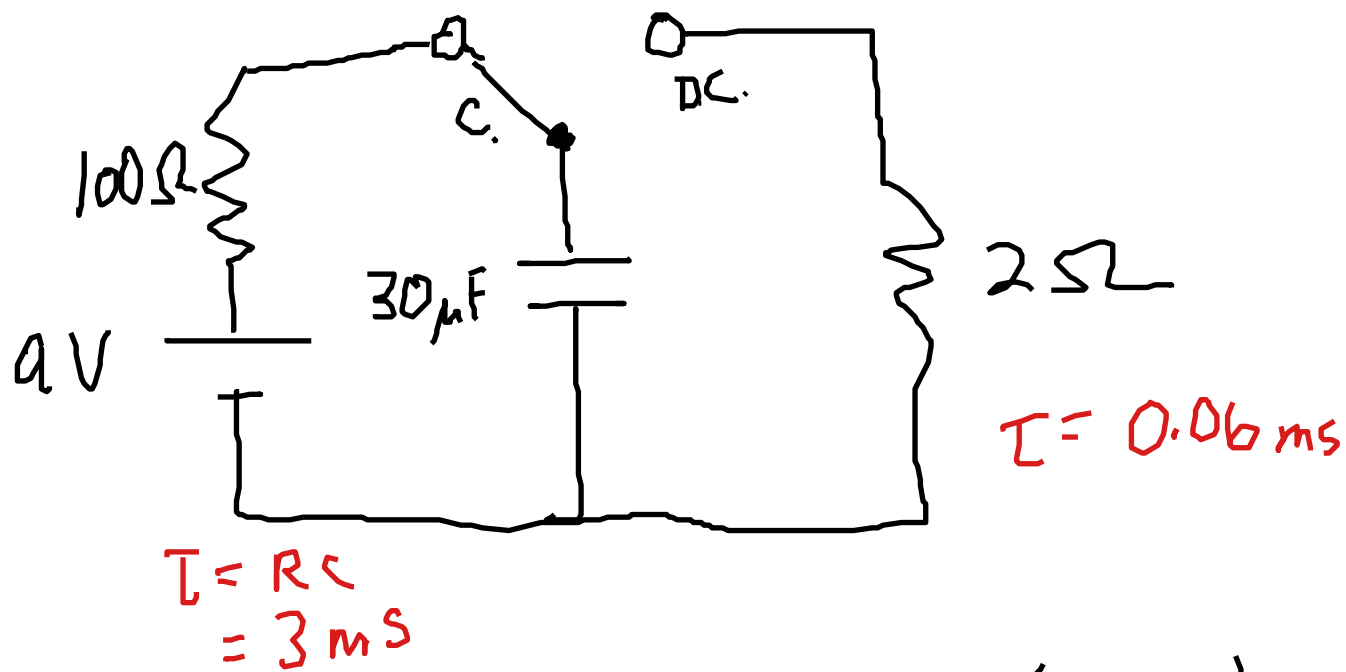
$$\tau = RC = (200)(300 \times 10^{-6}) = 60 \text{ ms}$$



Will this capacitor charge
or discharge faster?

Fast discharge, slow charge


- camera flash
- defibrillator

Fast charge, slow discharge

- electric car (theoretical)

Inductors

$$\Delta V = -L \frac{dI}{dt}$$

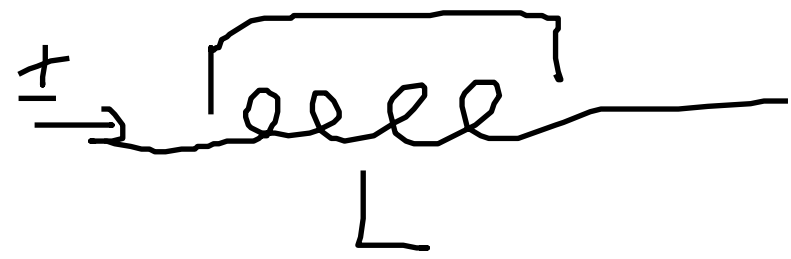


Inductance L : units of Henry


$$1 H = 1 \frac{Vs}{A} = 1 \Omega s$$



I inc. L acts like a resistor

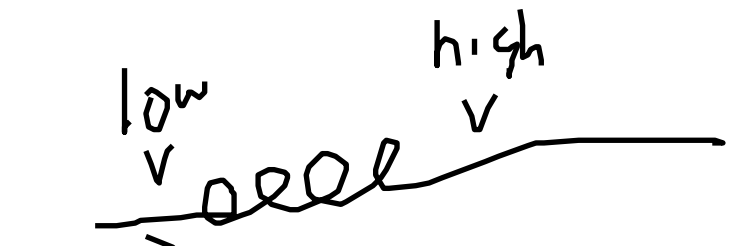

I dec. L acts like a battery

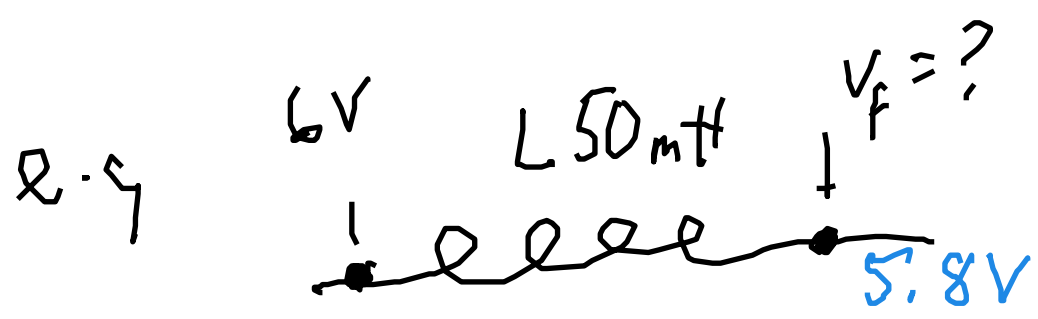

$$I(t) = (4 \frac{A}{s}) t$$

increasing

$$\Delta V = -L \frac{dI}{dt} = -(50 \times 10^{-3}) (4)$$

$$= -200 \times 10^{-3} V$$

$$\Delta V = -0.2 V$$

Alternating Current

$$V(t) = V_0 \cos(\omega t + \phi_0)$$

$$\mathcal{E}(t) = \mathcal{E}_0 \cos(\omega t + \phi)$$

$\mathcal{E}_0$: peak voltage

ω : angular frequency (rad/s)


$\omega = 2\pi f$ f : normal frequency (Hz)

Current must also oscillate with ω


$$I(t) = \underset{\text{peak current}}{I_0} \cos(\omega t + \phi_i)$$

$$\mathcal{E}_0 = I_0 Z$$

a whole-circuit equation

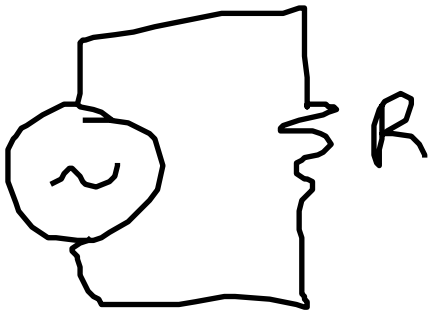


$$Z = R$$

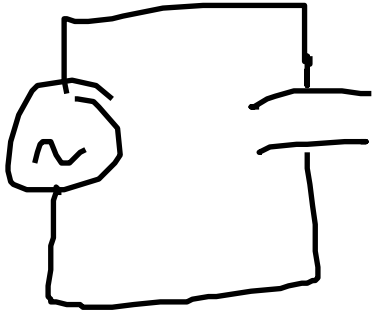


$$Z = \frac{1}{\omega C} = X_C$$

Capacitive
reactance

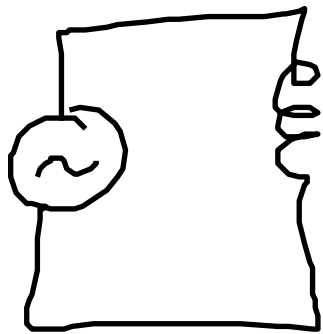

$$Z = \omega L = X_L$$

Inductive
reactance

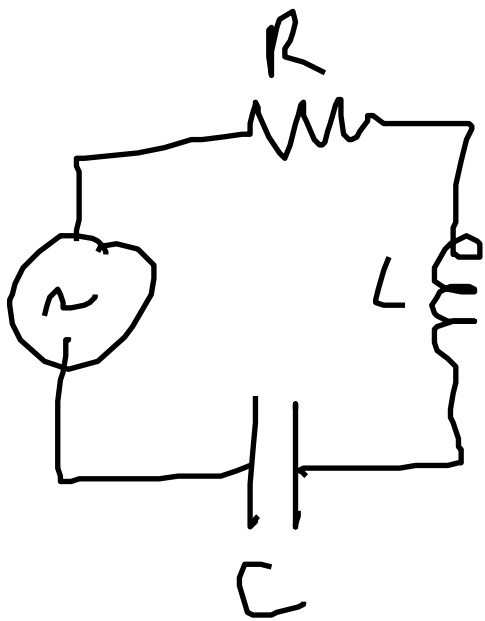

$$Z = \sqrt{R^2 + (X_C - X_L)^2}$$

7

$$I(t) = I_0 \cos \omega t$$

$$E(t) = E_0 \cos(\omega t - \phi)$$

$$\tan \phi = \frac{X_C - X_L}{R}$$

$\phi > 0$: current leads voltage

$\phi < 0$: current lags voltage