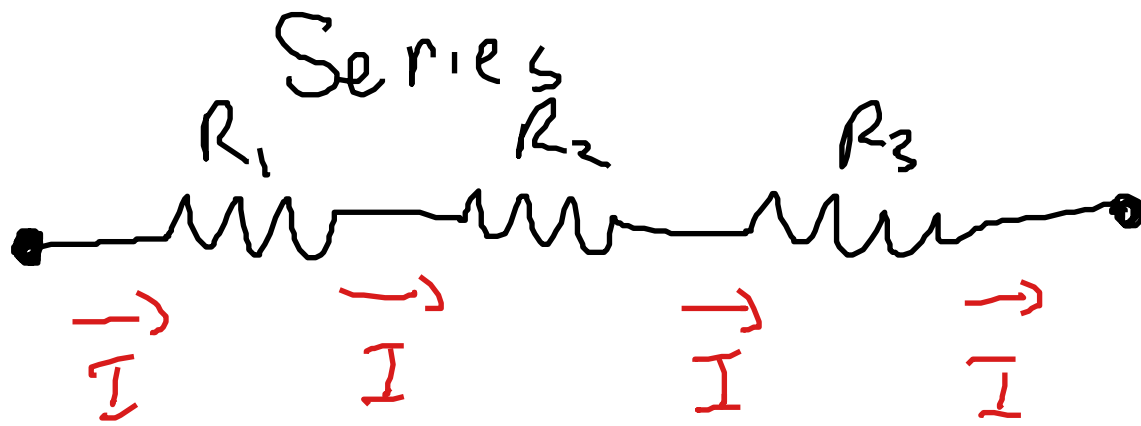




We can replace these
with a single resistor


having the same equivalent resistance:

series

$$R_{eq} = R_1 + R_2 + R_3 + \dots$$

Same
as



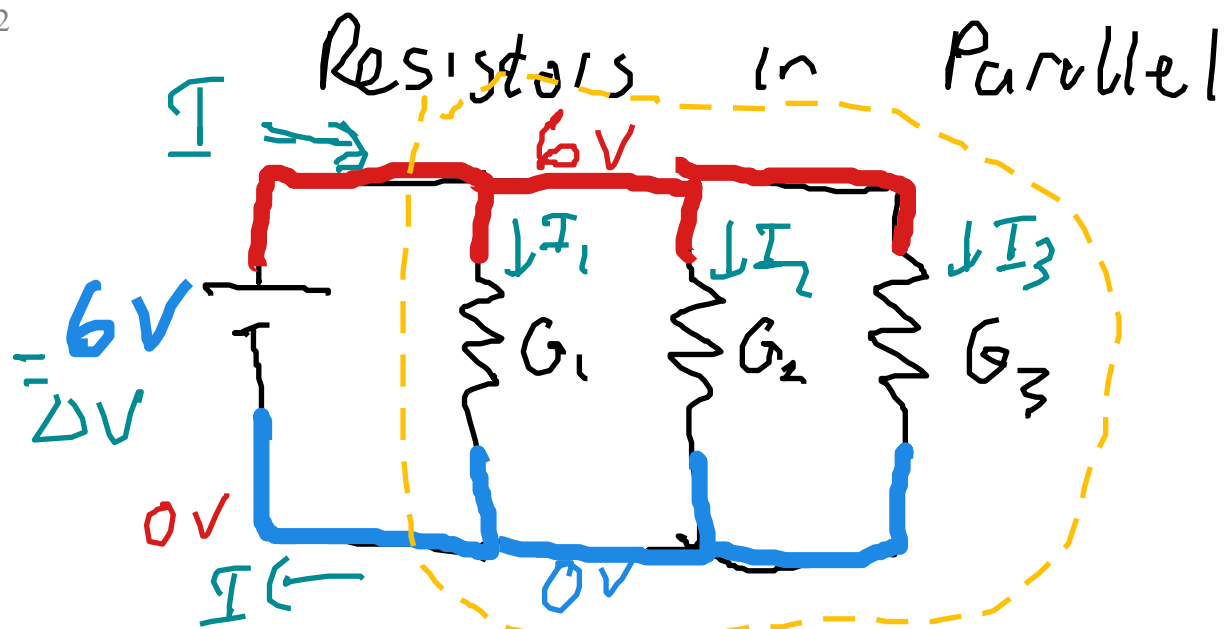

$$G = \frac{1}{R}$$


All have identical potential drops ΔV .

$$I = G \Delta V$$

$$I = I_1 + I_2 + I_3$$

$$G_{eq} \Delta V = G_1 \Delta V + G_2 \Delta V + G_3 \Delta V$$

$$(G_1 + G_2 + G_3) \Delta V$$

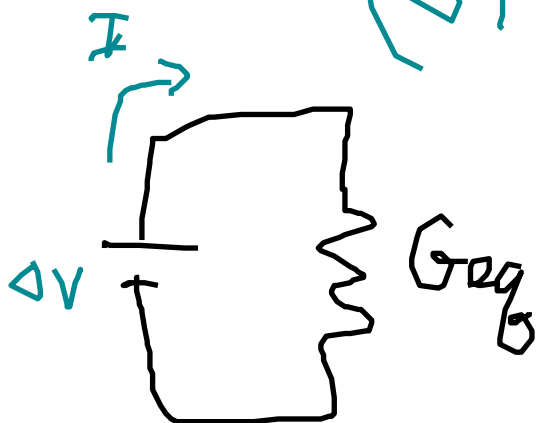


$$G_{eq} = G_1 + G_2 + G_3$$

Series: resistances add

Parallel: conductances add
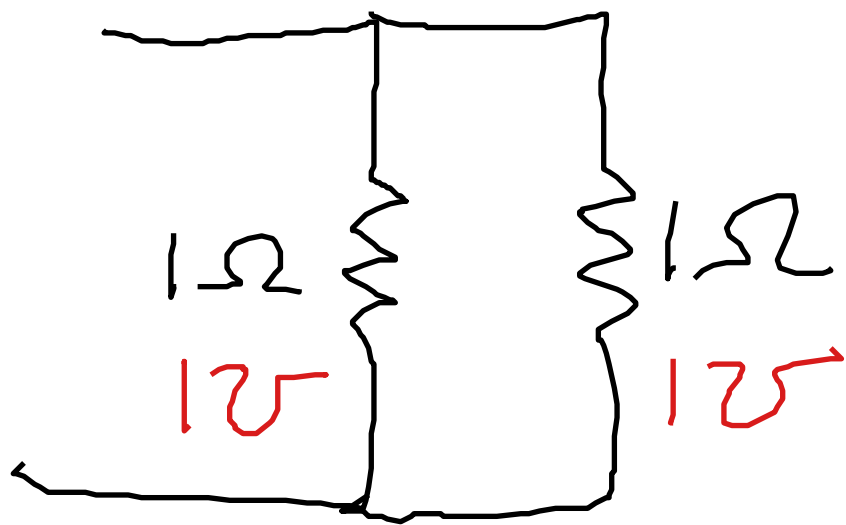
$$\hookrightarrow \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$



$$G_{eq} = 2\text{V}$$

$$R_{eq} = \frac{1}{2\text{V}} = \frac{1}{2}\Omega$$

$$\frac{1}{R_{eq}} = \frac{1}{1} + \frac{1}{1} = 2 \rightarrow R_{eq} = \frac{1}{2}$$

R_{eq} is


$$< 1\Omega$$

$$= 1\Omega$$

$$1 - 2\Omega$$

$$= 2\Omega$$

$$> 2\Omega$$

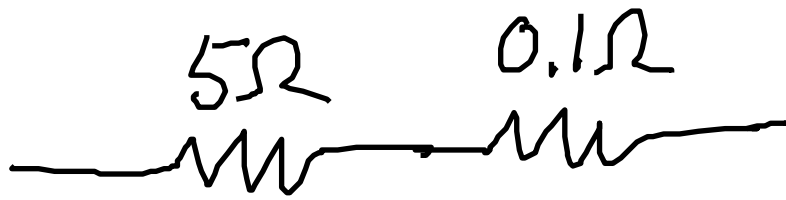


$$R_{eq} = 5 + 0.1 = 5.1$$

R_{eq} is larger than any
one resistance in series

like security line at airport



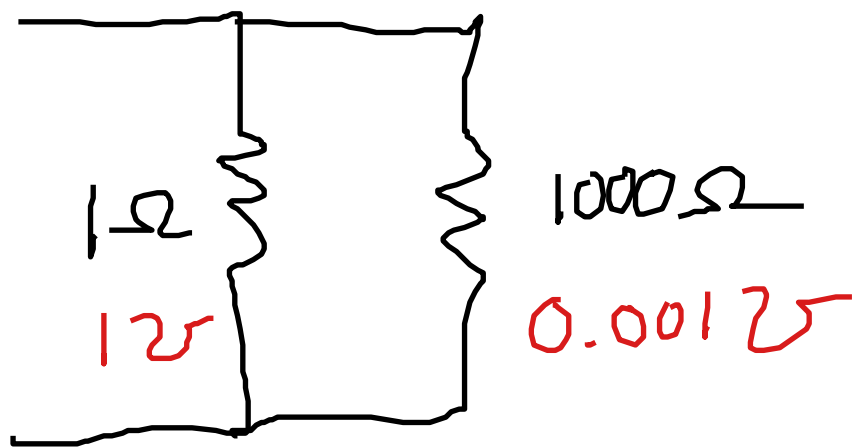← even a
quick additional
stop will
slow down
the line.




$$G_{eq} = 1.001S$$

$$R_{eq} = \frac{1}{1.001S} \approx 0.999\Omega$$

for resistors in parallel,

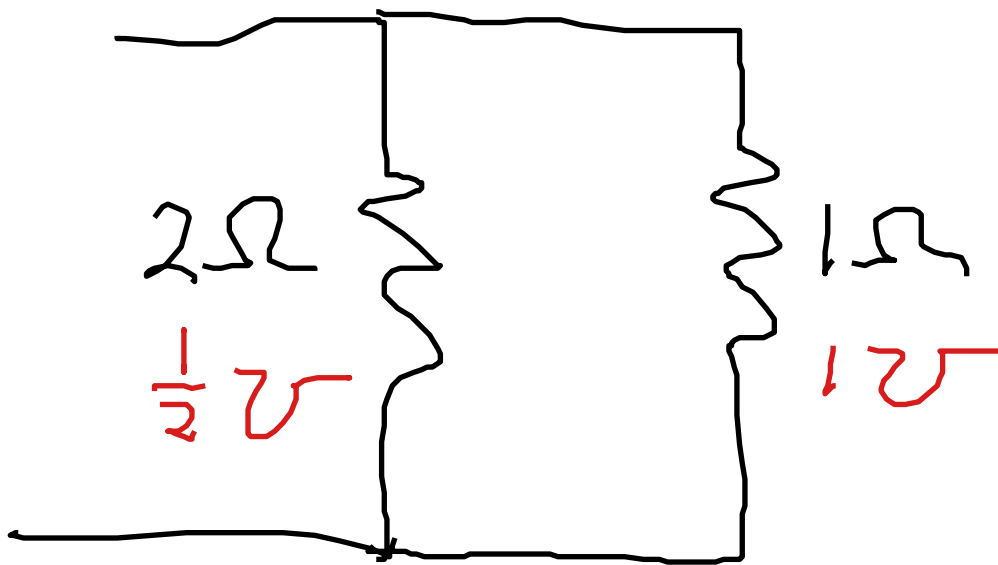R_{eq} is smaller than all individual resistors




$R_{eq}?$

$$G_{eq} = \frac{1}{2}V + 1V$$

$$= \frac{3}{2}V = 1.5V$$


$$R_{eq} = \frac{1}{\frac{3}{2}V} = \boxed{\frac{2}{3}\Omega}$$

7
Identifying Series and parallel

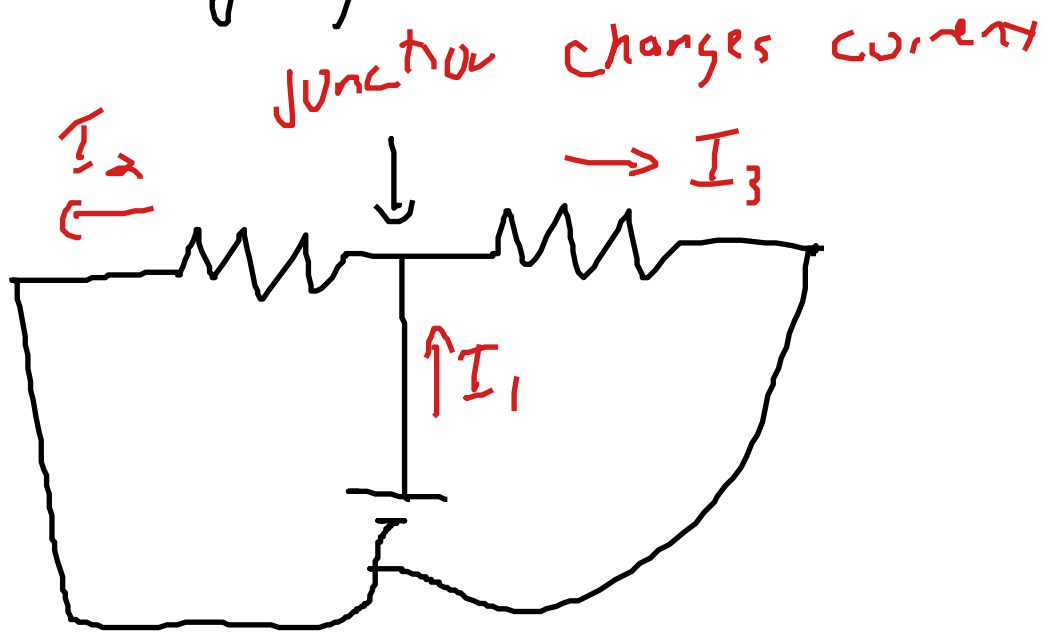

Series? parallel? neither?

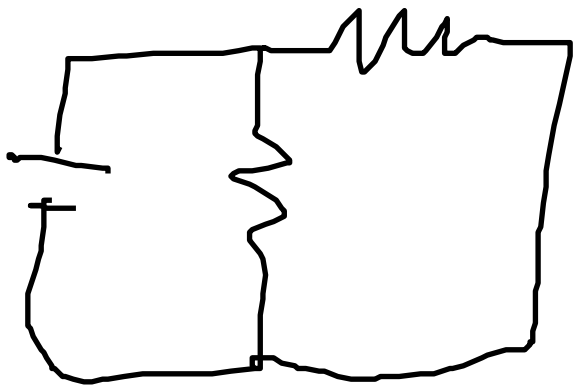because they have the
same potential drop
across them



Also in
parallel

- Series: if you can draw a path from one resistor to the other without crossing a junction, they are in series





A, B, C are
in series
with each other

D is not

9

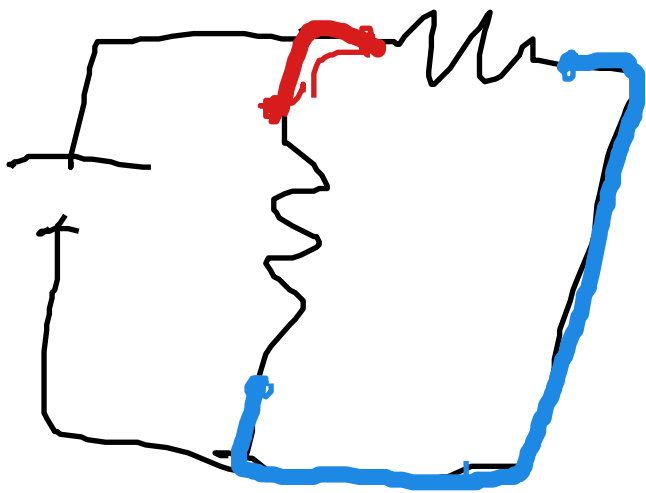- Parallel: if you can connect the heads of two resistors & their tails with paths that do not cross another circuit element (junctions don't count) then they are in parallel



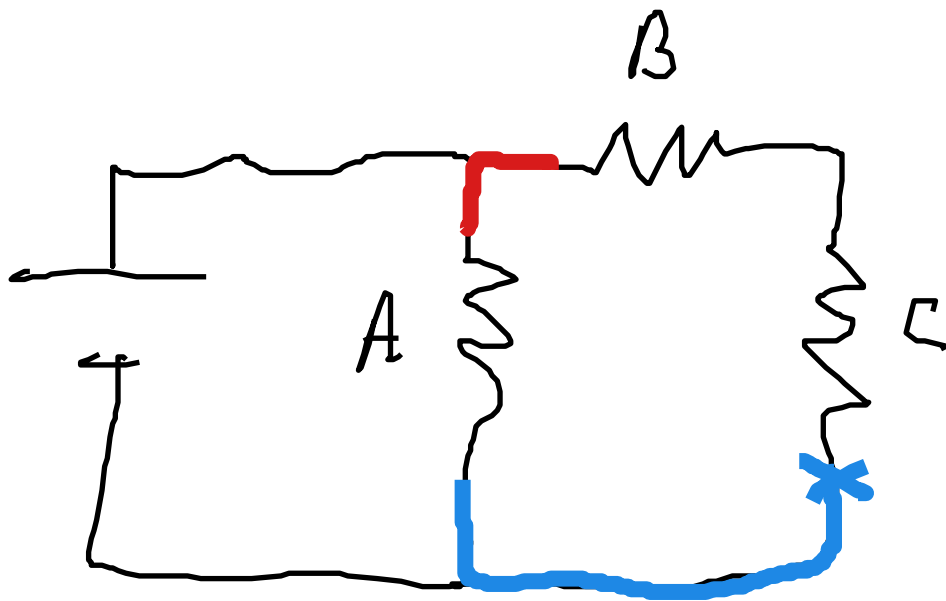

Are any of these
in parallel?

A & B are not in parallel

A & C are not in parallel

B & C are in series
not parallel

So NO

$$G_{eq} = G_1 + G_2 + G_3 \dots$$

Resistance Reduction

- Find resistors in series or parallel.
- Replace with Req.
- Continue until 1 resistor or as far as you can.

