

1
Conductor in Electrostatic

Equilibrium : $E = 0$ inside


$\Delta V = 0$ inside

constant V

Current : steady flow of charge

Electrostatic equilibrium means
no current

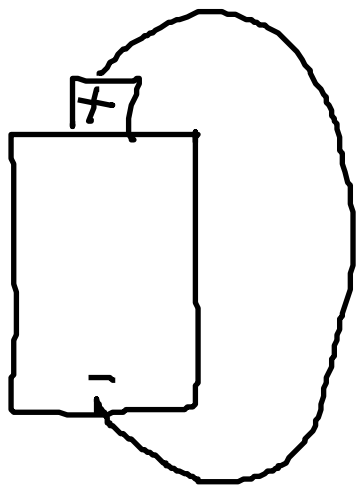battery:
maintains
a constant
 $\Delta V \neq 0$



metal wire
maintains
a $\Delta V = 0$


FIGHT!

which wins?

battery (in the short term)


there is $\Delta V > 0$ across

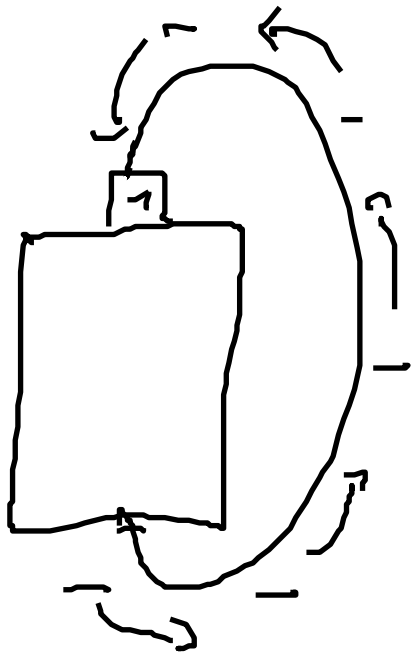the wire $\rightarrow$ current in the wire



What really happens

negative
charge
carriers

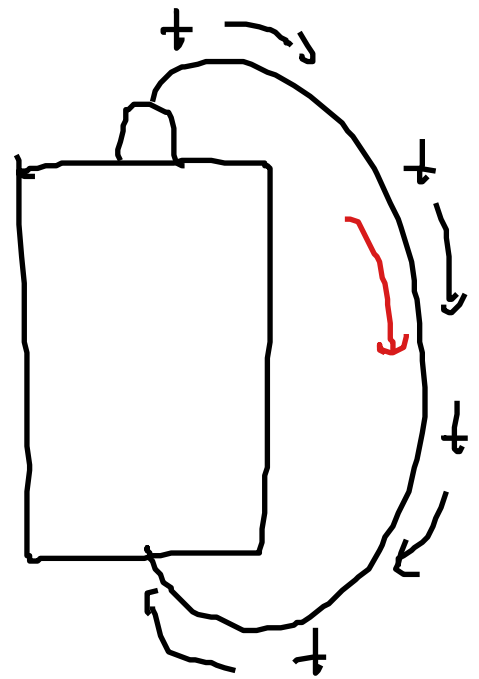

conventional
current

positive
charge
carriers


Current is defined to point
in direction positive charge
carriers would flow
from higher potential to
lower potential "downhill"

$$\text{Current} = \frac{\text{charge that flows past}}{\text{second}}$$


in physics: I

$$\text{units: } \frac{\text{coulomb}}{\text{second}} = \text{Ampere or Amp} \\ (1A)$$

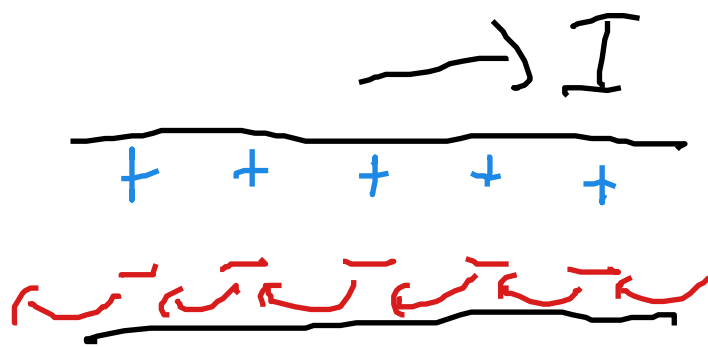I is proportional to # of
charge carriers and their speed



Wire has no net charge

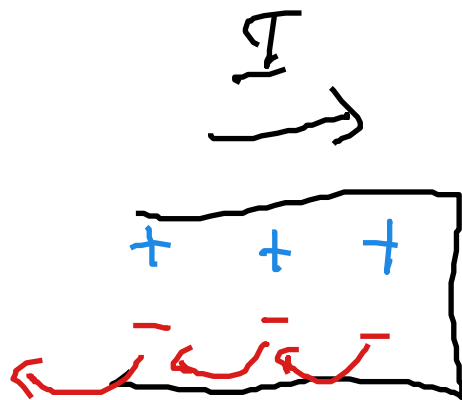



becomes +
charged -
pulls electrons
back

break in the wire

no steady current flows

Current flows in closed circuits

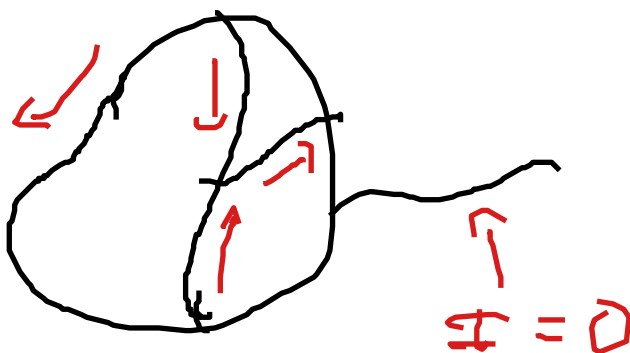

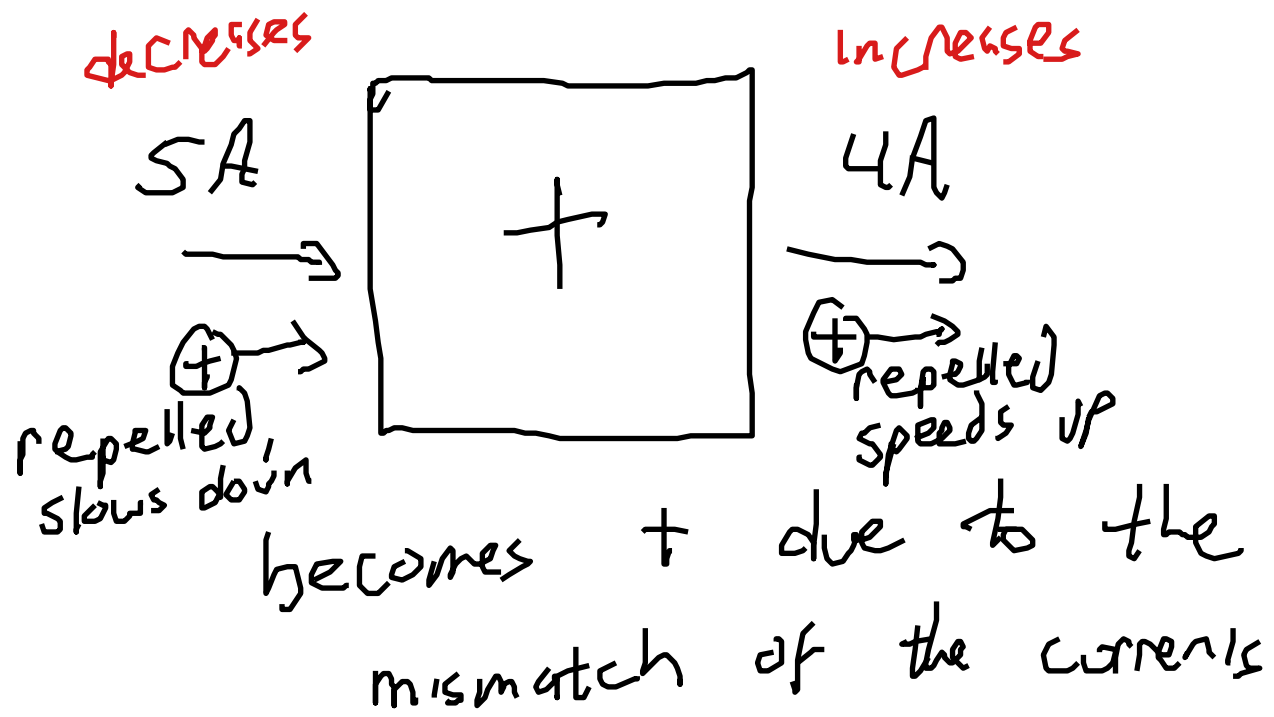


Currents even out quickly

Steady Current

$$\text{current in} = \text{current out}$$

"Conservation of Current"



"Kirchhoff's Junction Law"

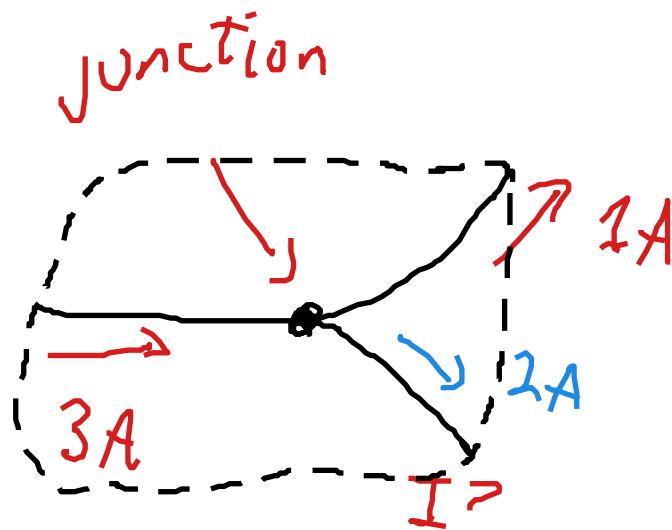

$I_N: 3A$

$OUT: 1A + 2A$

— — — — —

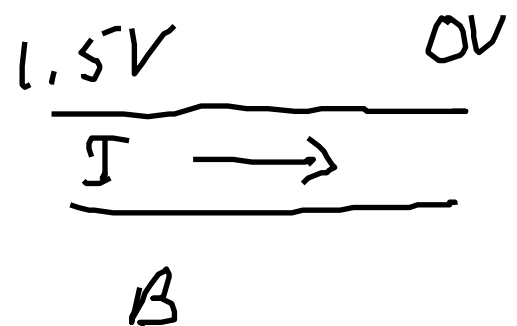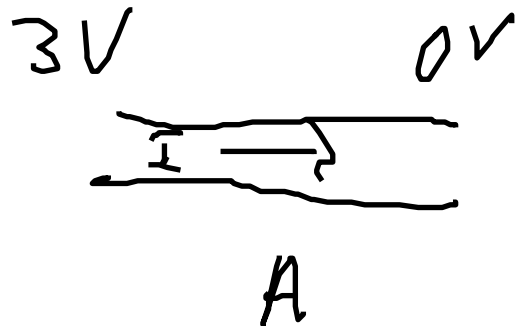

Current flows downhill

Which one has the

larger current?

A: steeper drop, more current


$$I \sim \Delta V$$

$$I = G \Delta V$$

G : "conductance" of wire
how well electricity flows

for a wire,

$$G = \sigma \frac{A}{L}$$

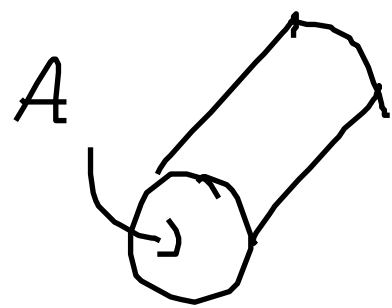

A : cross-sectional area of wire
(m^2)

L : length of wire (m)

σ : conductivity of material

9

metal $\sigma = 10^8$
glass $\sigma = 10^{-12}$

$$\frac{1}{G} \equiv R$$

resistance of wire
how badly electricity flows

$$I = G \Delta V \quad \begin{array}{c} \nearrow I = \frac{1}{R} \Delta V \\ \searrow \Delta V = IR \end{array}$$

Ohm's Law