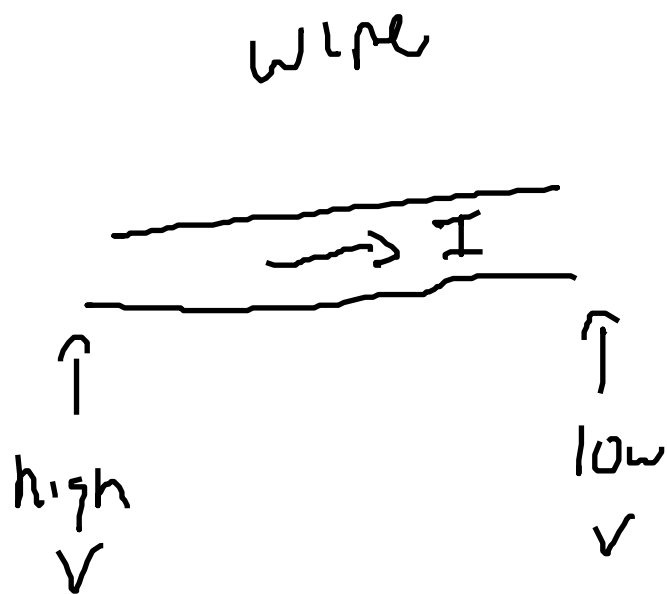




Ohm's Law

$$I = G \Delta V$$

Conductance

$$\Delta V = I R$$

resistance

$$G = \frac{1}{R}$$

Capital
omega
↓

Units of R : $\frac{\text{Volts}}{\text{Amperes}} = \text{Ohm } (\Omega)$

Units of G : $\frac{1}{\Omega}$

Official SI name

$\frac{1}{\Omega}$: siemens (S)

more fun name

mho ($\Uparrow$)

For a wire:

Conductance





$$G = \sigma \frac{A}{L}$$

σ : conductivity
of material

$$R = \rho \frac{L}{A}$$

$\rho = \frac{1}{\sigma}$: resistivity
of material

Copper wires

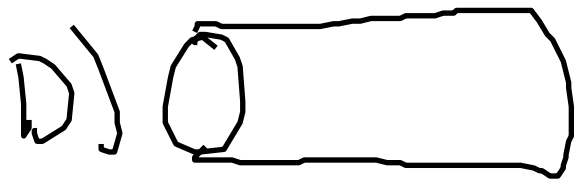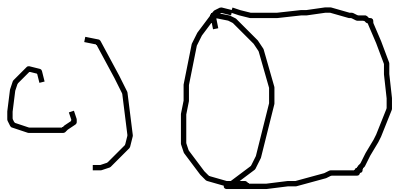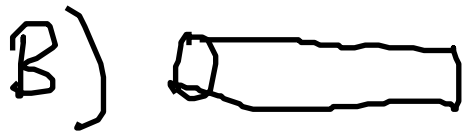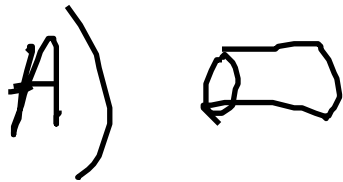

E) All the same


All devices with two terminals
(places to hook a battery)
have ^a resistance:

$$R \equiv \frac{\Delta V}{I}$$

$$G \equiv \frac{I}{\Delta V}$$

R might depend on ΔV
in this case

e.g. diode

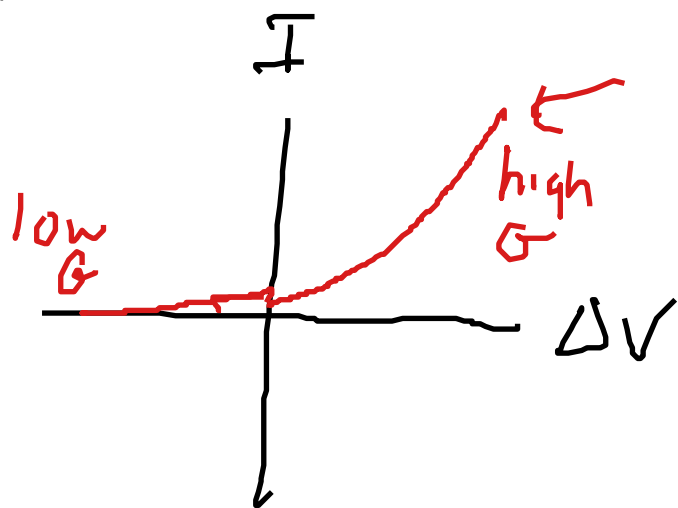


$$\frac{I}{\Delta V} = G(\Delta V)$$

non-ohmic device


because G & R are not
constant


Wires are ohmic devices

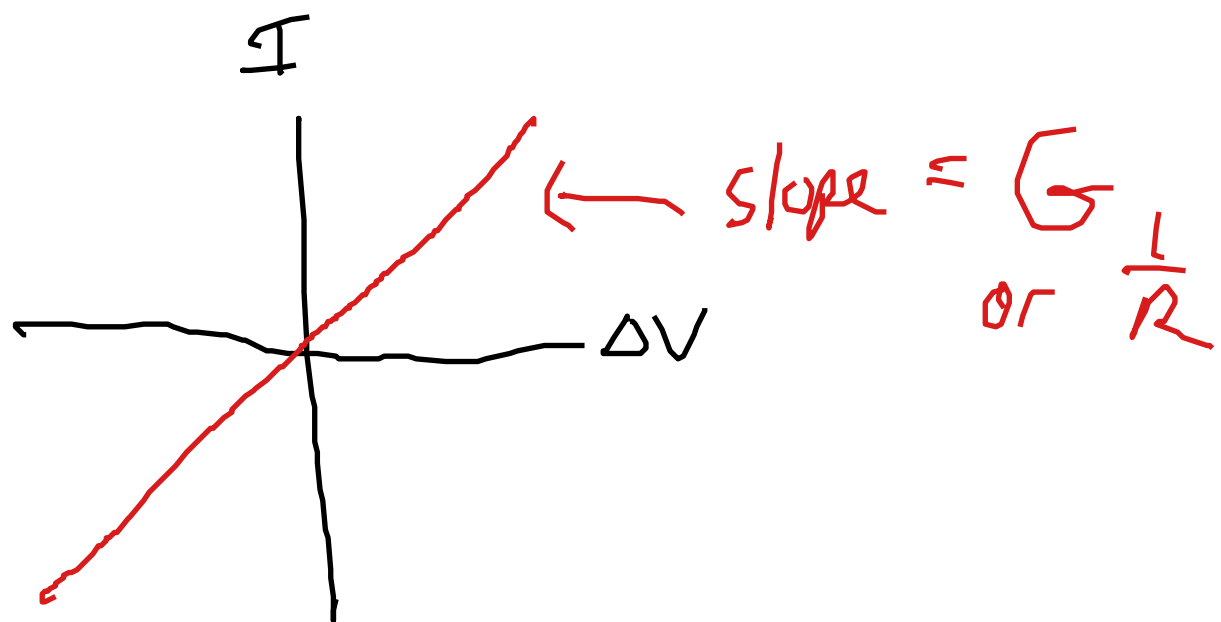

Certain devices are designed to be ohmic with a specific resistance resistors

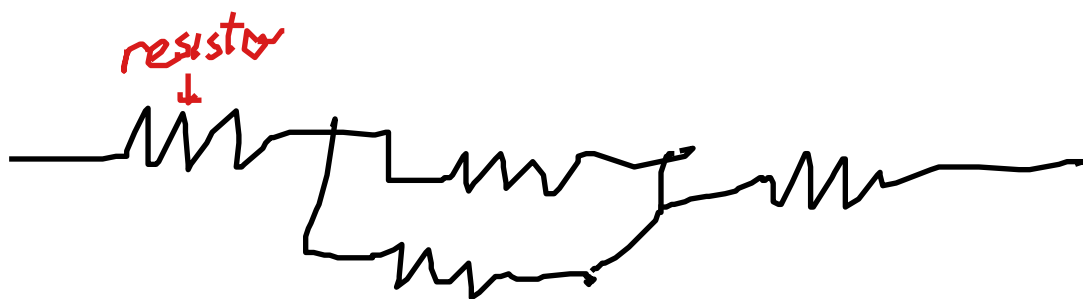Combinations of ohmic devices are also ohmic



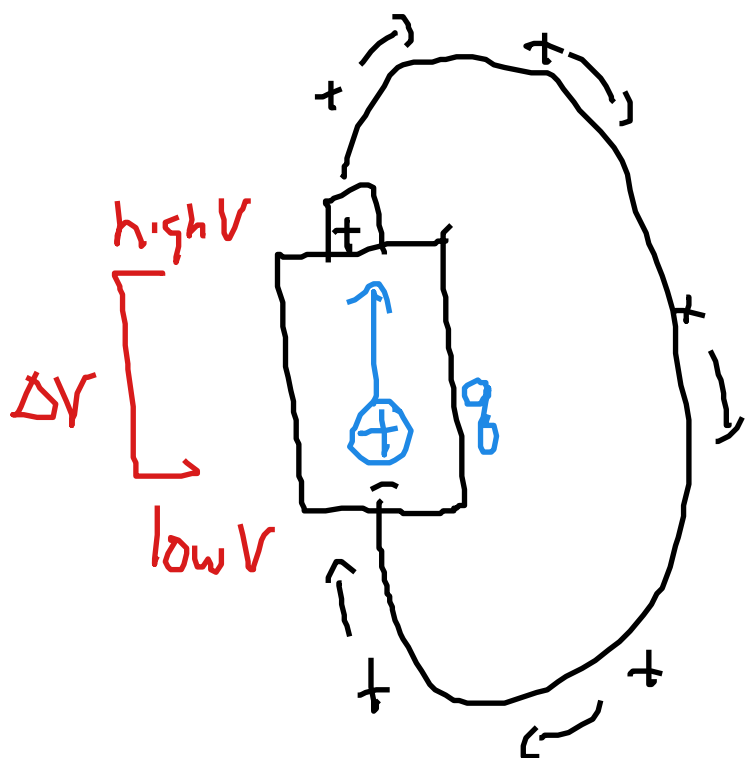

Work done by battery
on this charge q

$$\Delta PE = q \Delta V$$

$$\frac{\text{Work}}{\text{time}} = \frac{(\text{Charge}) (\Delta V)}{\text{time}}$$

power →

$$P = I \Delta V$$

Units of power: Watts (W)

$$1 \text{ Watt} = 1 \frac{\text{J}}{\text{s}} = 1 \underset{\text{A}}{\text{C}} \cdot \underset{\text{C}}{\text{J}} \text{V}$$

When current flows uphill,

$P = I \Delta V$ must be supplied
by a battery etc.

When current flows downhill,

$P = I \Delta V$ is released

as heat, light, sound, motion, etc

↑
for a plain wire

e.g. 3W light bulb connected to
two AA batteries (3V)

$$P = I \Delta V$$

$$3W = I(3V) \rightarrow I = 1A$$

7

$$\Delta V = IR$$

$$P = I^2 R$$


$$P = G(\Delta V)^2$$

$$= \frac{(\Delta v)^2}{R}$$

A) 40W light bulbs

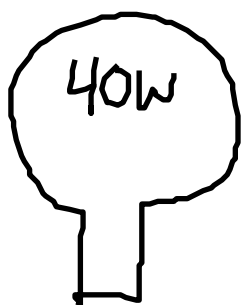B) 60 W light bulb

ΔV is same for both, $P = \frac{[\Delta V]^2}{R}$ ← same
higher ← lower




$$P = I \Delta V$$

$$(40) = I(120)$$

$$I = \frac{1}{3} A$$

$$= 0.3 A$$

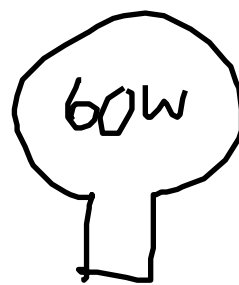

$$P = I \Delta V$$

$$(60) = I(120)$$

$$I = \frac{1}{2} A$$

$$= 0.5 A$$


Wires usually have low resistance

lab: $160 \text{ m}\Omega / \text{m}$

house wiring: $6.5 \text{ m}\Omega / \text{m}$

minimize energy loss during transmission

ideal wire: 0Ω

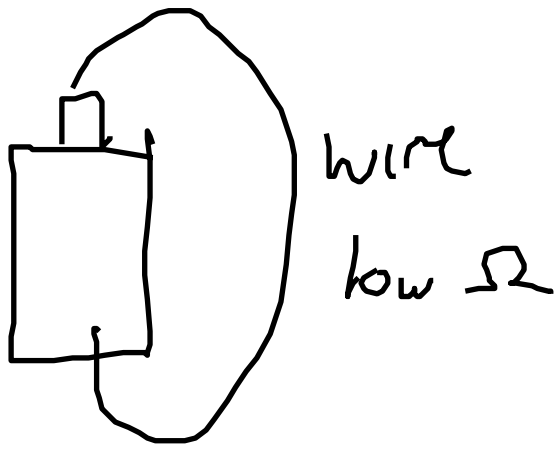

power output of wire is huge

huge $\rightarrow P = \frac{(\Delta V)^2}{R}$ $\leftarrow$ fixed by battery
 $R \leftarrow$ tiny

Short circuit