
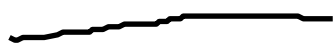


Schematic Circuit Diagrams

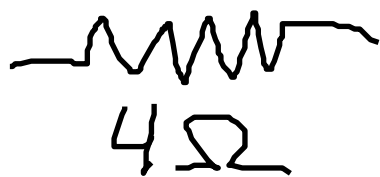


wire

(ideal wire: $R=0$)




resistor


(ohmic: $R = \text{constant}$)

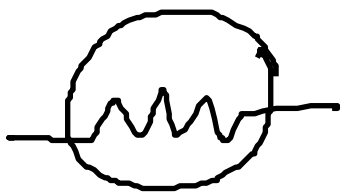


light bulb

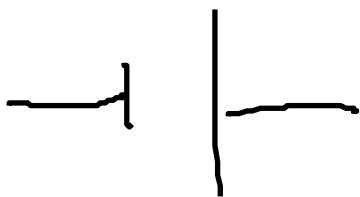

battery or
power supply

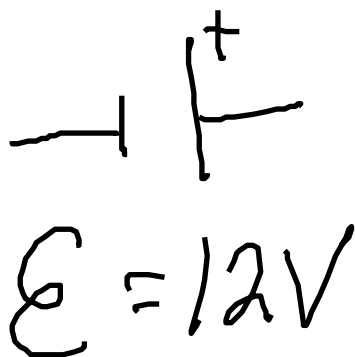

emf: potential
difference across battery

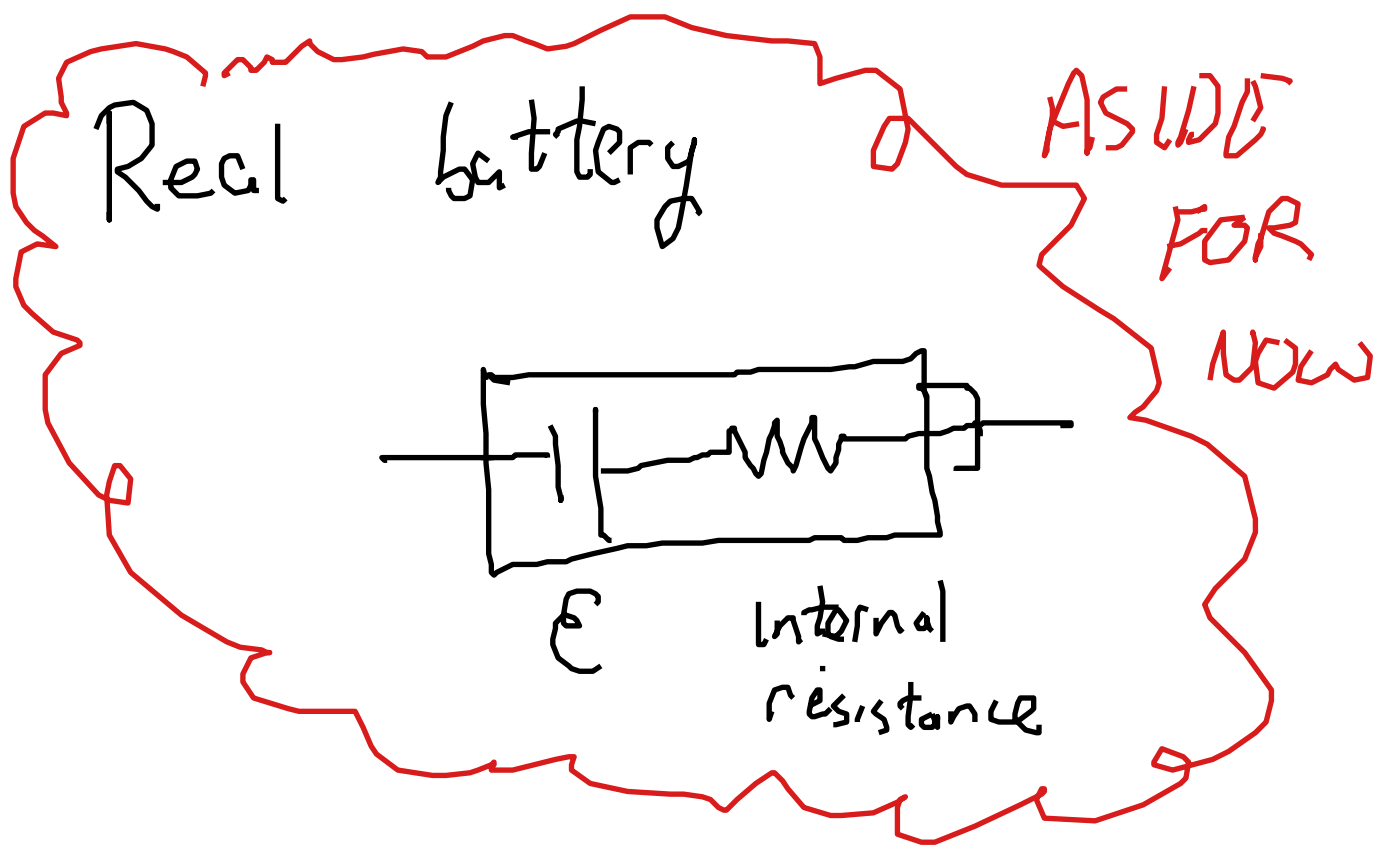


Ground!


We can call any one spot
on a circuit " $V=0$ "
(only ΔV matter)

In practice, ground also refers
to the potential of passers-by

$$\Delta V = IR = I(0) = 0$$

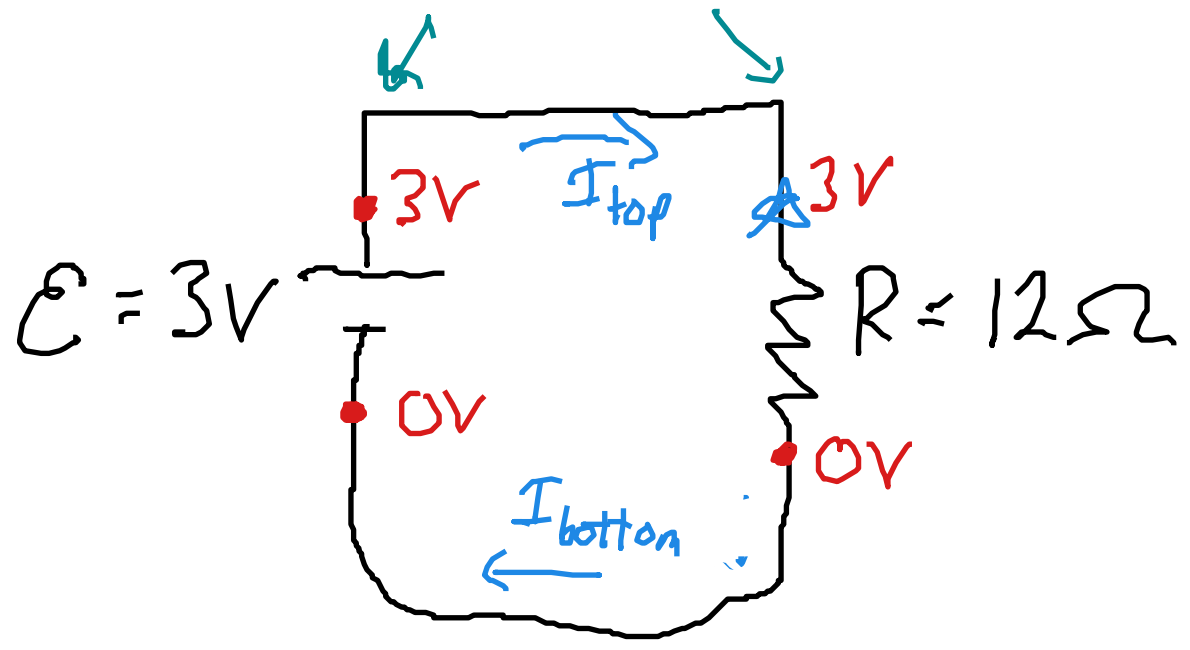

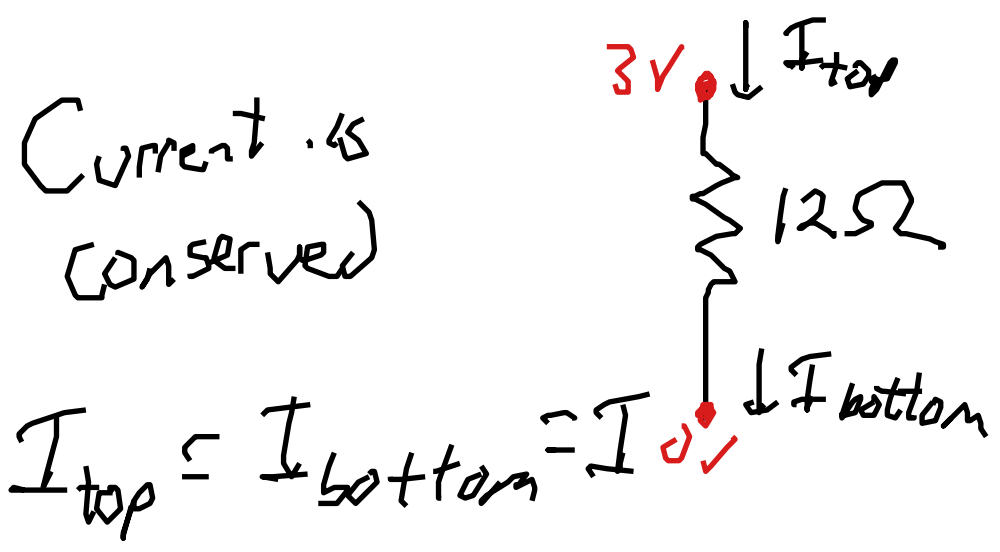Every point on an ideal wire has the same potential



Current is conserved

$$\Delta V = IR$$

$$3 = I(12)$$



$$0.25A = I$$

Current is not "used up" by resistor.

Current is a carrier for energy







Geometry doesn't matter

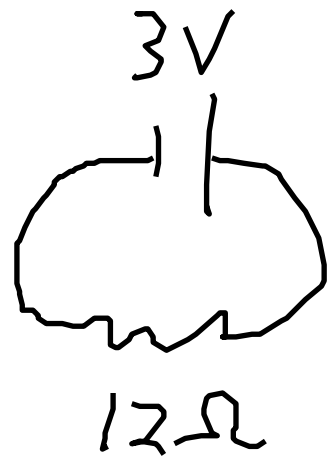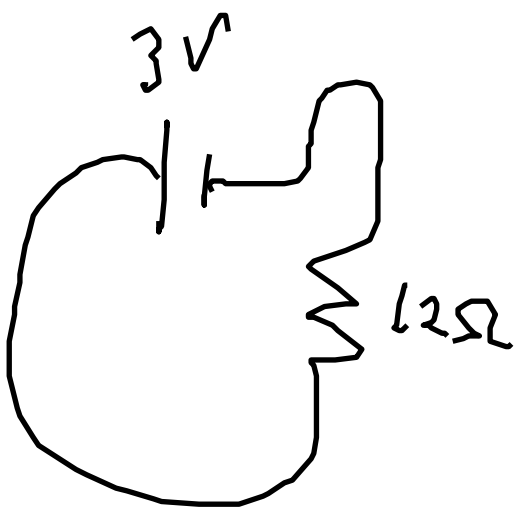


Connections matter

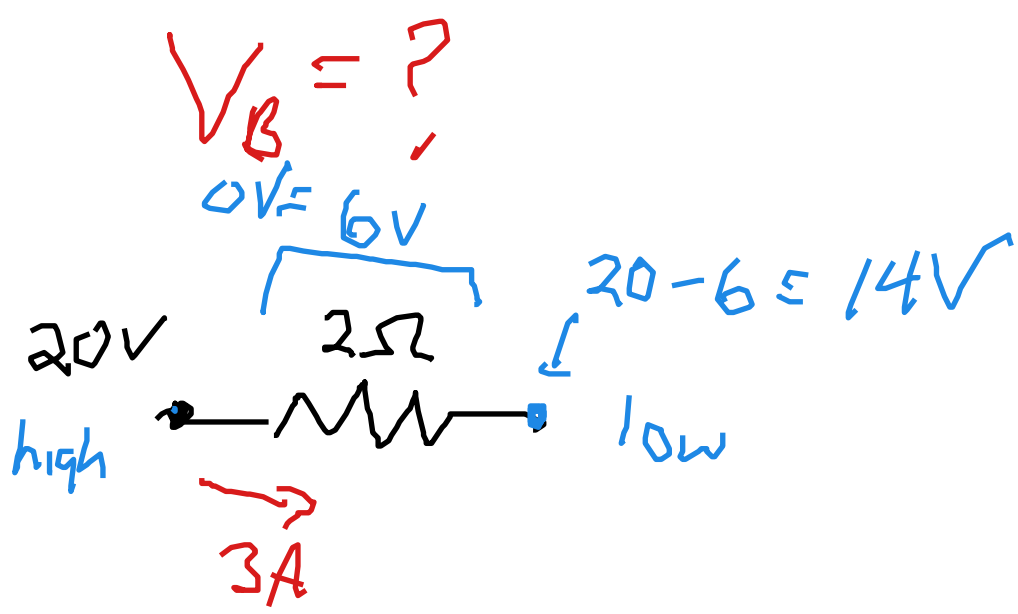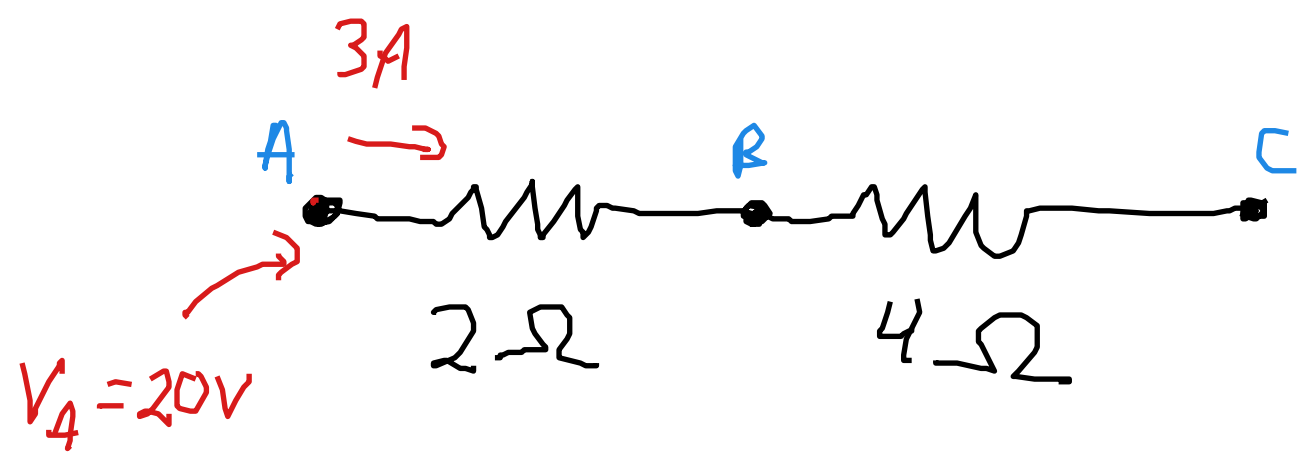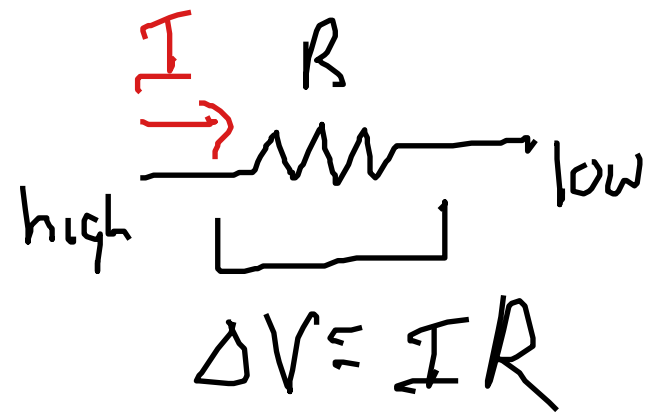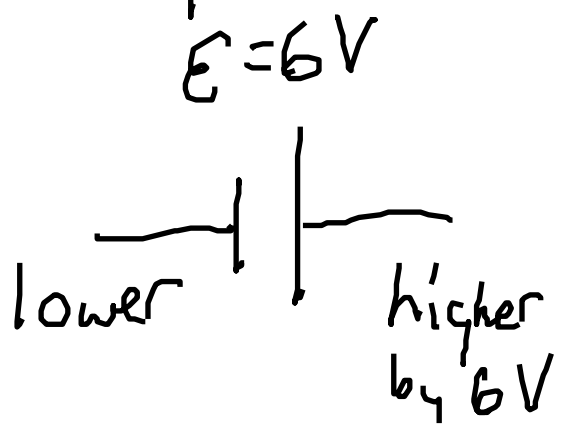Batteries & resistors involve potential changes



$$\Delta V = IR = (3A)(2\Omega) = 6V$$


What is potential at C?

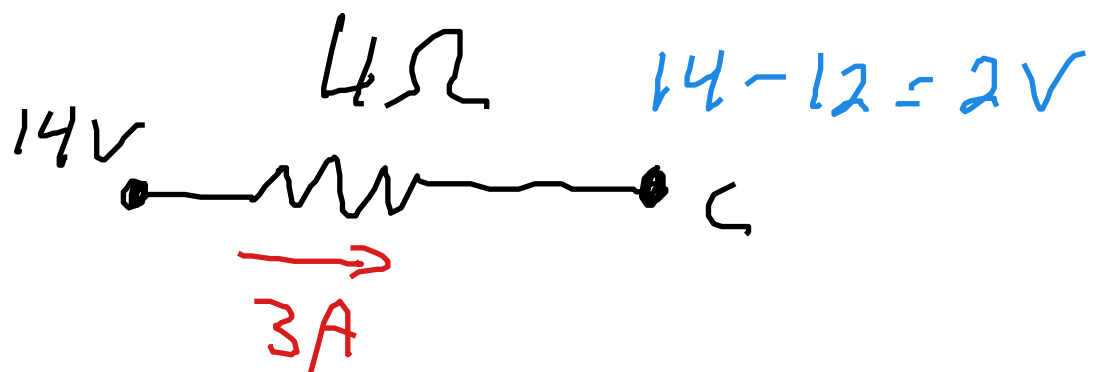

$$\Delta V = 12V = (3)(4)$$

Tally Method

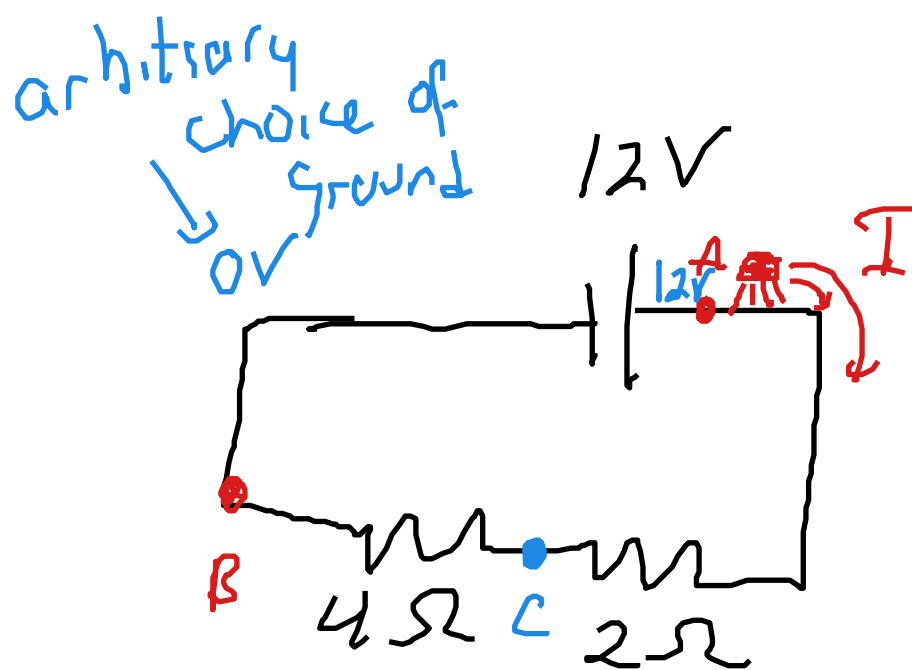- Start at point A
- Move towards point B, keeping track of ΔV along way
- $\Delta V = V_B - V_A =$ total tally of changes



$$\begin{array}{r} -I(2) \\ -I(4) \\ \hline \end{array}$$

$$V_B - V_A = -6I$$

$$V_B = V_A - 6I$$

$$\begin{array}{l} \text{if } V_B = 0 \\ V_A = 12 \end{array}$$

$$\begin{array}{l} 0 = 12 - 6I \\ I = 2A \end{array}$$

$$V_c$$

$$\frac{12 - 2(I)}{V_c}$$

$$12 - 2I = V_c$$

$$12 - 2(2) = V_c$$

$$8 = V_c$$