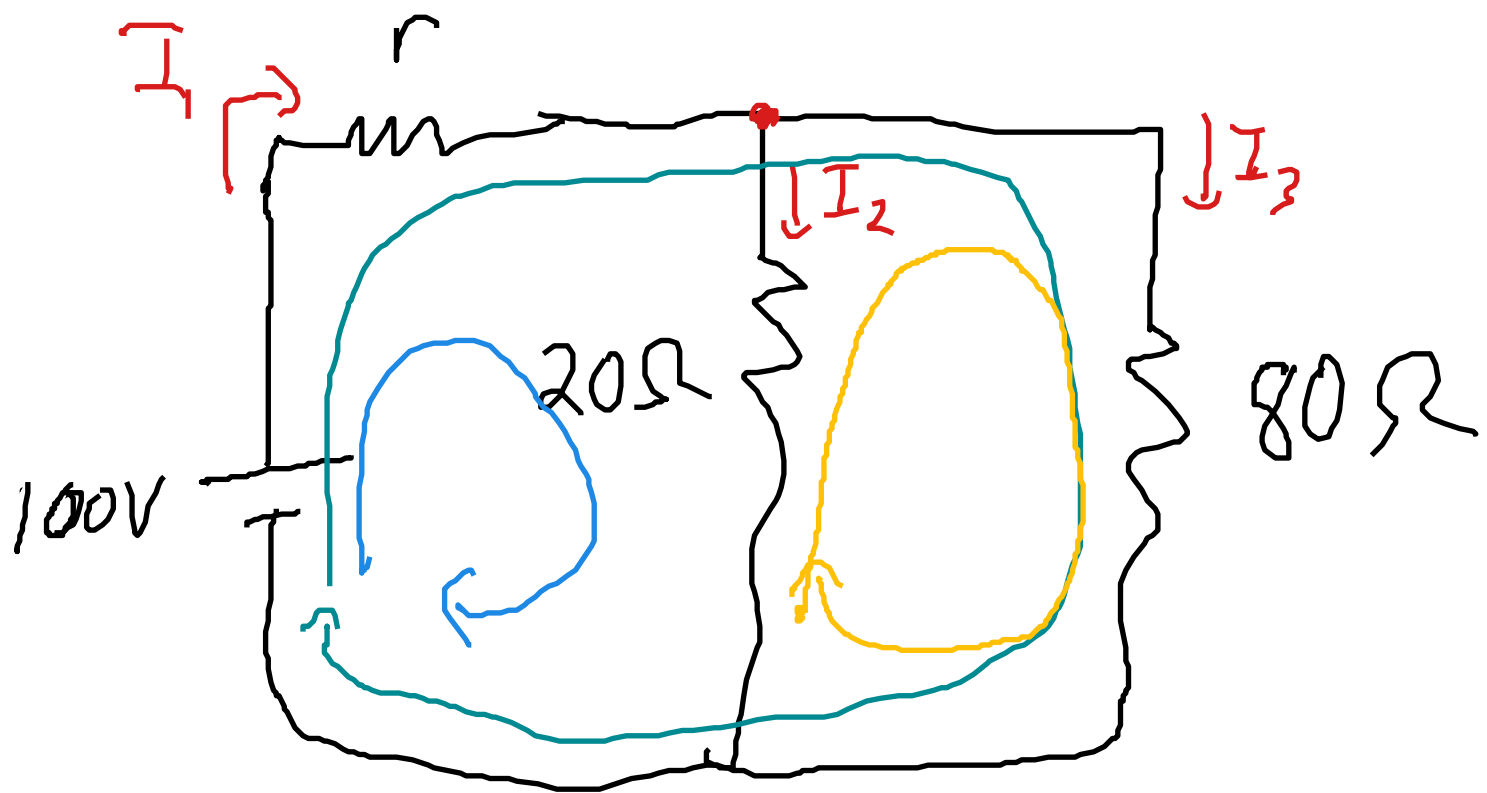




Junction: $I_1 = I_2 + I_3$

Loop: $100 - I_1 r - 20 I_2 = 0$

$100 - I_1 r - 80 I_3 = 0$

$20 I_2 - 80 I_3 = 0$

$$20 I_2 - 80 I_3 = 0$$

$$20 I_2 = 80 I_3$$

$$I_2 = 4 I_3$$

$$I_1 = I_2 + I_3$$

$$= 4 I_3 + I_3$$


$$I_1 = 5 I_3$$

$$100 - r(5 I_3) - 20(4 I_3) = 0$$

$$100 = I_3(5r + 80)$$

$$I_3 = \frac{20}{16+r} \quad I_1 = \frac{100}{16+r}$$

$$I_2 = \frac{80}{16+r}$$

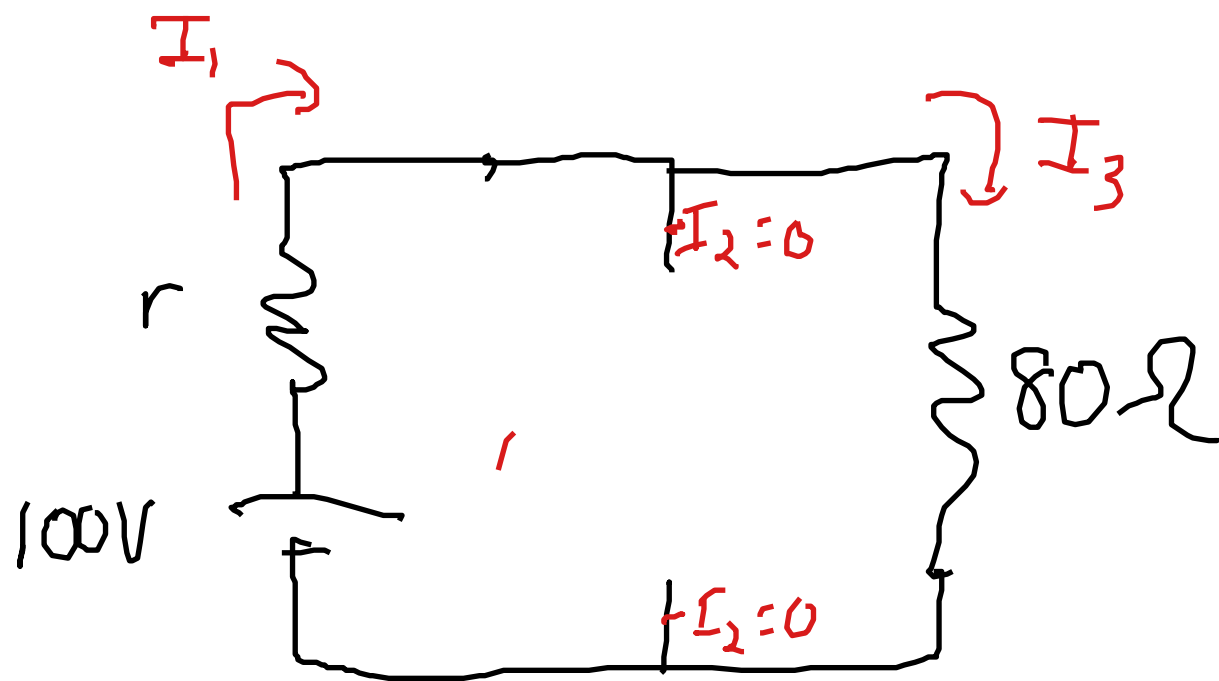

$$I_1 = I_3$$

$$100 - I_1 r - 80 I_3 = 0$$

$$100 - I_1 r - 80 I_1 = 0$$

$$100 = I_1 (80 + r)$$

$$I_3 = I_1 = \frac{100}{80 + r}$$

with 20Ω

$$I_3 = \frac{20}{16+r}$$

without 20Ω


$$I_3 = \frac{100}{807} \cdot \frac{1}{5}$$

$$= \frac{20}{16+(r/5)}$$

If r is tiny ($r \rightarrow 0$)

then these two currents
are roughly the same

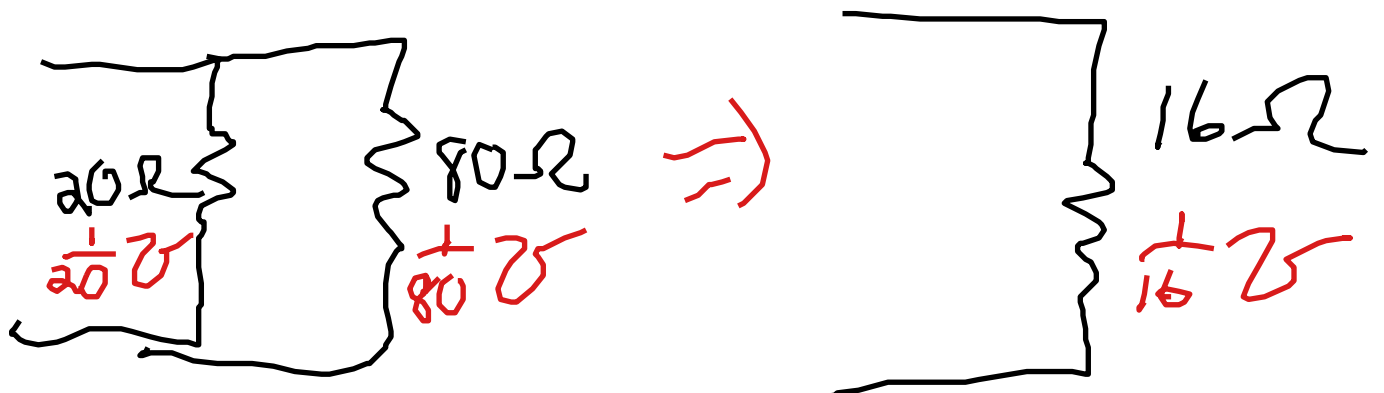If $r \ll 16\Omega$ then
internal resistance doesn't matter



If $r \ll R_{eq}$ of
parallel resistors, then
it doesn't matter

$$R_{eq} < R_1, R_2, \dots$$

if $r \ll R_1, R_2, \dots$

then we're probably OK.

So house wiring works well
(all devices are independent)
so long as all resistors are
much greater than the internal
resistance.

But low-resistance devices
 can mess ϵ/h up

high $\rightarrow P = \frac{(\Delta V)^2}{R}$


$\leftarrow$ const

$\leftarrow$ low

vacuum cleaners

microwaves

space heaters

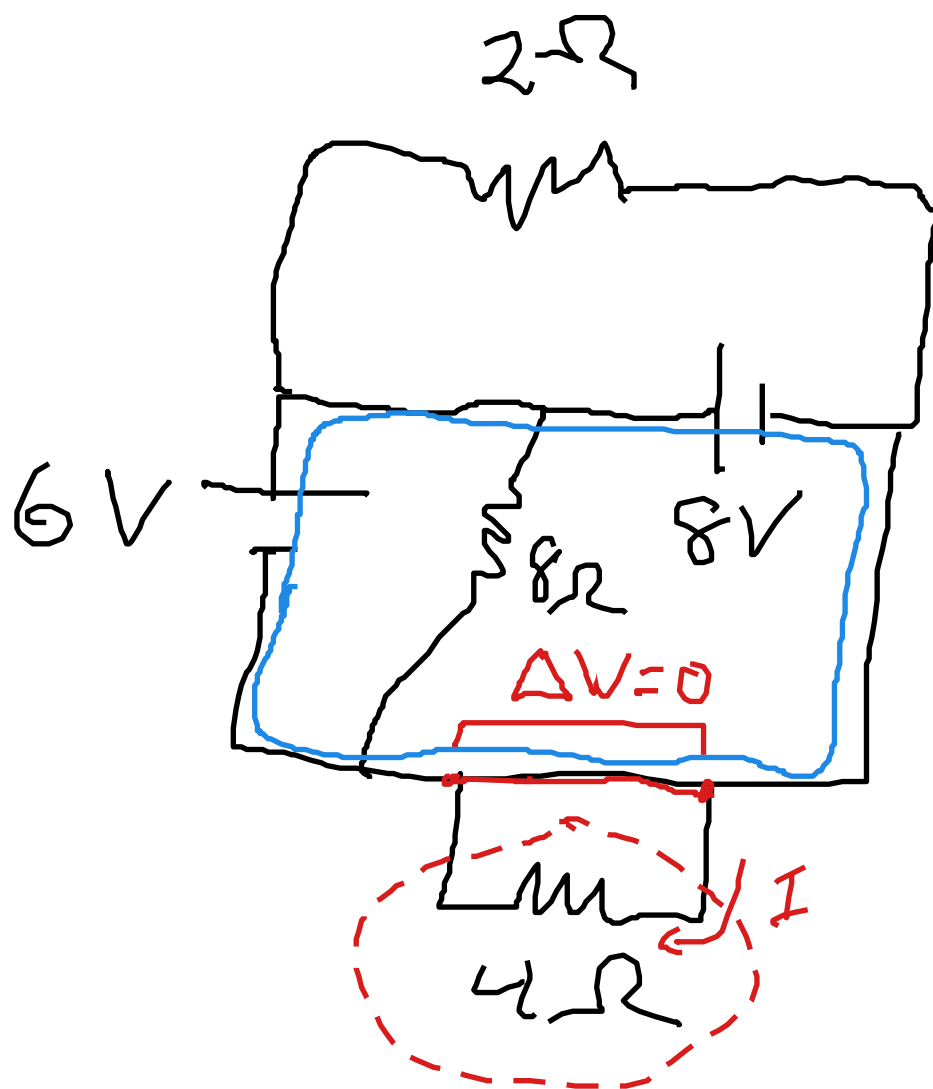

$$\Delta V = IR$$

$$0 = I(4)$$

$$I = 0$$

resistor is
 "short-circuited"
 - gets no current

$$+6 - 8 = 0$$

$$-2 = 0 \text{ ? ? ! ? ? }$$

short-circuiting the batteries
 here tiny

$$+6 - 8 - I r_{\text{wire}} = 0$$


Ammeters

2

Voltmeters

measure current

measure ΔV

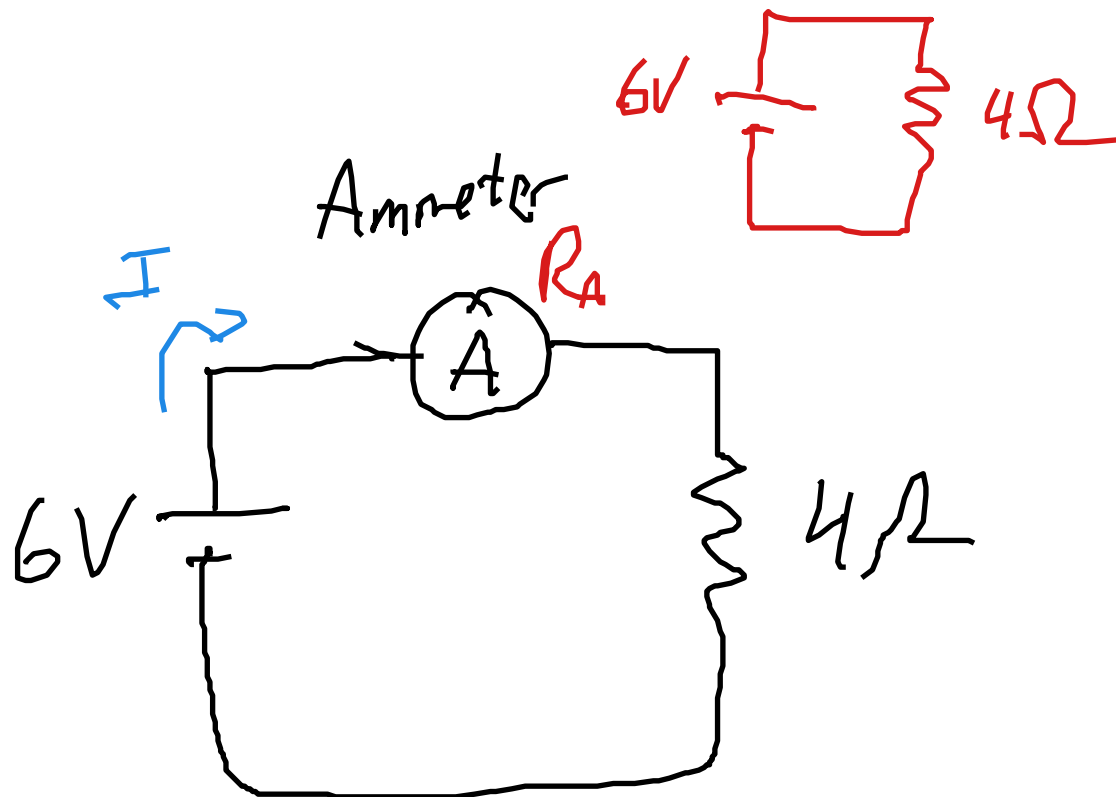

placed in
series with
the current
they're measuring


$$6 - IR_A - 4I = 0$$

$$I = \frac{6}{4 + R_A}$$

ammeters have tiny resistance


behave like a wire

Voltmeter

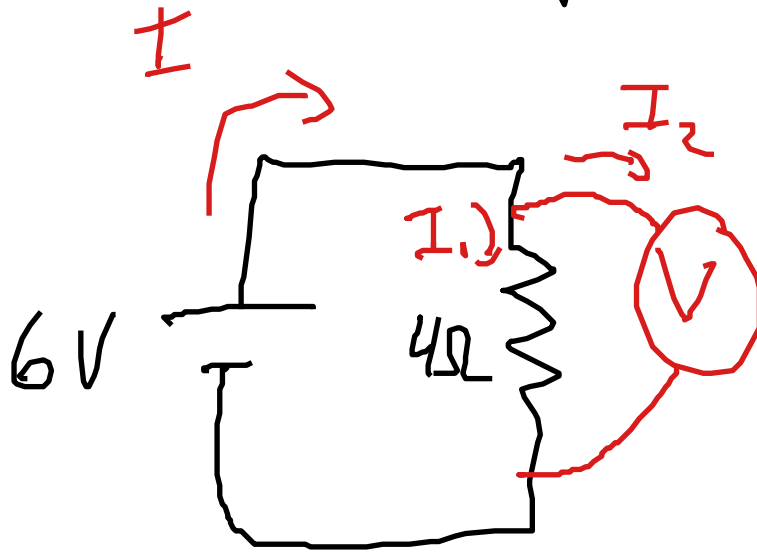


is placed in parallel with the device it's measuring

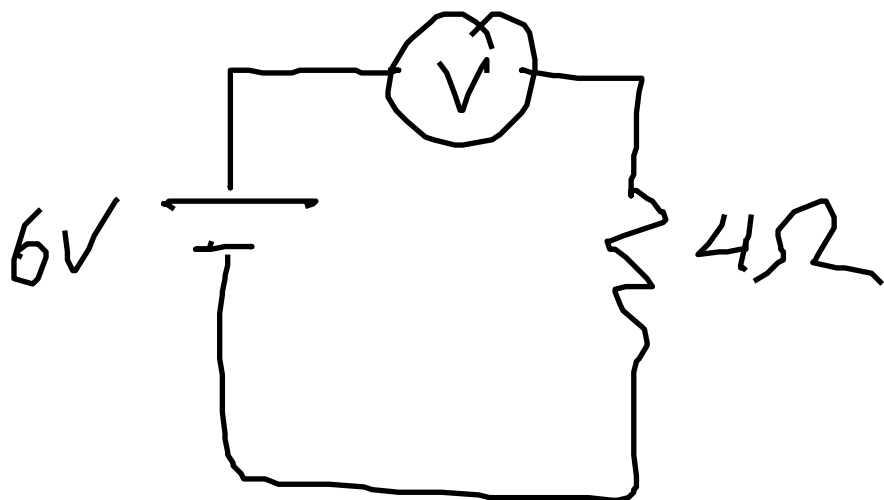voltmeters have huge resistance to avoid interference



no current

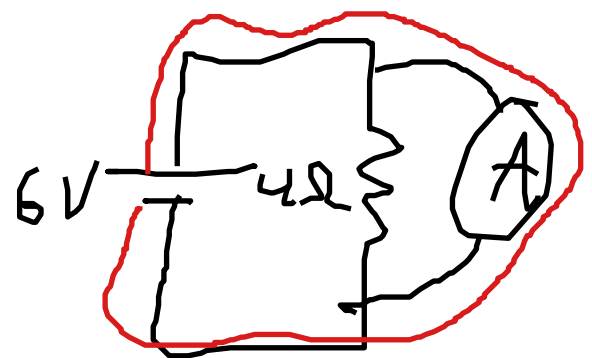

short-circuits the battery
(fuse is blown)