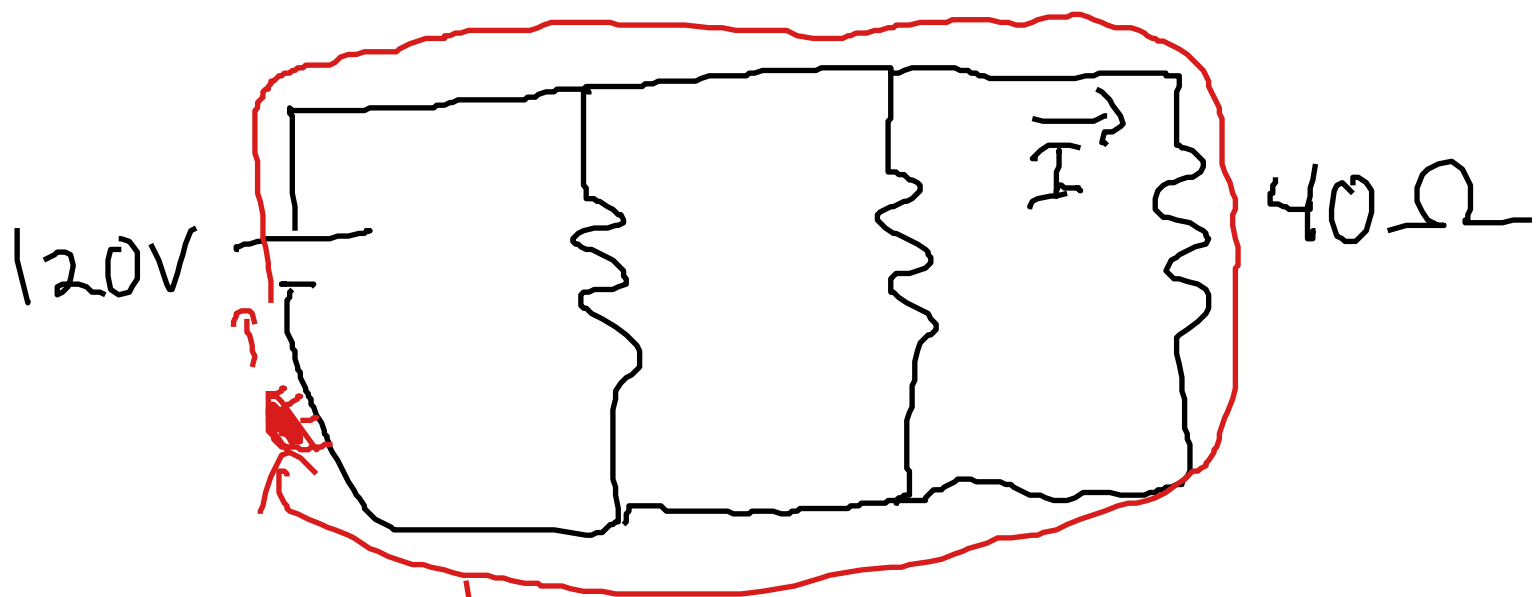




"ladybug" takes a walk around
 circuit keeping track of
 changes of potential.
 Returns to start? Total $\Delta V = 0$

$$+120 - 40I = 0$$

$$120 = 40I$$


$$3A = I$$

regardless of other parts
 of circuit

In a real house

battery

power supply

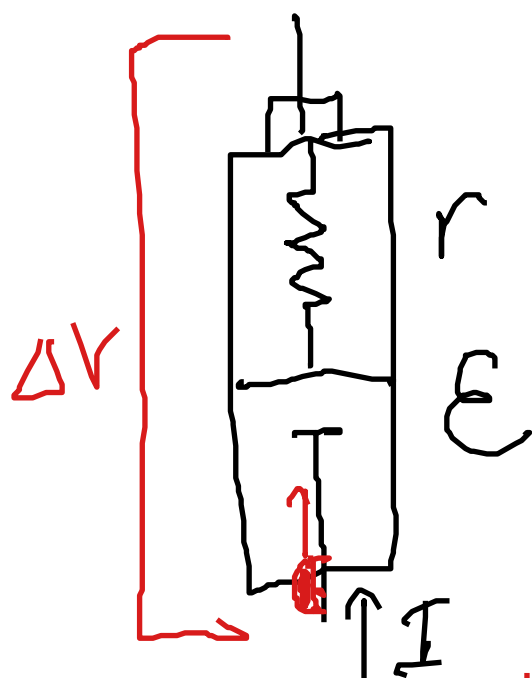


internal
resistance

up
battery


down
stream

$$\Delta V = +\mathcal{E} - Ir$$

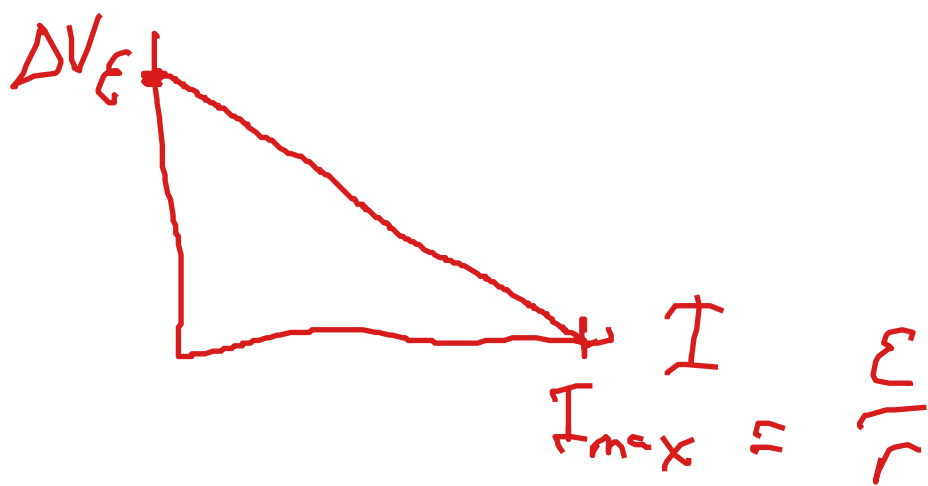

$$P = I \Delta V = I(\mathcal{E} - Ir)$$

$$= \mathcal{E}I - I^2 r$$

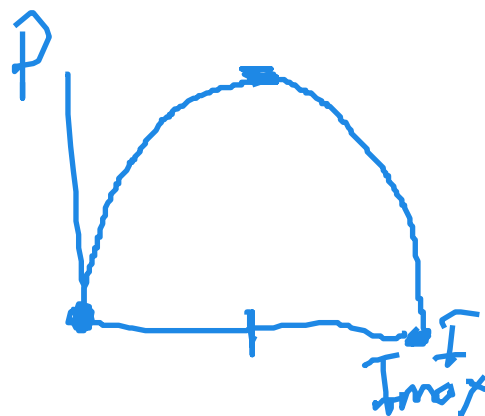

max P occurs where

$$\frac{dP}{dI} = 0$$

$$\frac{dP}{dI} : \mathcal{E} - 2Ir = 0$$

$$I = \frac{1}{2} \frac{\mathcal{E}}{r} = \frac{1}{2} I_{\max}$$

$$P_{\max} = P\left(\frac{1}{2} \frac{\mathcal{E}}{r}\right)$$



$$= \left(\frac{1}{2} \frac{\mathcal{E}}{r}\right) \left(\mathcal{E} - \left(\frac{1}{2} \frac{\mathcal{E}}{r}\right) r\right)$$

$$= \frac{1}{2} \frac{\mathcal{E}^2}{r} - \frac{1}{4} \frac{\mathcal{E}^2}{r}$$

$$= \frac{1}{4} \frac{\mathcal{E}^2}{r}$$

small r : large $P_{\max}$


large r : small $P_{\max}$

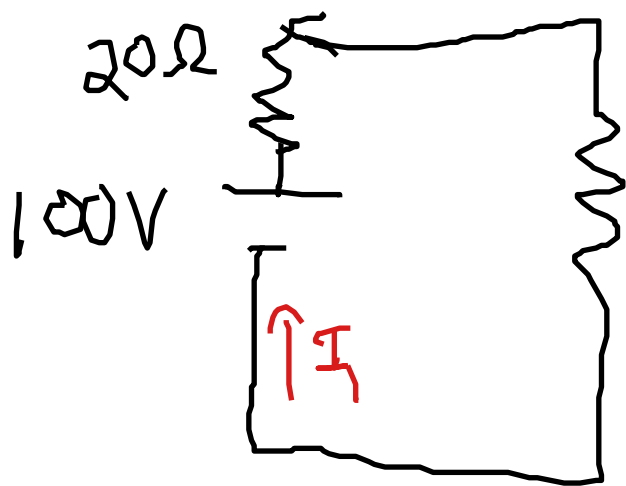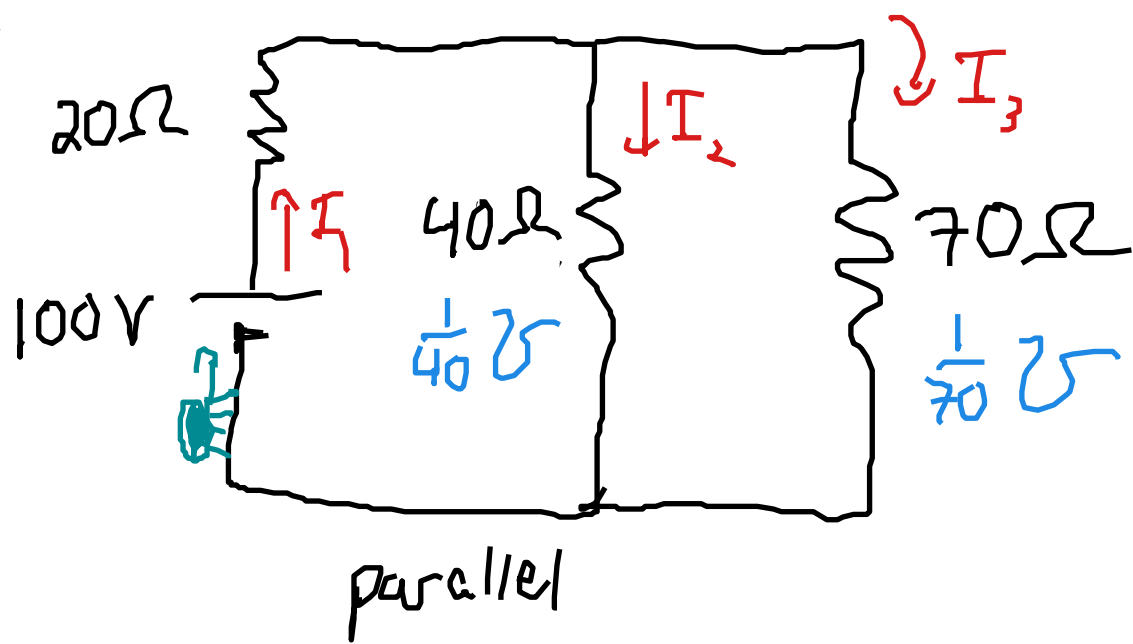

$$25.5 \Omega$$

$$\frac{1}{40} + \frac{1}{70} = 0.0393$$

series

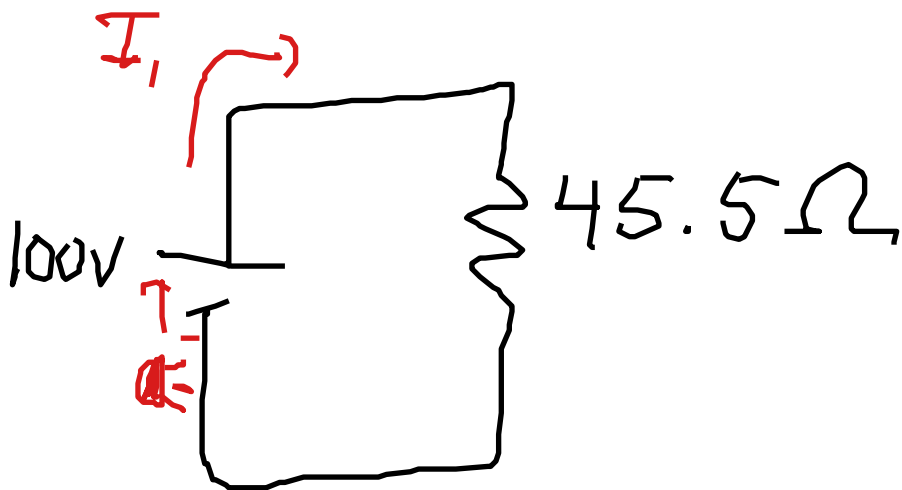

$$100 - 45.5 I_1 = 0$$

$$100 = 45.5 I_1$$

$$I_1 = \frac{100}{45.5} = 2.2 \text{ A}$$

5

$$100 - 20(2.2) - 40I_2 = 0$$

$$100 - 44 - 40I_2 = 0$$

$$56 = 40I_2$$


$$I_2 = \frac{56}{40} = 1.4A$$

$$100 - 20(2.2) - 70I_3 = 0$$

$$56 = 70I_3$$

$$\frac{56}{70} = I_3$$

$$0.8A = I_3$$

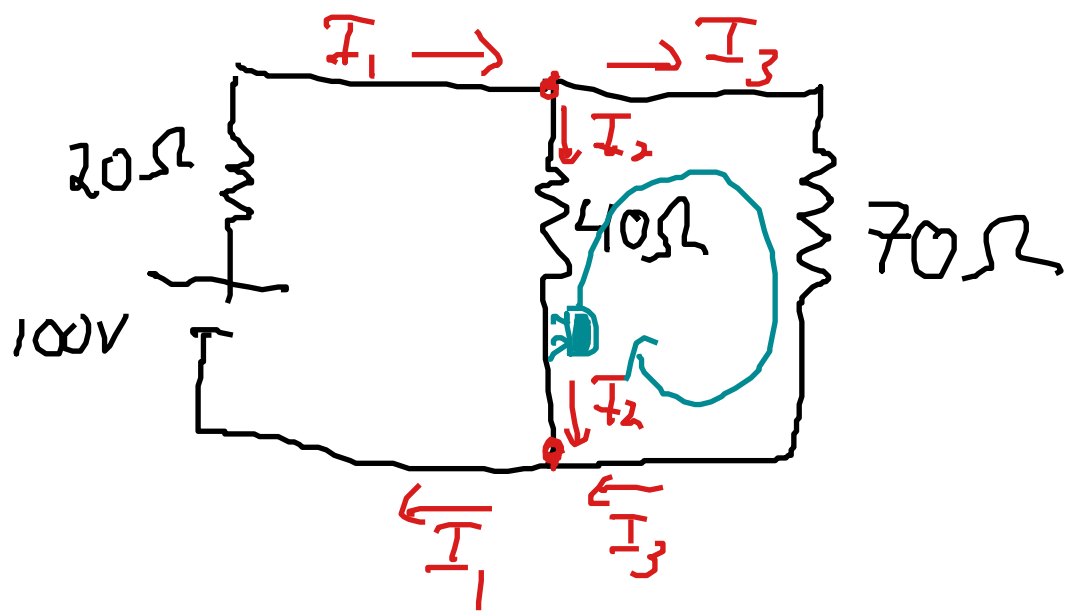

3 unknowns
need 3
equations

Junction Rule

current in = current out

$$I_1 = I_2 + I_3 \quad \checkmark$$

Loop Rule

left: $100 - 20I_1 - 40I_2 = 0$

Big: $100 - 20I_1 - 70I_3 = 0$

up the 40Ω

Right: $+40I_2 - 70I_3 = 0$