
Physics 2140 Homework #8

4 problems Solutions

▷ 1.

A cylindrical wire of length 1 m and radius 5 mm is made of copper, which has a resistivity of $\rho = 17 \times 10^{-9} \Omega \cdot \text{m}$. One end of the wire is 5 V higher than the other.

- (a) Find the resistance of the wire.
- (b) Find the current through the wire.
- (c) Find the power dissipated by the wire.

Answer: _____

(a) The resistance of a wire is

$$R = \rho \frac{L}{A} = \rho \frac{L}{\pi r^2} = (17 \times 10^{-9} \Omega \cdot \text{m}) \frac{1 \text{ m}}{\pi (0.005 \text{ m})^2} = 2.16 \times 10^{-4} \Omega = \boxed{0.21 \text{ m}\Omega}$$

(b) The current through the wire is given by Ohm's Law

$$I = \frac{\Delta V}{R} = \frac{5 \text{ V}}{2.16 \times 10^{-4} \Omega} = \boxed{23 \text{ kA}}$$

which is huge.

(c)

$$P = I \Delta V = (23 \text{ kA})(5 \text{ V}) = 1.15 \times 10^5 \text{ W} = \boxed{115 \text{ kW}}$$

▷ 2.

A human being can be electrocuted if a current as small as 50 mA passes near the heart. An electrician working with sweaty hands makes good contact with the two conductors he is holding, one in each hand. If his resistance is 2000Ω , what might the fatal voltage be?

Answer: _____

For a resistance $R = 2000 \Omega$, the potential difference required to create a current $I = 50 \text{ mA}$ is

$$\Delta V = IR = (50 \text{ mA})(2000 \Omega) = \boxed{100 \text{ V}}.$$

So a 100 V potential difference (less than the 110 V in normal electrical outlets) could be enough to be fatal. (Note that the resistance of skin can vary significantly depending on if it is wet or dry: from 100Ω for skin soaked in salt water, to $500 \text{ k}\Omega$ for very dry skin.)

▷ **3.**

A 40-watt incandescent light bulb is so called because when connected to a 120 V power supply, it emits 40 watts of power, not all of it as light.

- (a) Find the resistance of a 40 W bulb and a 60 W bulb.
- (b) Find the current through each, if they are connected separately to a 120 V power supply.
- (c) How would the power output of a 40 W light bulb change if it were used in a country where 220 V is the norm? Would it be brighter or dimmer?

Answer: _____

(a) The power output of a resistor is $P = I\Delta V$; because $I = \frac{\Delta V}{R}$ according to Ohm's Law, we can either write the power as

$$P = I^2 R \quad \text{or} \quad P = \frac{(\Delta V)^2}{R}$$

We choose one equation or the other, depending on whether we know I or ΔV . In this case, we hook both light bulbs up to the same 120 V power supply, so ΔV is the same for both, so we use the form

$$P = \frac{(\Delta V)^2}{R} \implies R = \frac{(\Delta V)^2}{P}$$

and the resistances are

$$R_{40} = \frac{(120)^2}{40} = 360 \Omega \quad \text{and} \quad R_{60} = \frac{(120)^2}{60} = 240 \Omega$$

Note that the higher-wattage bulb has the lower resistance.

(b) Since the power output is $P = I\Delta V$ and the drop in potential across each is 120 V, the current through each is $I = \frac{P}{\Delta V}$, or

$$I_{40} = \frac{40 \text{ W}}{120 \text{ V}} = 0.33 \text{ A} \quad \text{and} \quad I_{60} = \frac{60 \text{ W}}{120 \text{ V}} = 0.5 \text{ A}$$

(c) The resistance of the bulb is what stays constant as we go from one country to another: the 40 W light bulb has a resistance of 360Ω . The power output is $P = (\Delta V)^2/R$, so when $\Delta V = 220 \text{ V}$,


$$P = \frac{(220 \text{ V})^2}{360 \Omega} = 134 \text{ W}$$

So the light bulb will be much brighter (unless it burns out). Notice that the power is proportional to the potential difference squared, so a doubling of the voltage quadruples the power output.

▷ 4.

The figure shows an 8 V battery connected in series with a 2Ω resistor and two 1Ω resistors.

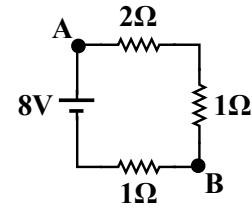- (a) Find the current through the circuit.
- (b) Find the drop in potential ΔV across the 2Ω resistor.
- (c) Find the potential difference between the points marked A and B.



Answer: _____

(a) We use the loop rule here, assuming the current through the circuit is I clockwise. Start at the negative terminal of the battery and move clockwise: we go up the battery (+8), down the first resistor ($-2I$), down the second ($-1I$), and down the third ($-1I$), before returning to the starting point. Thus

$$0 = 8 - 2I - 1I - 1I \implies 8 = 4I \implies I = 2 \text{ A}$$

(b) The potential drop across a resistor is given by Ohm's Law: $\Delta V = IR = (2 \text{ A})(2 \Omega) = 4 \text{ V}$.

(c) If we start at A and go clockwise, then we go down the first resistor ($-2I$) and down the second ($-1I$) and get to B. Thus the potential difference between A and B is

$$\Delta V = V_B - V_A = -2I - 1I = -(2 \Omega)(2 \text{ A}) - (1 \Omega)(2 \text{ A}) = -6 \text{ V}$$

Thus the potential difference between the two points is 6 V ; more specifically $V_B = V_A - 6 \text{ V}$, because V_B is lower than V_A .