


# Physics 2140 Homework #9

## 4 problems

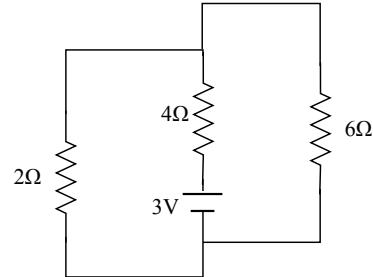**Complete by November 5**


▷ 1.

Find the current through all three resistors.




▷ 2.

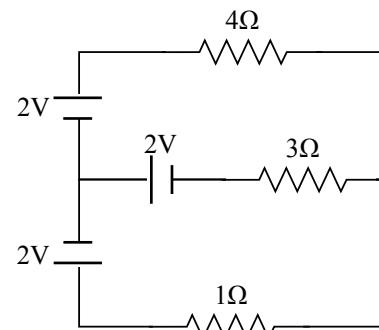Find the current through all three batteries. Note that the current will run backward through at least one battery; assume that this can happen without any difficulty (it will end up recharging the battery).



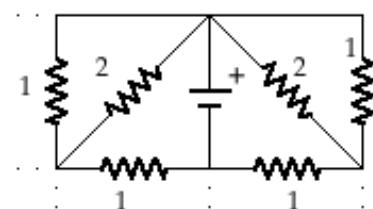3.

In the figure below, the battery has emf  $\mathcal{V} = 5\text{ V}$  and the resistors are all  $1\Omega$  or  $2\Omega$ . Find the effective resistance of all the resistors combined, and find the current through the battery.



▷ 4.

Find the current through the resistor labelled “ $I?$ ”, if all batteries are 3 V and all resistors are  $2\Omega$ . Hint: Simple loops! (Watch the Youtube video linked to on the website if you don’t know what that means.)

